

**Northeastern University
College of Engineering**

EECE2150 Circuits and Signals: Biomedical Applications

Final Exam


April 29, 2015

Name: _____


- Show all work** leading to the solutions.
- Place a box or circle around all final results.**
- You may use your calculators, but are not permitted to share them.
- Turn off your cell phone**, and remove it from your table.
- This test contains **5 problems and one 5-point extra credit problem**. If you need more space, you can write on the back of the pages.

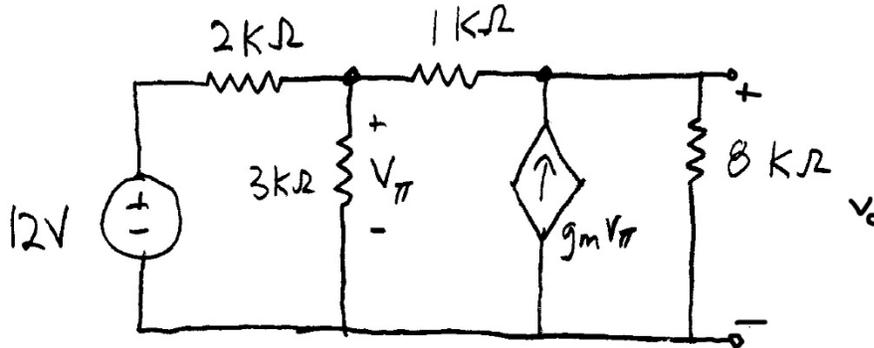1. (20 pts) In the circuit below the $g_m = 0.03 \frac{A}{V}$.
- Write a set of node-voltage equations and an equation of constraint expressing v_π in terms of your node voltages.
 - Put your equations in standard form

$$\begin{bmatrix} A_{11} & A_{12} \\ A_{21} & A_{22} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} d_1 \\ d_2 \end{bmatrix}$$
 - Find the solution for v_o **OR** write the MATLAB commands you would use to find v_o .




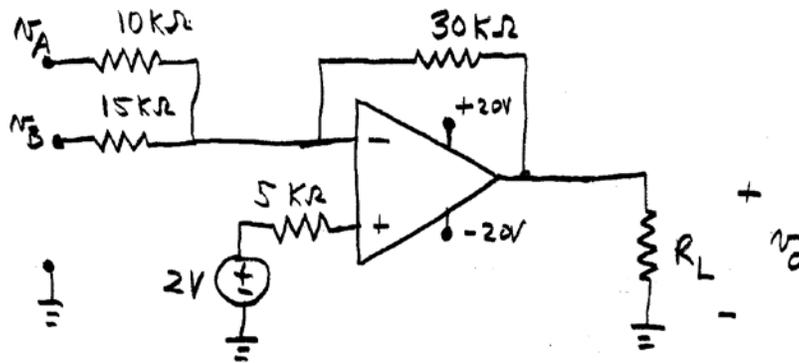2. (20 pts) The op amp in the circuit below can be assumed to be ideal. If $v_A = 4\text{ V}$ and $v_B = 1\text{ V}$ find the output voltage v_o .



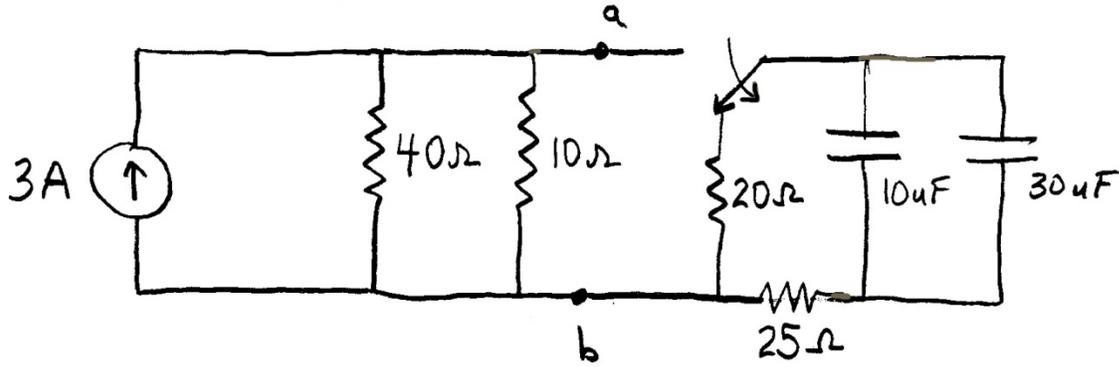3. (20 pts) In the circuit shown, the switch is thrown as shown at time $t = 0$.


- Convert the circuit to the left of points (a)-(b) to a Thevenin voltage source.
- What is the equivalent capacitance of the two capacitors?
- Find an expression for the voltage across the capacitors as a function of time $V_C(t)$.
- What is V_C at $t = 4 \text{ ms}$?





4. (20 pts) In the circuit below $v_s(t) = 3 \cos 8000t$ V

a. Find the steady-state expression for $i_o(t)$

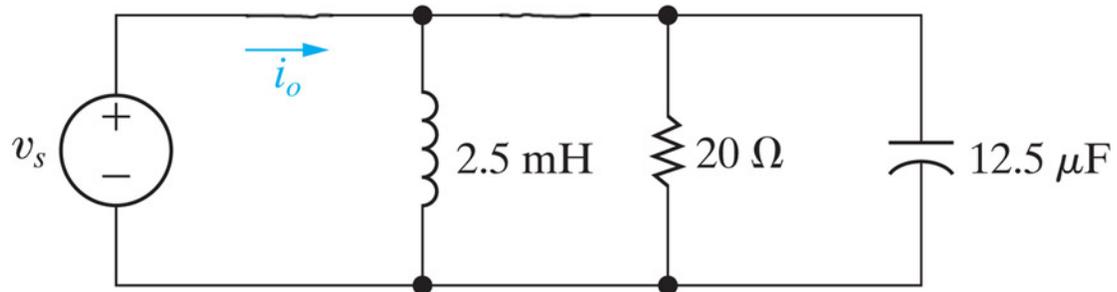b. Find the real power dissipated in the circuit (or equivalently the real power supplied by the source).



5. (20 pts) The following questions refer to the circuit shown.
- Is the op am circuit shown below a low-pass or high-pass filter?
 - Assuming that the capacitor has a value $C=10\ \mu\text{F}$, select values of R_1 and R_2 to give a cut-off frequency of $\omega_0 = 1.0$ radians/s and a high-frequency gain $\left|\frac{V_o}{V_s}\right|=5$.
 - Assuming that you have a V_s that has Fourier components as shown in the graph, sketch what you would expect the Fourier components of V_o to be – i.e. make a plot similar to the one shown below for $V_o(\omega)$.

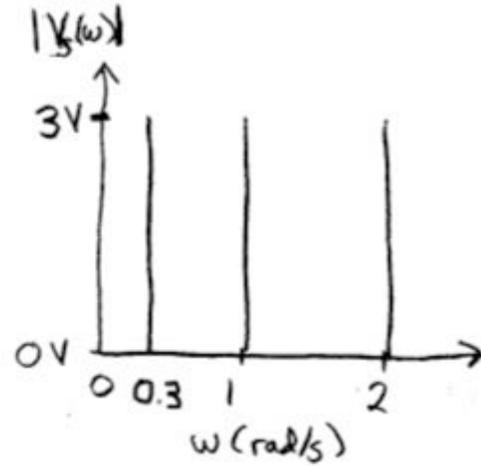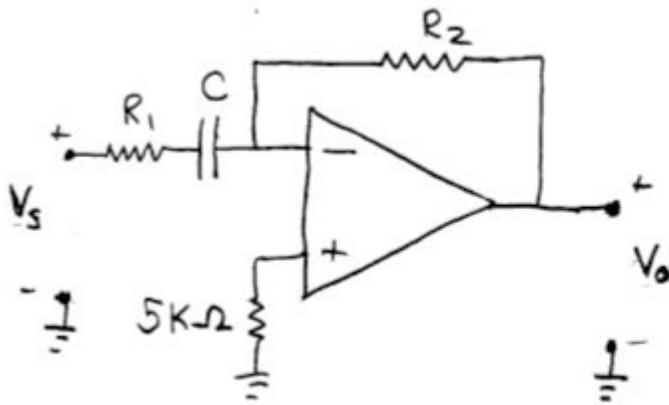

Extra Credit: (5 pts) Derive the frequency at which the transfer function $H(\omega) = V_o/V_i$ of the following circuit is equal to zero.

