

EECE 2150 – Circuits and Signals, Biomedical Applications
Final Exam – Section 3

Name:


Instructions:

- Closed book, closed notes; Computers and cell phones are not allowed
- You may use the equation sheet provided but no other notes or papers
- Scientific calculators are allowed
- **Complete all 6 problems**
- The point value of each question correlates approximately with the length and/or difficulty of the solution. The problems are not necessarily meant to be in order of difficulty.
- Show all work and **place a box around all your final answers**. The more clear your work is the better the chance you will get any appropriate partial credit.
- Show your work for partial credit
- You may write on both sides of the pages but be sure it is clear what problem any work corresponds to.
- Write your name on both sides of all pages. Do that now !!

Question 1 (10 Points)

Name:

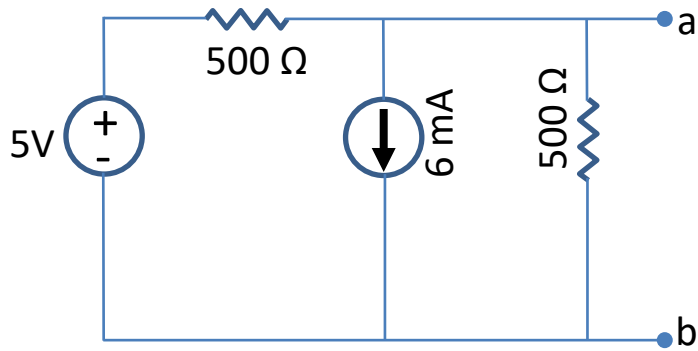1) Find the Thevenin equivalent circuit across terminals a,b for the circuit below:




Answers: $V_{Th} =$

$R_{Th} =$

Question 2 (20 Points)

Name:

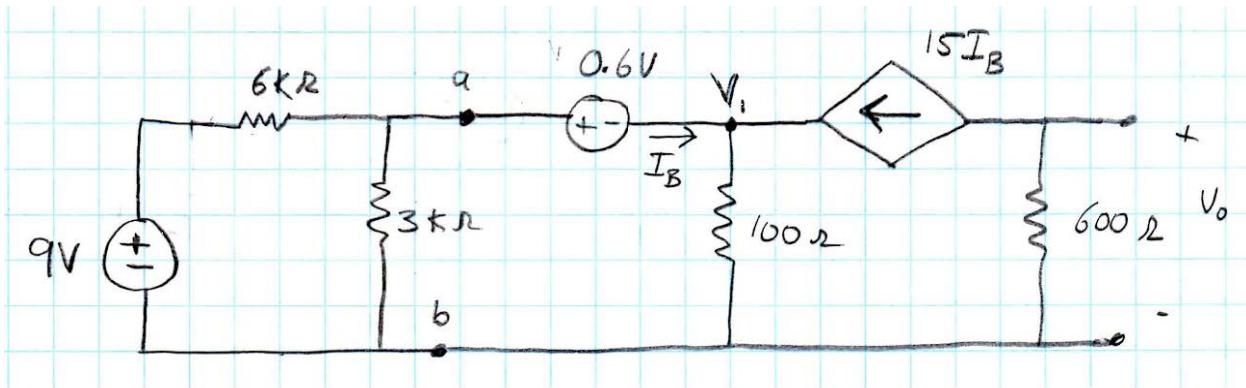

2A) (15 points) Use the node-voltage or mesh-current circuit analysis methods (or any other method you prefer) to solve for V_1 and I_B in the circuit above. Hint: It may simplify your analysis to consider the Thevenin equivalent circuit to the left of terminals (a,b) , but this is optional


2B) (5 points) Find V_o

(extra space on the next page)

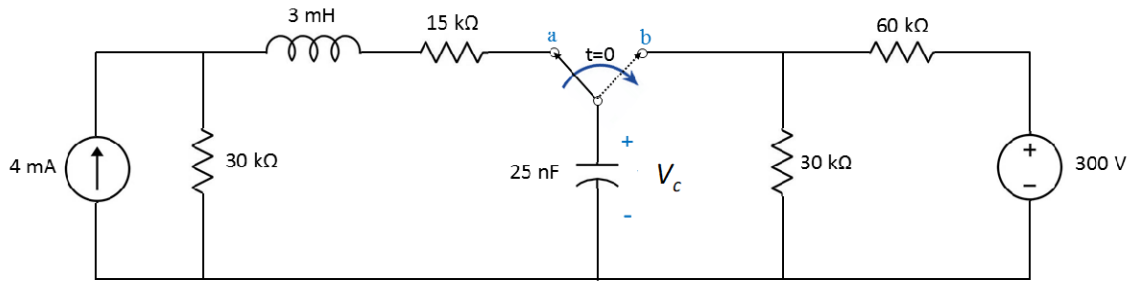Question 3 (16 Points)

Name:

For the circuit below, the switch has been in position (a) for a long time. At time $t=0$ the switch changes to position (b).



3A) **(6 points)** Find the voltage across the capacitor V_c for time $t = 0$, just before the switch changes


3B) **(10 points)** Find and sketch $V_c(t)$ for time $t \geq 0$.

(extra space on the next page)

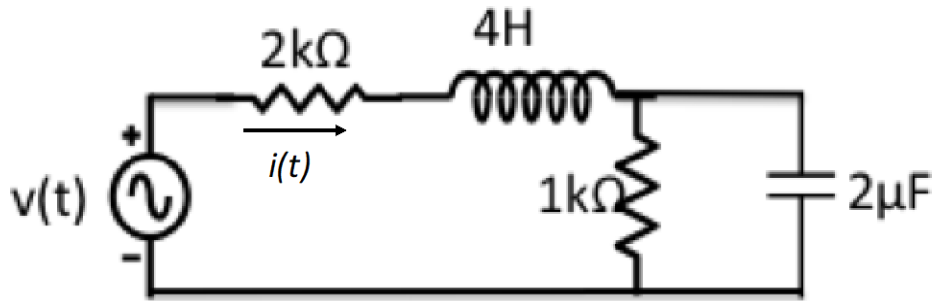Question 4 (20 Points)

Name:

For the circuit below, the voltage source is $v(t) = 2 \cos(500t)$



- (4A) (8 points) What is the equivalent impedance seen by the source? Reduce your answer to a single complex number in either polar or rectangular form.
- (4B) (4 points) What two real circuit elements (e.g. R's, L's, C's, diodes etc.) in **series** will yield the equivalent impedance at the frequency above. State the physical component values, not just the impedance.
- (4C) (8 points) Using the phasor domain analysis technique, find the current produced by the source $i(t)$

(extra space on the next page)

Question 5 (10 Points)

Name:

Assume that you are acquiring (digitizing) an analog signal that is fed directly into the input of an analog-to-digital converter (ADC) with a fixed input range of +/- 25V.


The analog signal has the form: $v(t) = 11 \cos(10,000t + 45^\circ) V$

5A) (4 points) What is the minimum sampling frequency F_s (in samples / second) you would use to avoid distortion? What type of distortion would this prevent?

5B) (6 points) Given the input range of your ADC, assuming your application required a **maximum** quantization error of **1mV** in your digitized signal, what is the minimum number of bits (resolution) your ADC would need? Explain your answer.

Question 6 (24 Points)

Name:

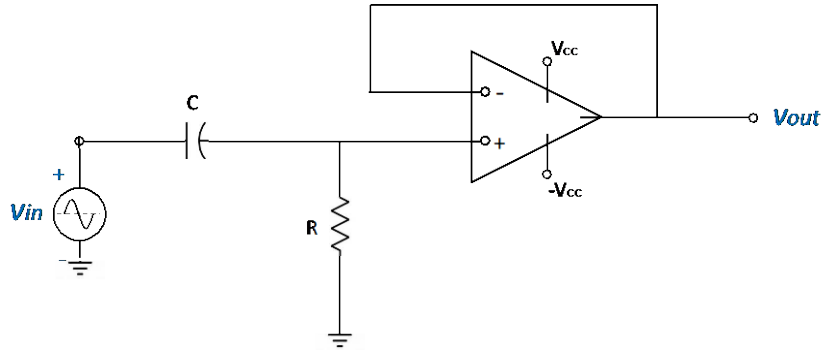

6A) (6 points) Assuming that the op amp is ideal, find an expression for the transfer function $H(\omega) = V_{out}(\omega) / V_{in}(\omega)$ of the circuit above (i.e. in phasor domain) in terms of R , C , and ω

6B) (6 points) On the diagram below, sketch $|H(\omega)| = |V_{out}(\omega) / V_{in}(\omega)|$ as a function of ω . Label your axes, and key points on the curve in terms of R and C . **What kind of filter is this?**



(question continues on the next page)

6C) **(4 points)** Choose values for R and C so that the corner (i.e. cut-on or cut-off) frequency ω_c of the filter is 30,000 radians/s. What is the maximum gain of the resulting circuit ?

6D) **(8 points)** With the values of R and C you picked above, find $V_{out}(t)$ if $V_{in}(t) = 5 + 5\cos(25,000t - 30^\circ) + 5\cos(10^6t)$
If you could not answer the previous part, use $R = 100\text{k}\Omega$ and $C = .5\mu\text{F}$ (Note these are not the correct values for the previous part of the problem!)

Extra credit: **(5 points)**: How would you modify this circuit so that the corner (i.e. cut-off or cut-on) frequency is the same as in your design above but the maximum gain increases by a factor of 5 ?

