


# EECE 2150 - Circuits and Signals: Biomedical Applications Fall 2017 - Section 3, Quiz 8

Prof. Charles A. DiMarzio

9 November 2017

Student Name: \_\_\_\_\_

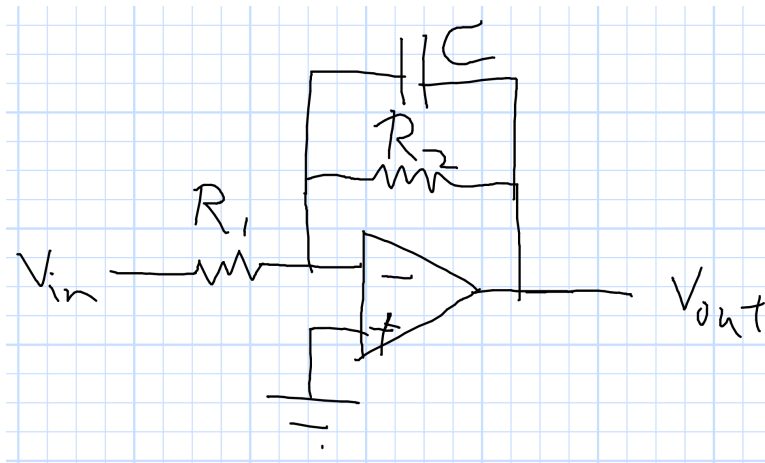Consider the circuit in the figure.  $R_1 = 50\ \Omega$ ,  $C = 10\ \mu\text{F}$ .



1. Select  $R_2$  to provide 26 dB of mid-band gain.

$R_2 =$  \_\_\_\_\_  $\Omega$ .

2. Select  $C$  to provide a cutoff frequency of 16 Hz.

$C =$  \_\_\_\_\_  $\mu\text{F}$ .

3. What is the phase of the gain at very low frequencies? At very high frequencies? Convert to degrees.

$f \rightarrow 0 : \phi =$  \_\_\_\_\_ deg.

$f \rightarrow \infty : \phi =$  \_\_\_\_\_ deg.

1. 20 dB is a factor of 100 in power, and 6 dB is a factor of 4, so the power gain is 400.  $|A_v| = \sqrt{400} = 20$ .

$$\frac{R_2}{R_1} = 20$$

$$R_2 = 1 \text{ k}\Omega.$$

2.

$$f_c = \frac{1}{2\pi R_2 C}$$

$$C = \frac{1}{2\pi R_2 f_c} = 9.95 \mu\text{F}$$

3. At low frequency,

$$A_v = -\frac{R_2}{R_1}$$

. A negative real number has a phase of  $180^\circ$

At high frequency,

$$A_v = -\frac{Z_2}{Z_1} = -\frac{1}{j\omega C R_1}$$

$$= \frac{j}{\omega C R_1} = \frac{\pi}{2}$$

.

A positive real number has a phase of  $90^\circ$ .