

EECE 2150 - Circuits and Signals: Biomedical Applications Fall 2018 - Section 3

Quiz 4

Prof. Charles A. DiMarzio

4 October 2018

Student Name: _____

The circuit shown is an inverting amplifier, with $R_1 = 2\text{ k}\Omega$, $R_2 = 12\text{ k}\Omega$, $R_3 = 2\text{ k}\Omega$, $R_L = 10\text{ k}\Omega$


1. What is the voltage gain of the amplifier?

2. If we connect an ideal voltage source, $V_{in} = 100\text{ mV}$, to the input, what is the current from that source. Assume positive current is from left to right in R_1 .

3. How much power is produced by the source?

4. For the same input, what is the output voltage?

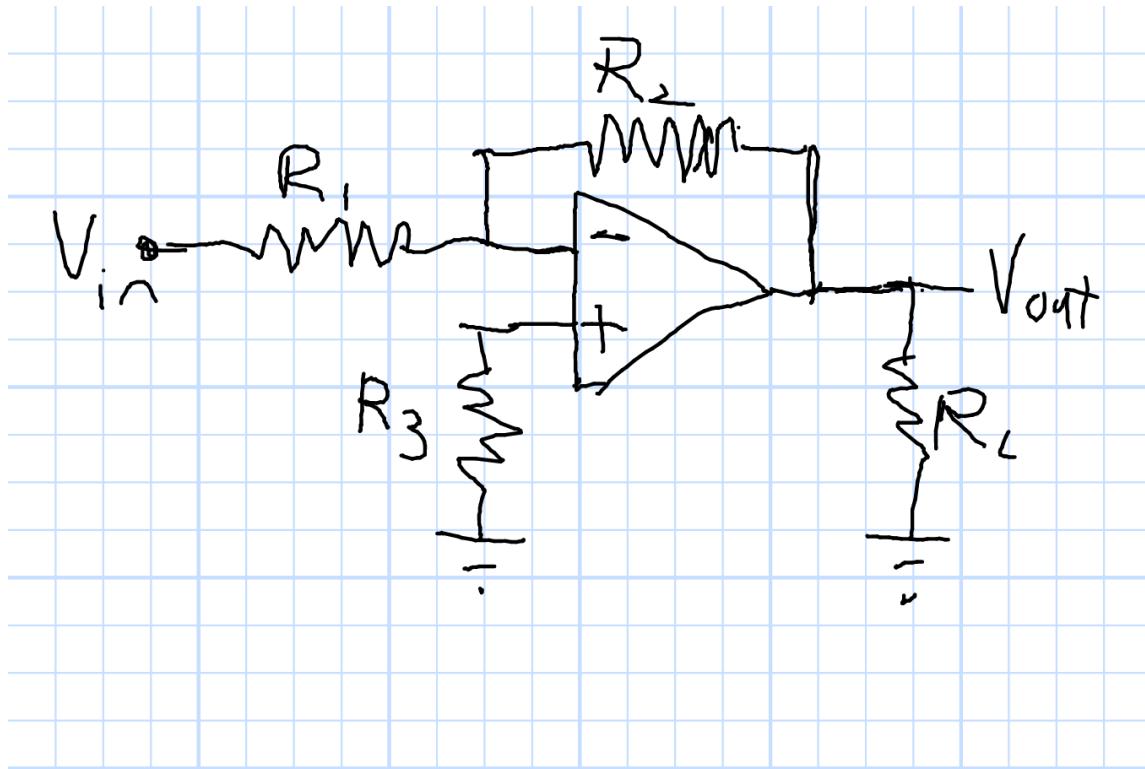5. How much power is absorbed by the load?



1.

$$A_V = -\frac{R_2}{R_1} = -\frac{12 \text{ k}\Omega}{2 \text{ k}\Omega} = -6.$$

2.

$$i = \frac{V_{in} - 0}{R_1} = 100 \text{ mV} / 2 \text{ k}\Omega = 50 \mu\text{A}.$$

Note that R_3 doesn't matter. No current flows in it so $V_+ = 0$.

3.

$$P = iV = 50 \mu\text{A} \times 100 \text{ mV} = 5 \mu\text{W}.$$

4.

$$V_{out} = A_V V_{in} = -6 \times 100 \text{ mV} = -600 \text{ mV}.$$

5.

$$P = \frac{V^2}{R_L} = \frac{(-600 \text{ mV})^2}{10 \text{ k}\Omega} = 36 \mu\text{W}.$$