

EECE 2150 - Circuits and Signals: Biomedical  
Applications Fall 2022  
Quiz 7

Prof. Charles A. DiMarzio

26 October 2023

Student Name: \_\_\_\_\_

The amplifier circuit in the figure is intended to take the derivative of the input voltage,  $v_{in}$ . The capacitor  $C = 1\ \mu\text{F}$ ,  $R_1 \approx 0$ , and  $R_2 = 2\ \text{k}\Omega$ . The amplifier has power supply rails at  $\pm 12\ \text{V}$ .

1. Write the current,  $i_1(t)$  as a function of  $v_{in}(t)$ .

\_\_\_\_\_ .

2. What is the current,  $i_2$  as a function of  $v_{in}(t)$ .

\_\_\_\_\_ .


3. What is  $v_{out}$  as a function of  $v_{in}(t)$ .

\_\_\_\_\_ .

4. What is the “gain?” Be careful here, because by “gain” I mean the ratio of  $v_{out}$  to  $\frac{dv_{in}}{dt}$ . This gain has units. Be sure to include them in the answer.

\_\_\_\_\_ .

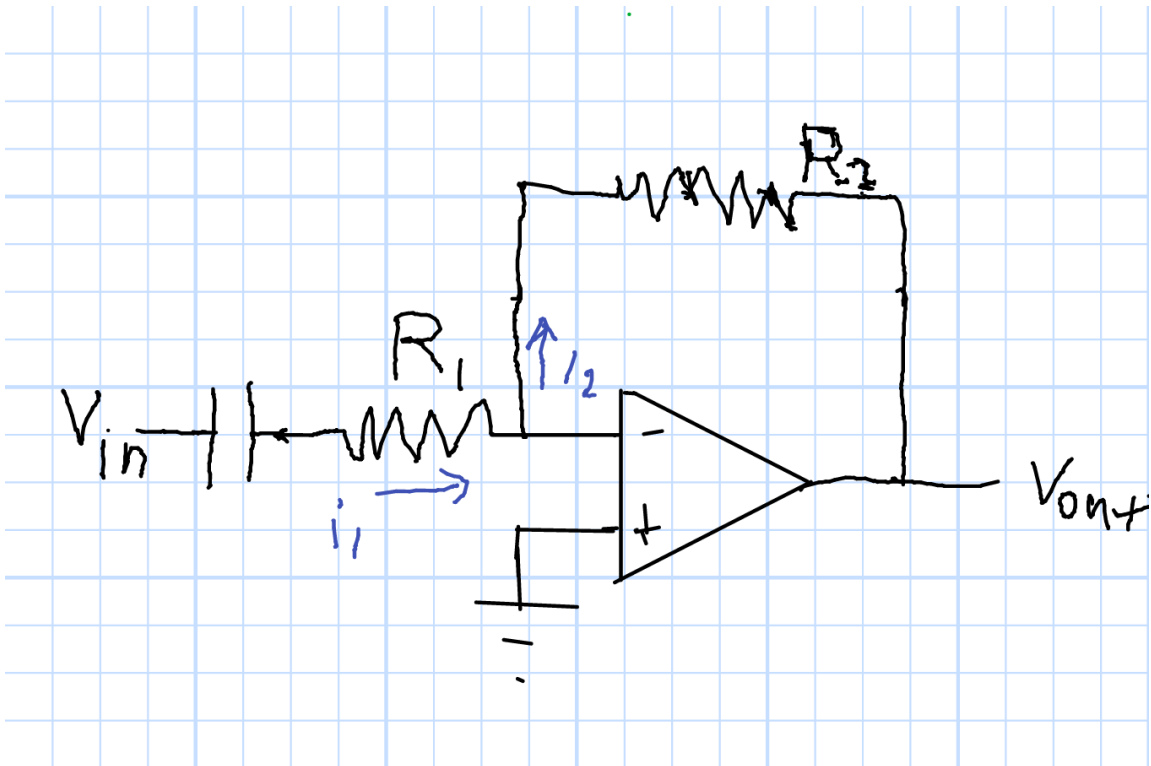5. If the input is a pulse such that  $v_{in} = 1\text{ V}$  for  $0 < t < 5\text{ }\mu\text{s}$ , and zero for all other times, sketch the output.



1.  $i_1 = C \frac{dv_1}{dt}$

2.  $i_2 = C \frac{dv_1}{dt}$

3.  $v_{out} = -R_2 C \frac{dv_1}{dt} = -2 \times 10^{-3} \text{ sec}$

4. Negative 12 volt spike at  $t = 0$  and positive at  $t = 5 \mu\text{s}$ .