

EECE 2150 - Circuits and Signals: Biomedical  
Applications Fall 2023  
Quiz 8

Prof. Charles A. DiMarzio

9 November 2023

Student Name: \_\_\_\_\_

For the filter circuit in the figure, the gain,  $A(f)$  varies with frequency,  $f$ . The component values are  $R_1 = R_2 = 1\text{ k}\Omega$ ,  $C = 318\text{ pF}$ , and  $L = 31.8\text{ mH}$ .

1. What is the gain at very low and very high frequencies?

$A(0) =$  \_\_\_\_\_ .  $A(\infty) =$  \_\_\_\_\_ .

2. Is the gain higher or lower at frequencies in between these extreme values?

Higher       Lower

3. What type of filter is this?


Low Pass       High Pass       Band Pass       Band Stop

4. What is the frequency at which the gain reaches its extreme (maximum or minimum) value?

$f_{center} =$  \_\_\_\_\_ .

5. What is the gain at this frequency?

$A_v =$  \_\_\_\_\_ .

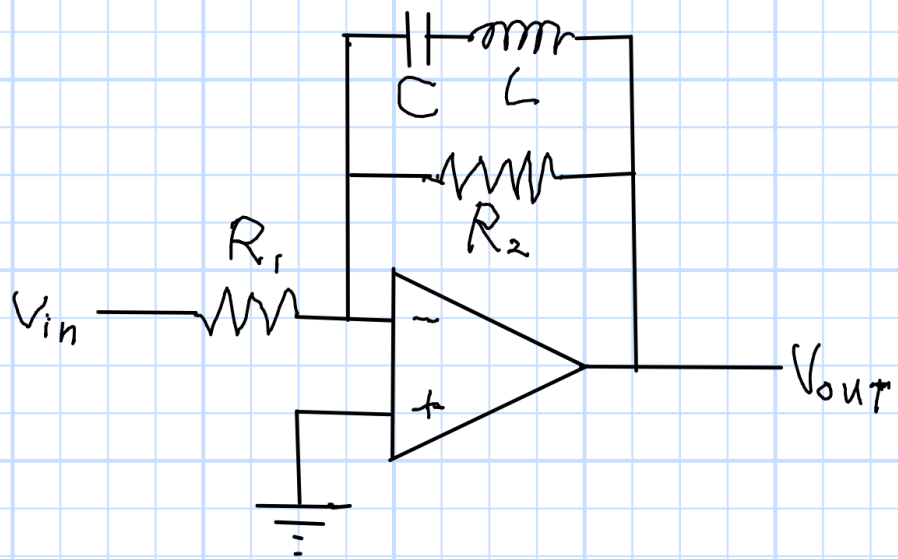

## Solutions

1. What is the gain at very low and very high frequencies?

$$A(0) = -R_2/R_1 = -1 \quad A(\infty) = -R_2/R_1 = -1.$$

2. Is the gain higher or lower at frequencies in between these extreme values?

× Lower

3. What type of filter is this?

× Band Stop

4. What is the frequency at which the gain reaches its extreme (maximum or minimum) value?

$$f_{center} = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = 50 \text{ kHz}$$

5. What is the gain at this frequency?

$$A_v = 0.$$