

Circuits and Signals: Biomedical Applications Week 4

Charles A. DiMarzio
EECE-2150
Northeastern University


Sep 2023

Week 4 Agenda


- Source Transformation
 - Thévenin Equivalent Circuit
 - Norton Equivalent Circuit
- Superposition
- Class Problems
 - Determining Equivalent Circuits
 - Using Equivalent Circuits
- Wheatstone Bridge

Why Equivalent Circuits

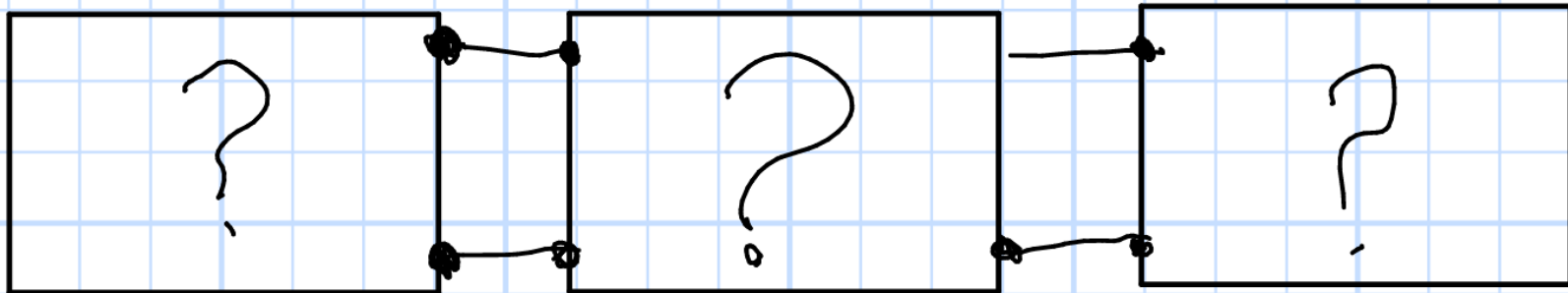
Each box contains a complicated Circuit...



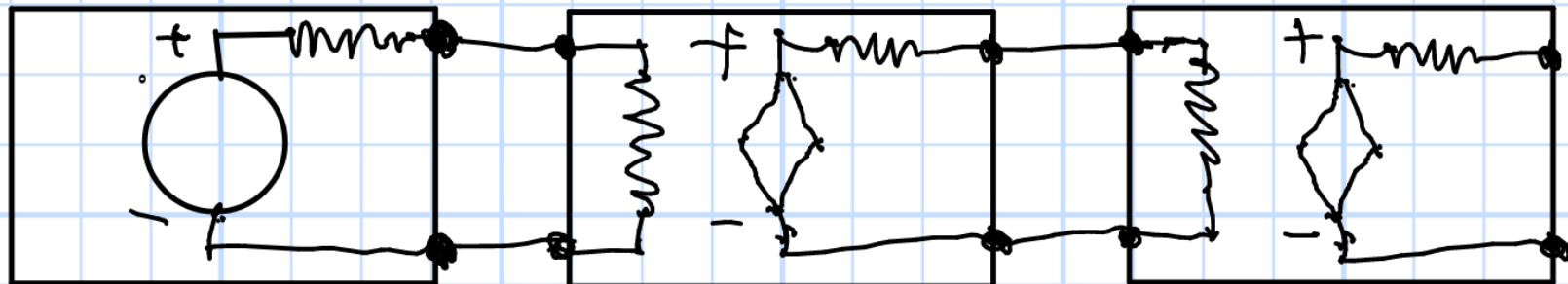
...but we don't really care what is in them.




Equivalent Circuits

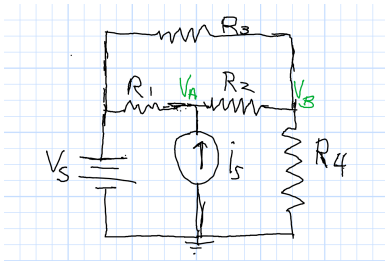


A Circuit

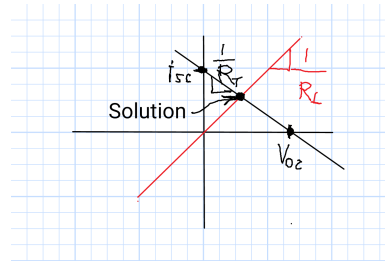

I-V Plots

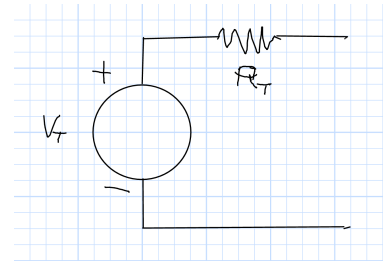

Thévenin

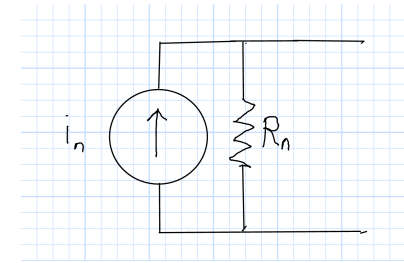

Norton



R_4 is the Load: Analyze everything else.

For a linear circuit, i vs. v is a straight line. Need two of v_{oc} , i_{sc} , R_T

- Calculation Options: Use any one.
 - Calculate V_{oc} and i_{sc}
 - Calculate V_{oc} and R_T
 - Calculate R_T and i_{sc}
- Equivalent Circuits
 - Thévenin: Voltage Source, V_{oc} , with Series R_T
 - Norton: Current Source, i_{sc} , with Parallel $R_N = R_T$

Thévenin Equivalent Circuit
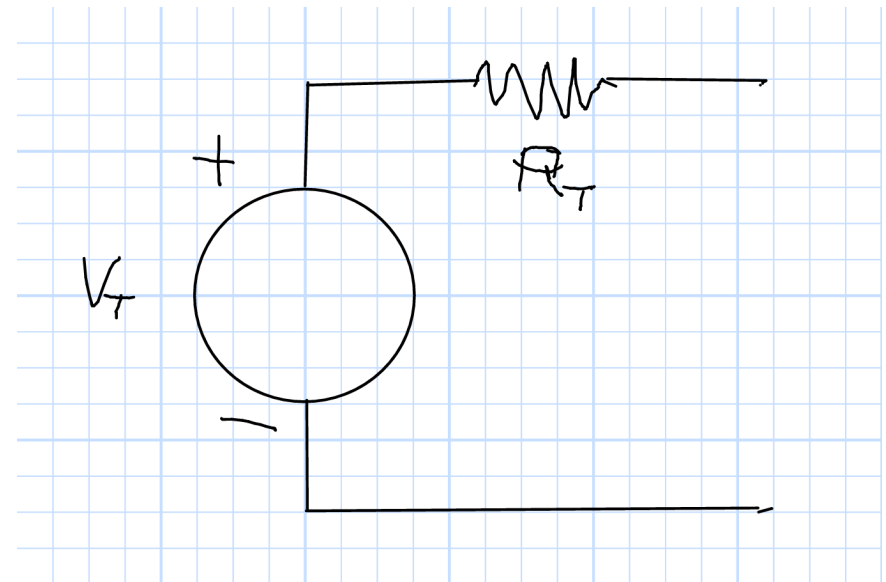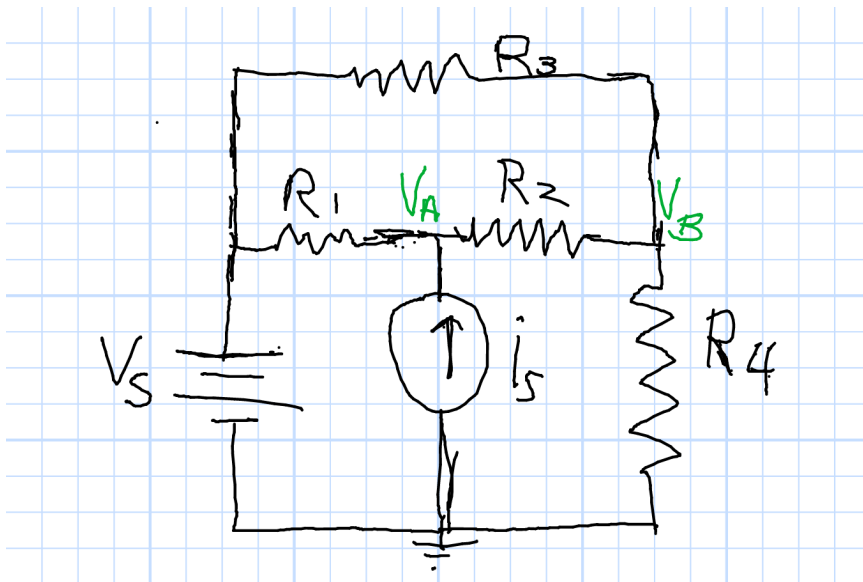
$$R_1 = 1\text{k}\Omega, R_2 = 1\text{k}\Omega, R_3 = 5\text{k}\Omega, v_s = 12\text{V}, i_s = 6\text{mA}$$



R_4 is the Load: Draw a circuit for everything else.


Linear Circuits: i vs. v is a straight line.

We need two points to determine the line.

$i = 0$: Open Circuit Voltage. $v = 0$: Short-Circuit Current

Load Resistor: $i = \frac{v}{R_4}$ Everything Else: $i = \frac{v_T - v}{R_T}$


Thévenin Concept

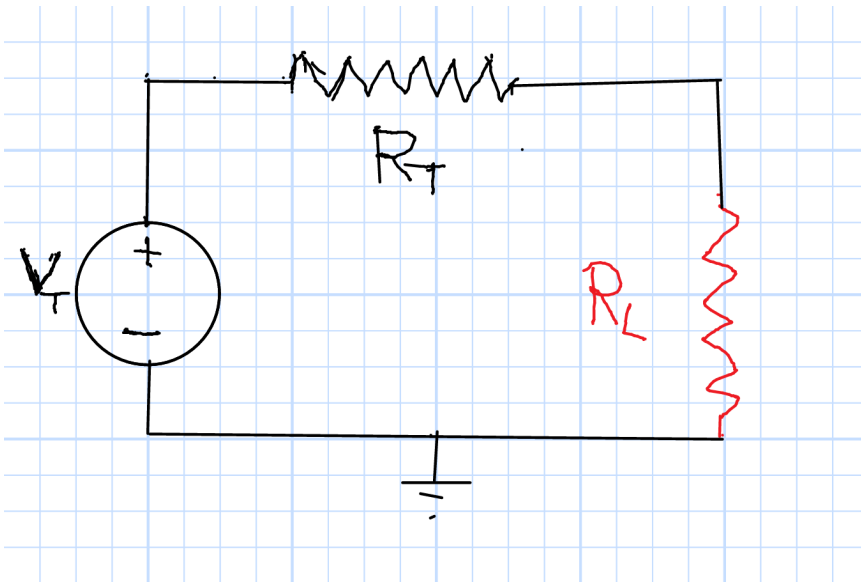

Circuit Equation

$$i = \frac{v_T - v}{R_T}$$

Load Line



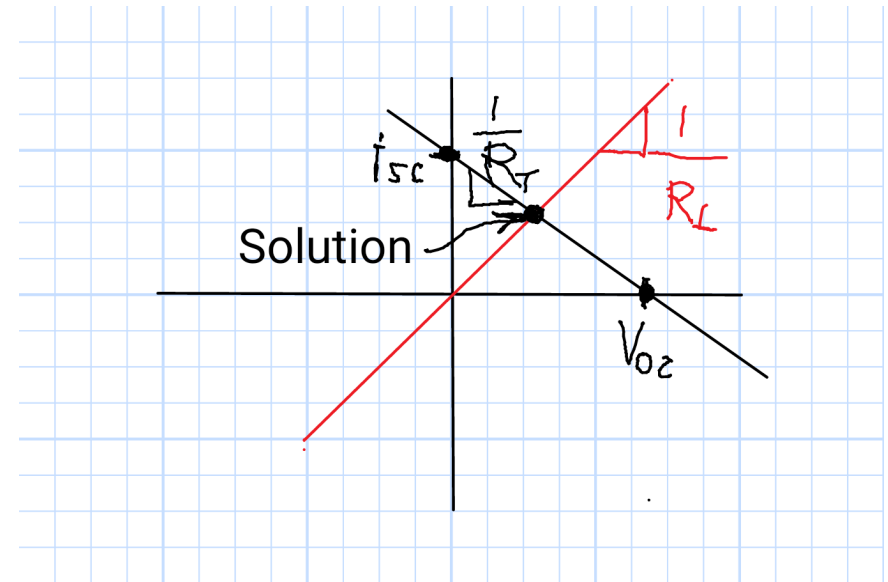


Load Equation

$$i = \frac{v}{R}$$




Solution is at the intersection.

Thévenin Calculation: v_{oc} , i_{sc}

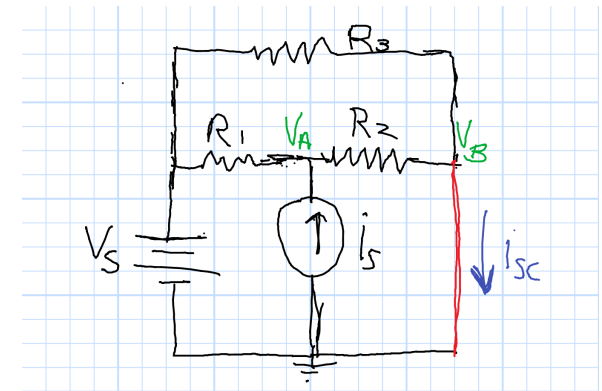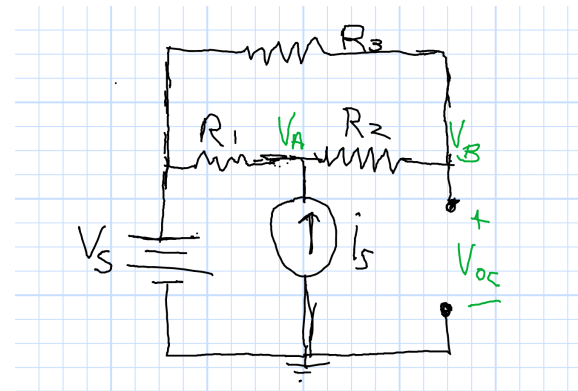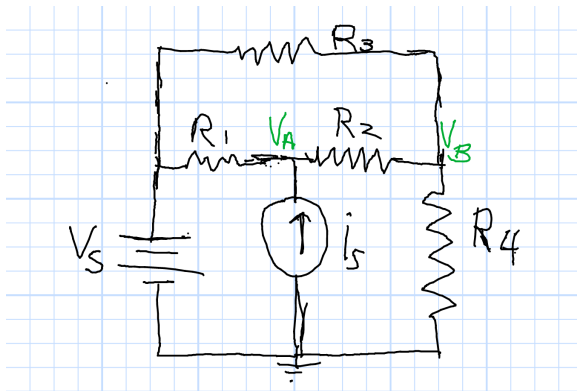



- Calculate Open–Circuit Voltage, v_{oc} .
- Calculate Short–Circuit Current, i_{sc} .
- Find Equivalent Circuit, $v_T = v_{oc}$ and $R_T = \frac{v_{oc}}{i_{sc}}$.

Thévenin Calculation

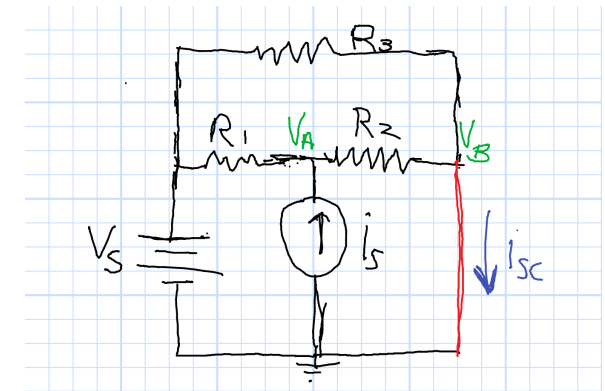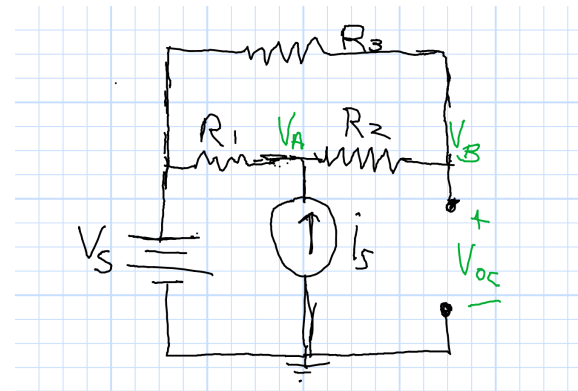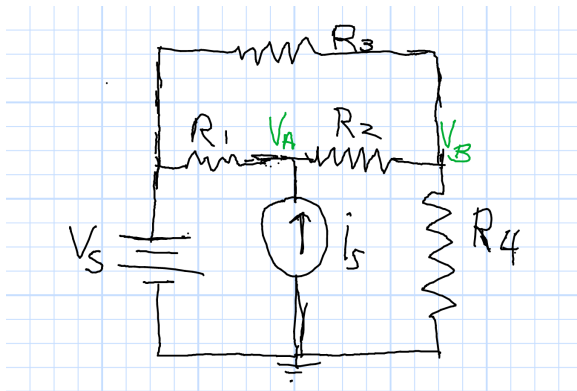

- OC: Draw with one equivalent resistor: $v_A = v_s + i_s [R_1 \parallel (R_2 + R_3)]$,
Voltage Divider: $v_{oc} = v_s + (v_A - v_s) \frac{R_3}{R_3 + R_2} = 16.28\text{V}$.
- SC: $\frac{v_s - v_A}{R_1} + i_s - \frac{v_A}{R_2} = 0$, $\left(\frac{1}{R_1} + \frac{1}{R_2}\right) v_A = \frac{v_s}{R_1} + i_s$
 $v_A = 9\text{V}$, $i_{sc} = \frac{v_s}{R_3} + \frac{v_A}{R_2} = 11.4\text{mA}$
- Equivalent Circuit, $v_T = 16.28\text{V}$ and $R_T = \frac{v_{oc}}{i_{sc}} = 1430\text{Ohms}$.

Alternative: Find R_T

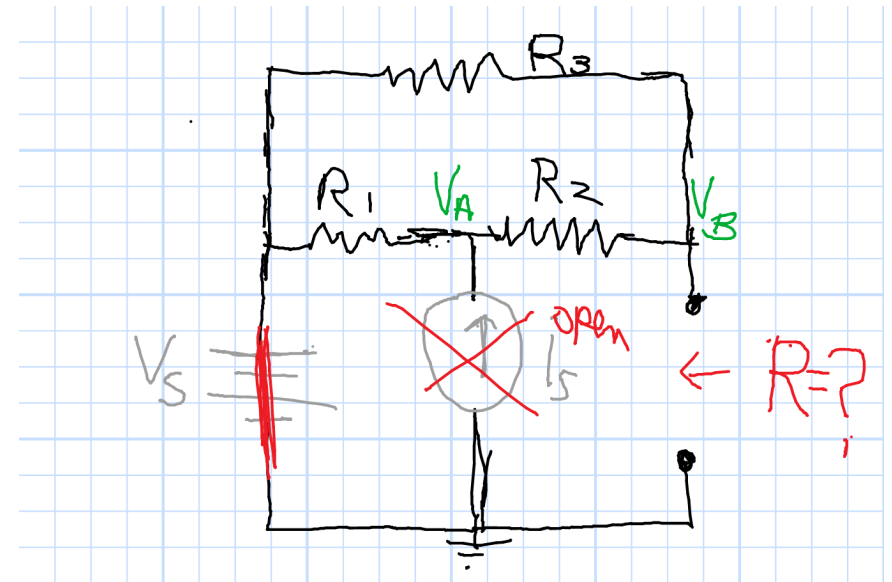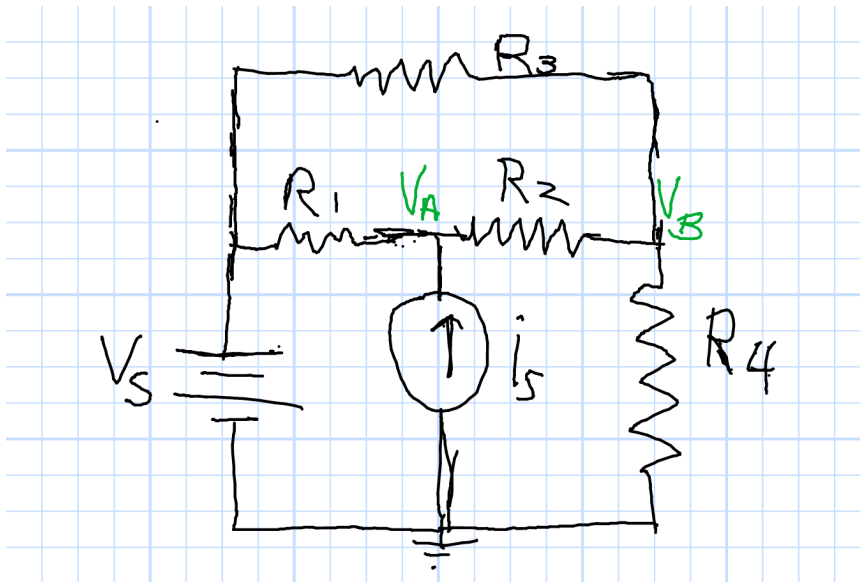

Zero the Sources:

Voltage Sources Shorted ($v = 0$)


Current Sources Opened ($i = 0$)

Use Series and Parallel Combinations

Do This if v_{oc} or i_{sc} Looks Messy.


In This Example, $R_T = (R_1 + R_2) \parallel R_3 = 1430\text{Ohms}$

Thévenin Example: Parallel Batteries

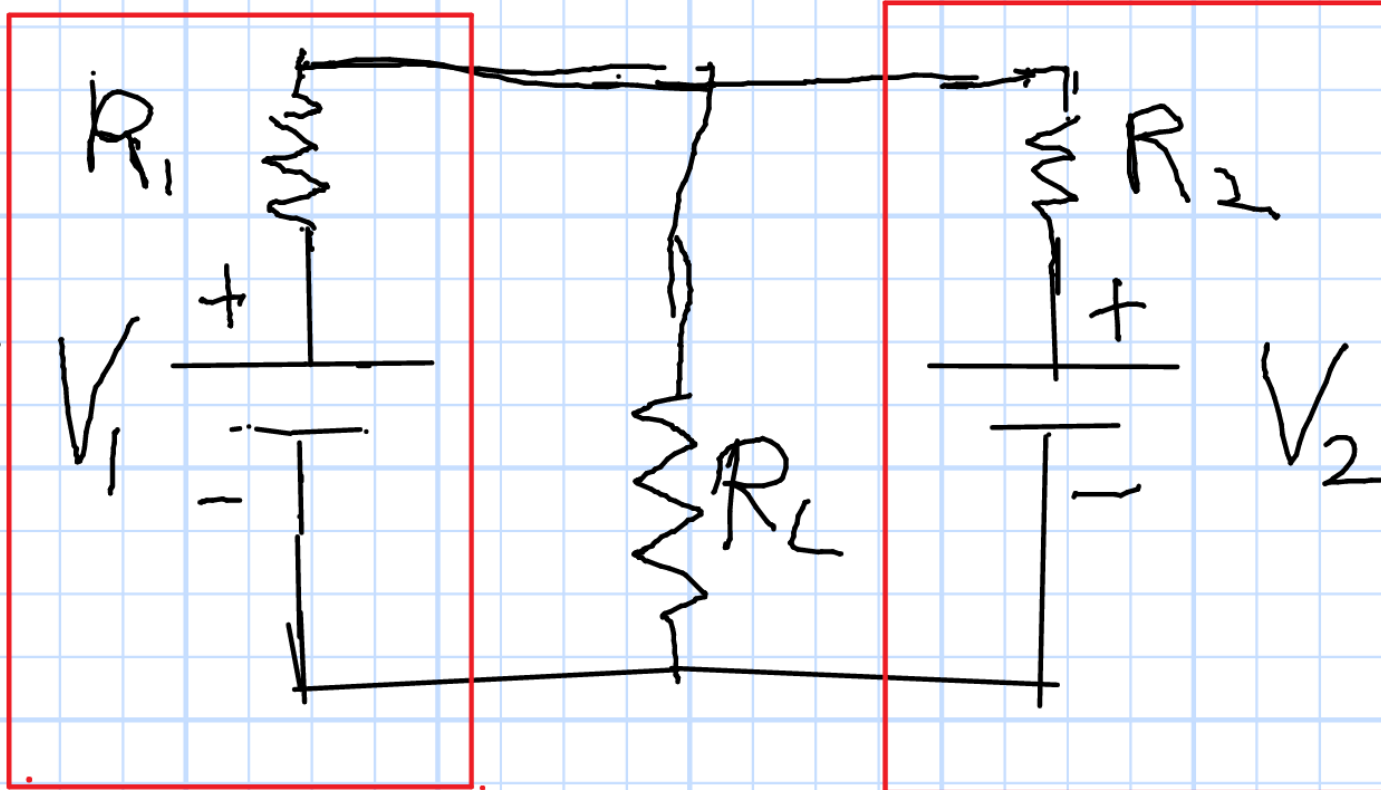


Parallel Batteries Solution
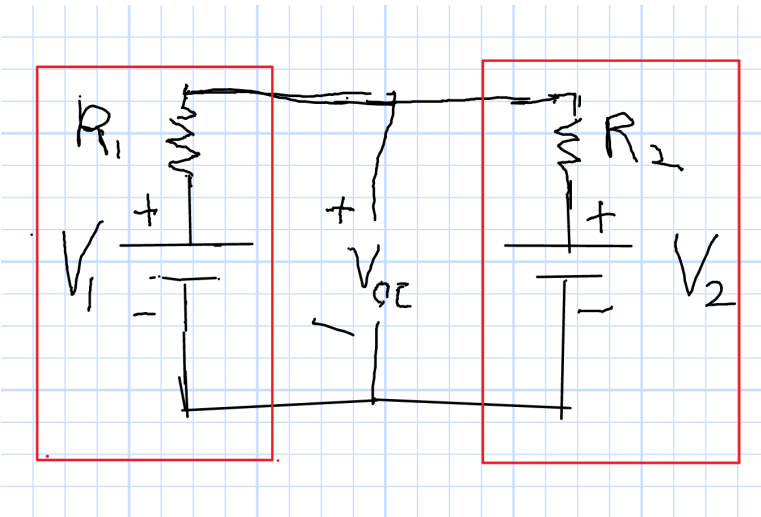
$$v_1 = 12\text{V}, R_1 = 1\Omega, v_2 = 11.9\text{V}, R_2 = 3\Omega$$



Voltage Divider
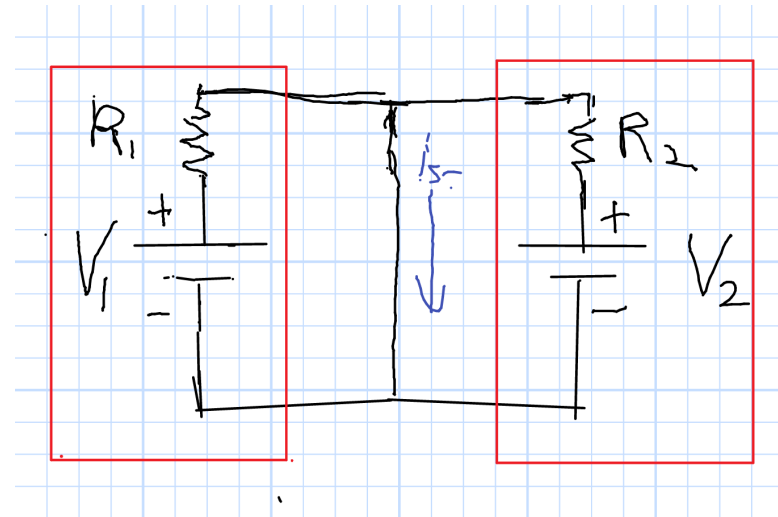
$$\begin{aligned} v_{oc} &= v_1 - (v_1 - v_2) \frac{R_1}{R_1 + R_2} \\ &= v_1 \frac{R_2}{R_1 + R_2} + v_2 \frac{R_1}{R_1 + R_2} \\ &= \frac{v_1 R_2 + v_2 R_1}{R_1 + R_2} \\ &= 11.97\text{V} \end{aligned}$$





KCL

$$i_{sc} = \frac{v_1}{R_1} + \frac{v_2}{R_2} = \frac{v_1 R_2 + v_2 R_1}{R_1 R_2}$$

Thévenin Resistor

$$R_T = \frac{v_{oc}}{i_{sc}} = 0.75\Omega$$

Norton Equivalent Circuit

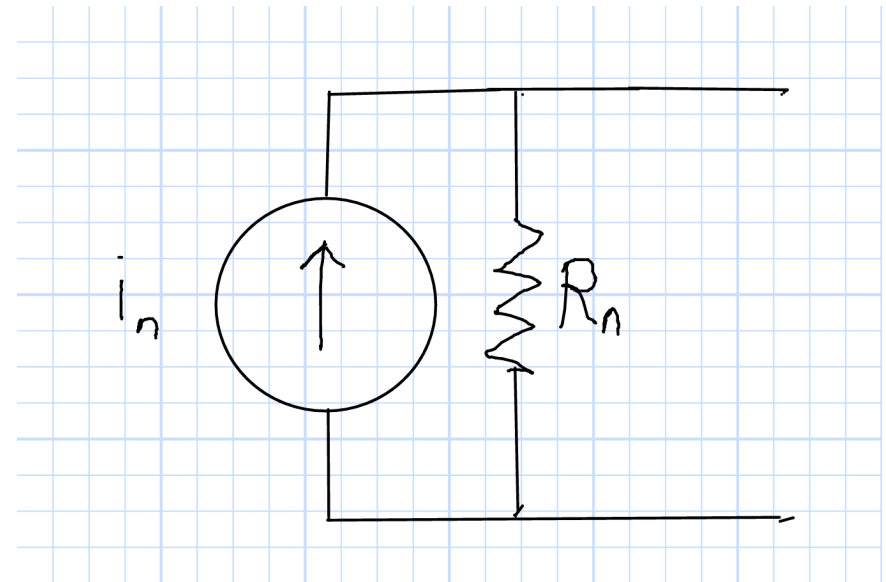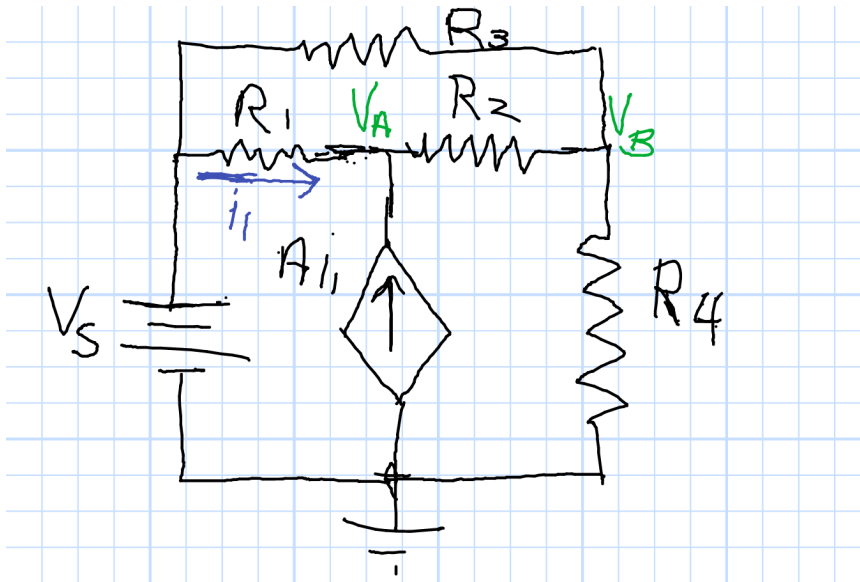

R_4 is the Load: Draw a circuit for everything else.

Linear Circuits: i vs. v is a straight line.

We need two points to determine the line.


$i = 0$: $V_{oc} = 16.28V$. $v = 0$: $i_{sc} = 11.4ma$

Load Resistor: $i = \frac{v}{R_4}$

Solution: Current Divider

Everything Else: $i = i_N - \frac{v}{R_N}$

Norton Example

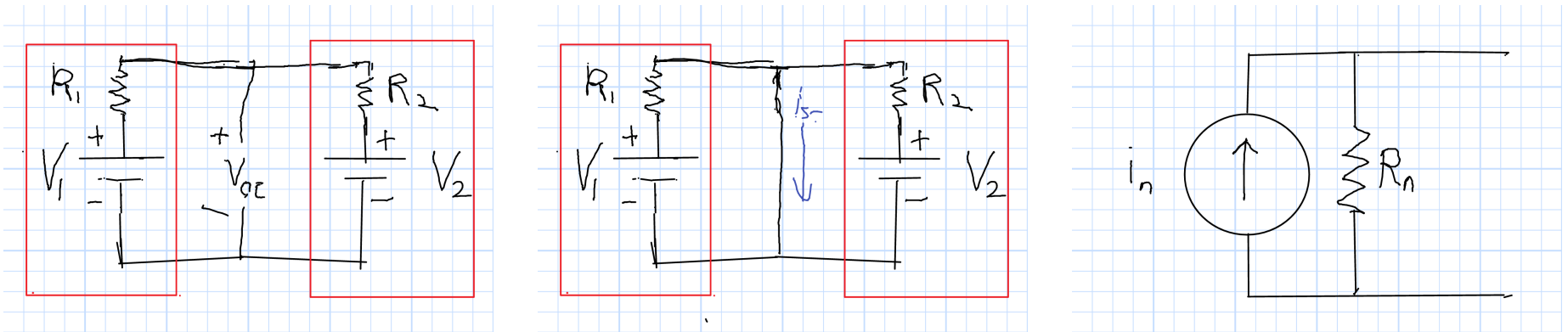

From Thévenin Equivalent


$$v_{oc} = 11.97\text{V} \quad R_T = 0.75\Omega$$

$$i_{sc} = \frac{v_1}{R_1} + \frac{v_2}{R_2} = \frac{v_1 R_2 + v_2 R_1}{R_1 R_2} = 15.96\text{A}$$


Norton Equivalent

$$i_N = i_{sc} = 15.96\text{A} \quad R_N = R_T = 0.75\Omega$$


Superposition Example (1)

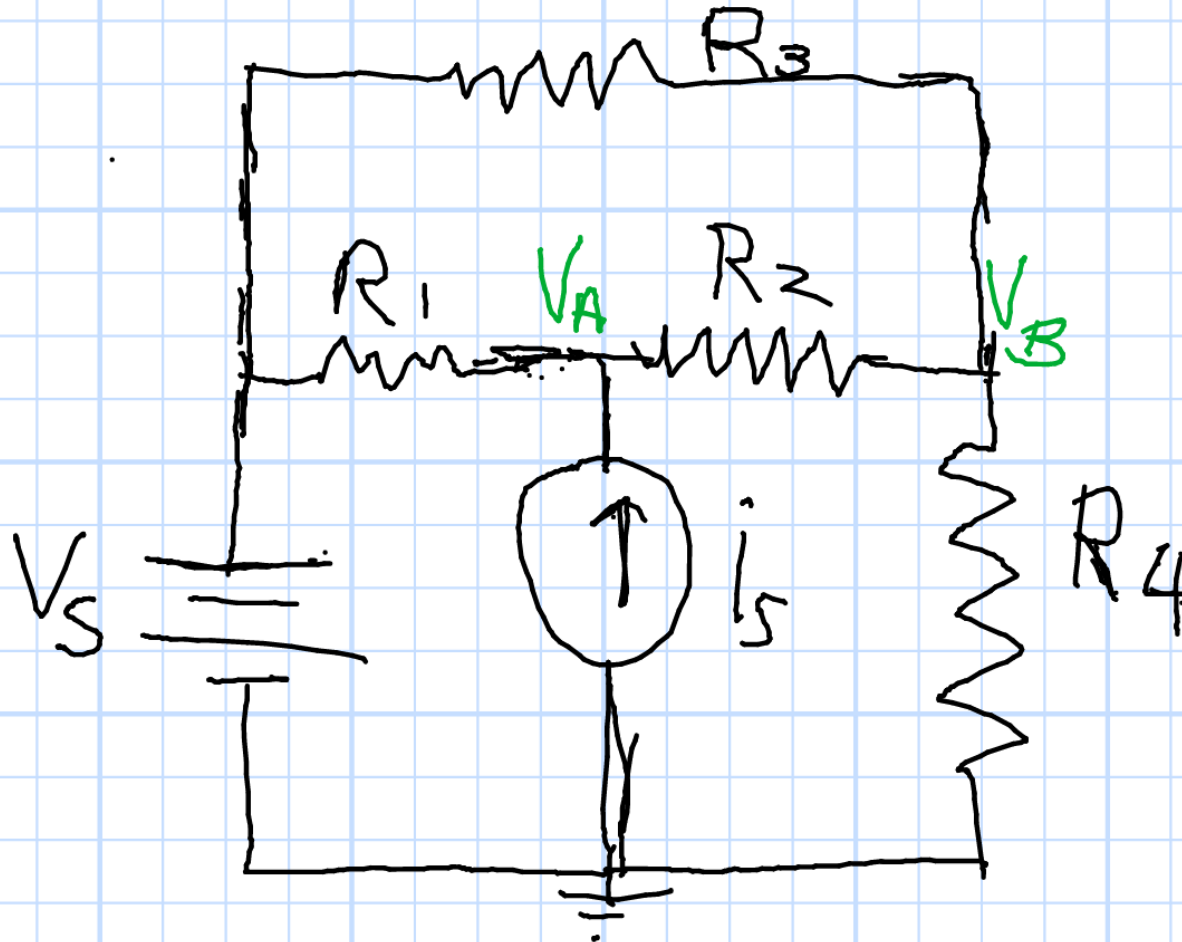


Superposition Example (2)

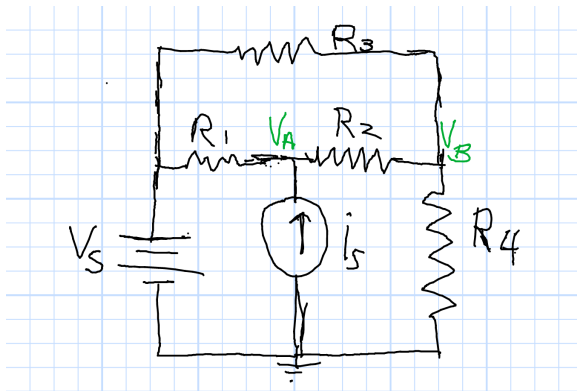

Original

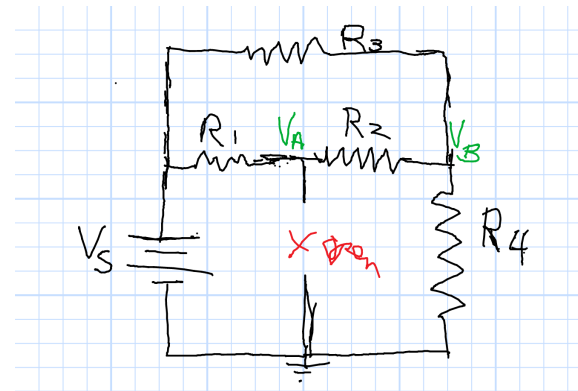


Zero Current Source
Open

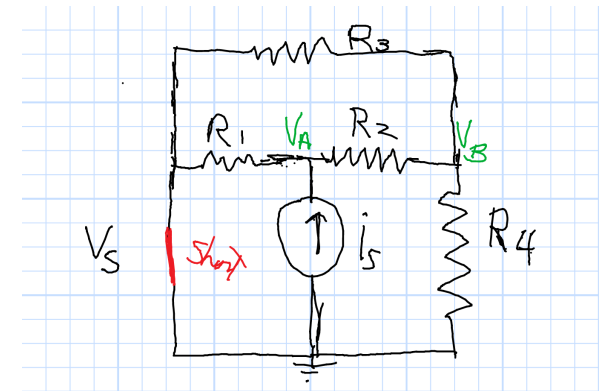

Zero Voltage Source
Short

- Zero the Sources One at a Time
- Solve the Circuit for All Unknowns in Each Case
- Sum the Results

Superposition Solution

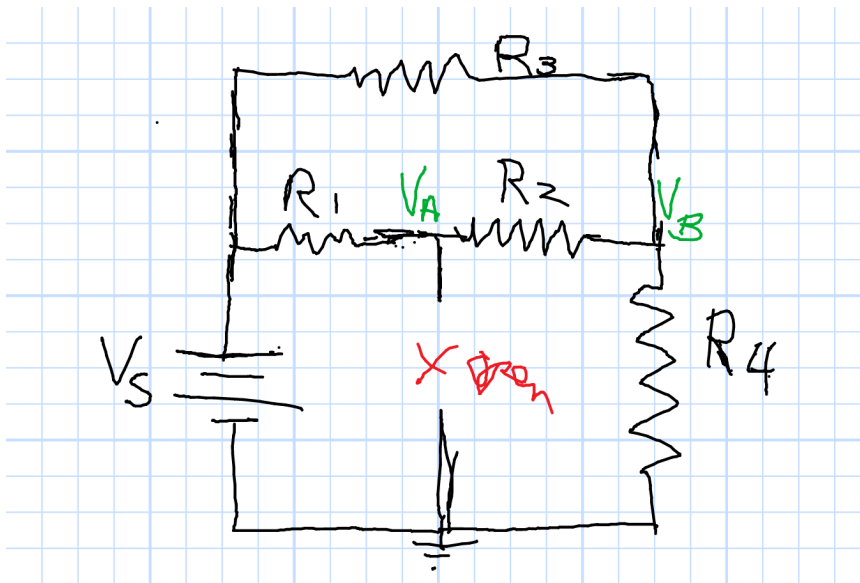


Series-Parallel Solution

$$i = v_s / [(R_1 + R_2) \parallel R_3] + R_4$$

$$v_B = iR_4$$

Voltage Divider
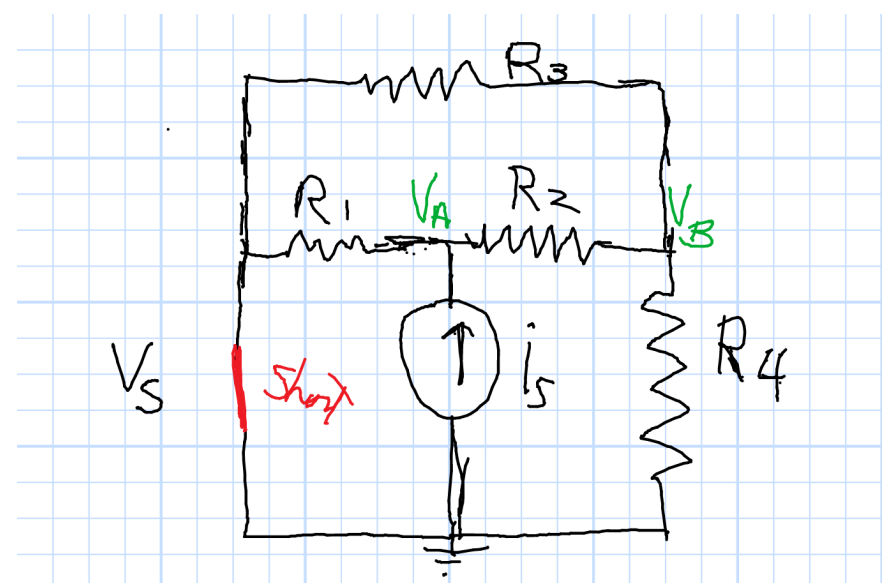
$$v_A = v_s + (v_B - v_s) \frac{R_1}{R_1 + R_2}$$



Series-Parallel Solution

$$v_A = i_s \{R_1 \parallel [R_2 + (R_3 \parallel R_4)]\}$$




Current Divider (i_2 to the right)

$$i_2 = i_s \frac{R_1}{R_1 + R_2 + (R_3 \parallel R_4)}$$

$$v_B = i_2 (R_3 \parallel R_4)$$

Conclusion
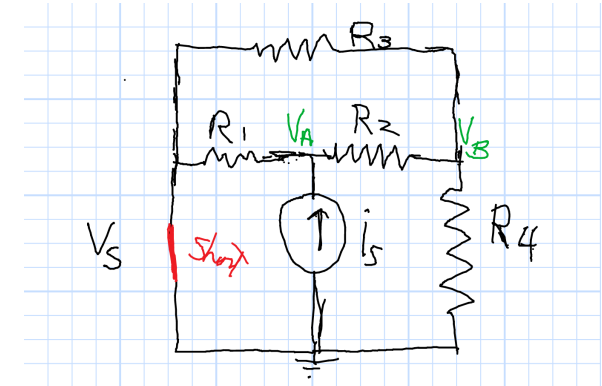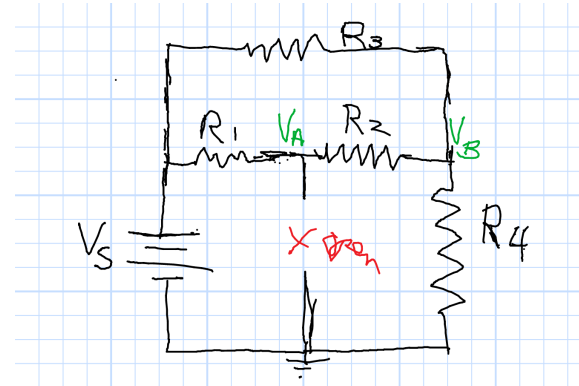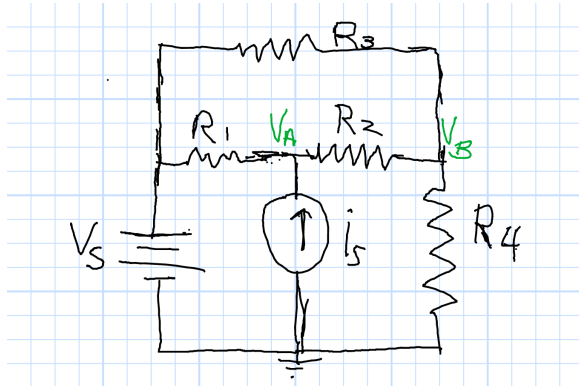
$$v_s = 12V, i_s = 6mA, R_1 = R_2 = 1k\Omega, R_3 = 5k\Omega, R_4 = 200\Omega$$



v_{total}

=

v_1

+

v_2

$$v_A = 6.74V$$

$$v_B = 1.47V$$

$$v_A = 3.26V$$

$$v_B = 0.53V$$



$$v_A = 10.0V$$

$$v_B = 2.0V$$

Same Result We Had Before.

Parallel Batteries: Superposition
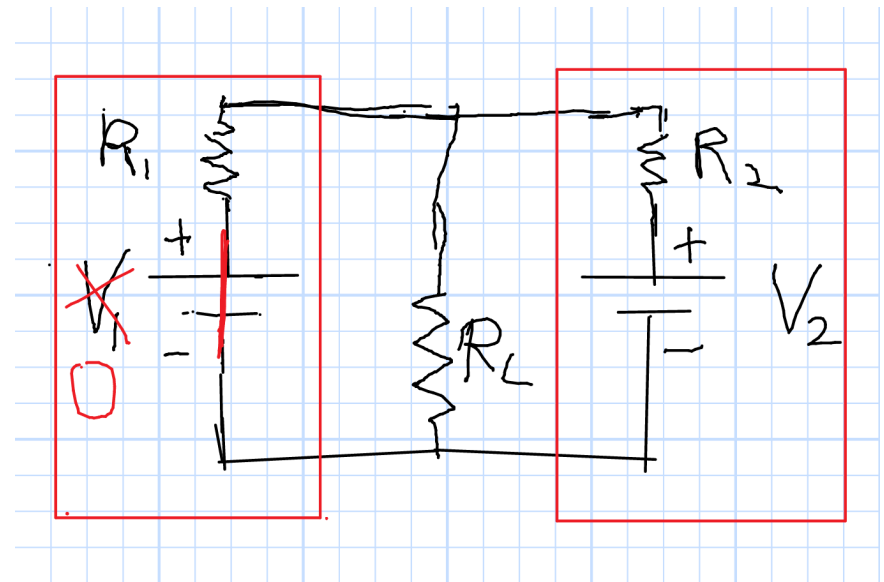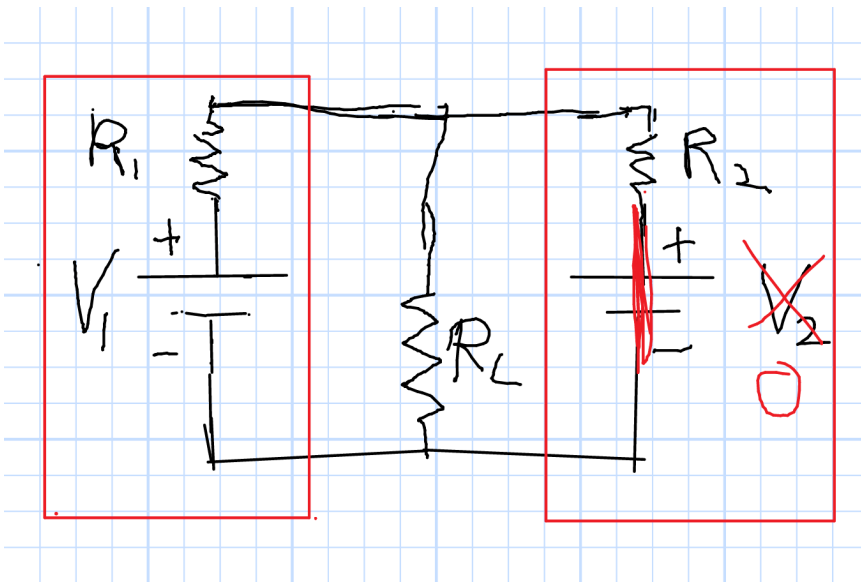
$$v_1 = 12\text{V}, R_1 = 1\Omega, v_2 = 11.9\text{V}, R_2 = 3\Omega$$




$$v_L = v_1 \frac{R_L \parallel R_2}{R_1 + (R_L \parallel R_2)} = 7.83\text{V}$$

$$v_L = v_2 \frac{R_L \parallel R_1}{R_2 + (R_L \parallel R_1)} = 2.59\text{V}$$


$$v_L = 7.83\text{V} + 2.59\text{V} = 10.4\text{V}$$

Balancing the Load

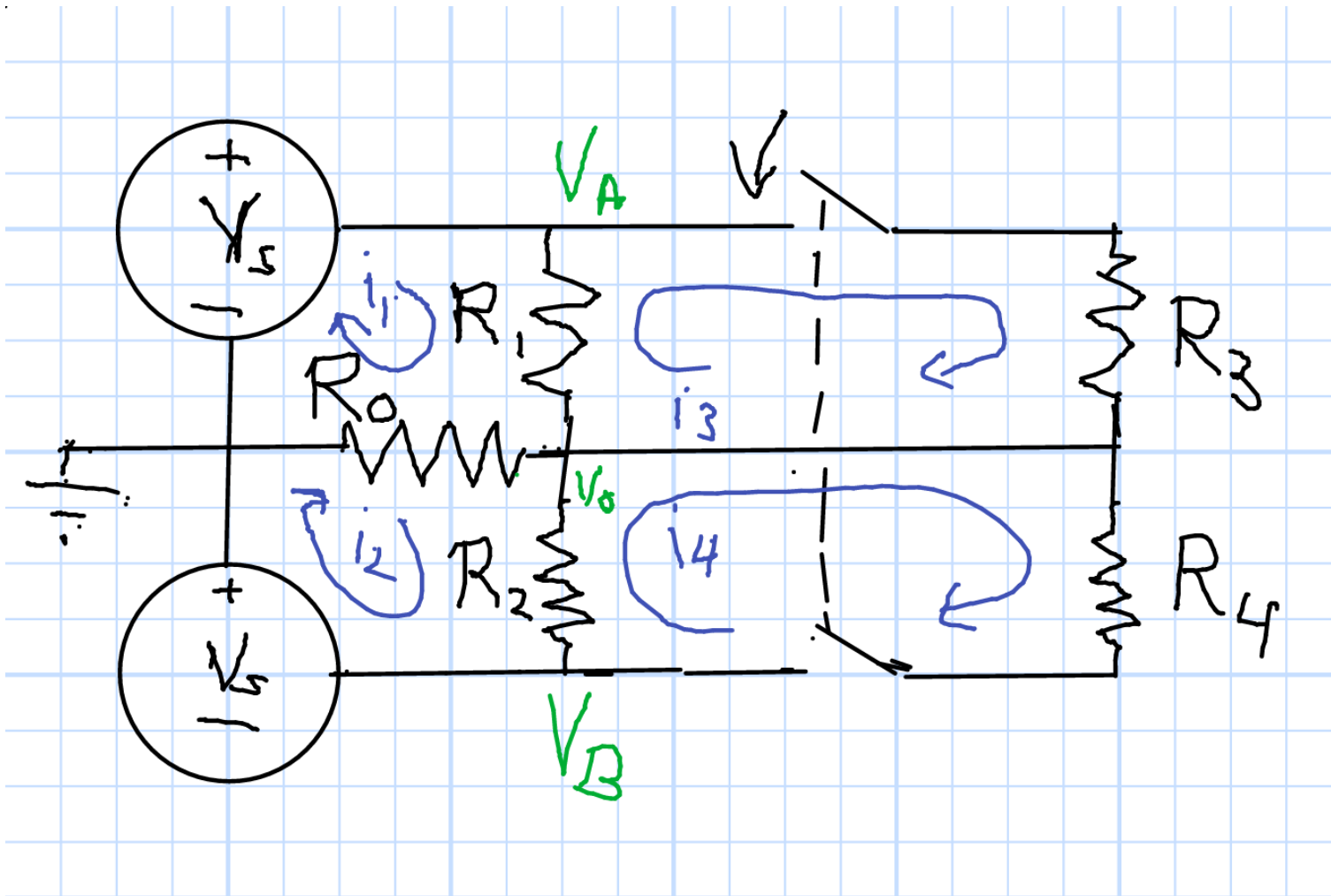

Source: $v_s = 120\text{V RMS}$. Bad Ground: $R_0 = 20\Omega$
 Lights: $R_1 = 14.4\Omega$, $R_2 = 144\Omega$. Stove: $R_3 = R_4 = 7.2\Omega$.

Stove Off

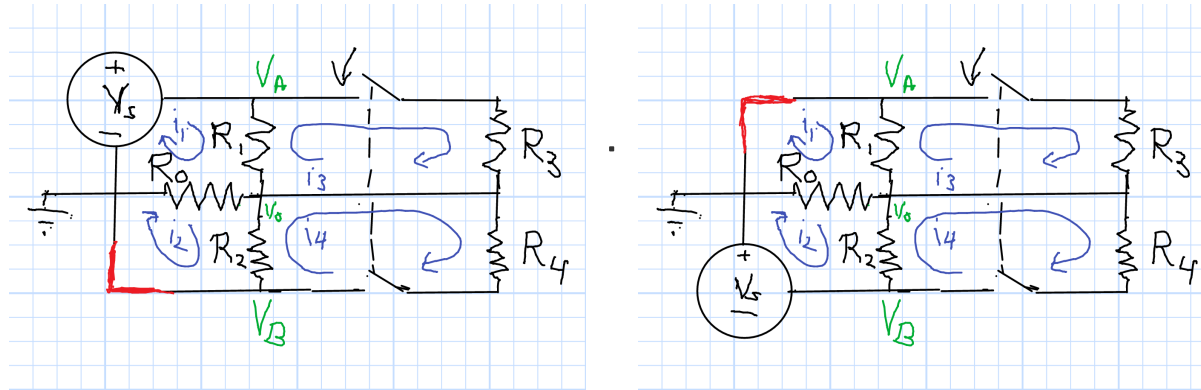

Voltage Divider with Top Source: Zero Bottom so $R_2 \parallel R_0$

$$v_1 = v_s \frac{R_1}{R_1 + (R_0 \parallel R_2)}$$

$$v_2 = v_s \frac{R_0 \parallel R_2}{R_1 + (R_0 \parallel R_2)}$$

Bottom Source: Zero Top so $R_1 \parallel R_0$

$$v_1 = -v_s \frac{R_1 \parallel R_0}{R_2 + (R_0 \parallel R_1)}$$

$$v_2 = -v_s \frac{R_2}{R_2 + (R_0 \parallel R_1)}$$

Total

$$v_1 = 60.7\text{V}$$

$$v_2 = 179.3\text{V}$$

$$\text{Check } v_1 + v_2 = 240\text{V}$$

$$v_A = 120\text{V}$$

$$v_B = -120\text{V}$$

$$v_0 = v_A - v_1 = 59.3\text{V}$$

Stove On: Balance Load

Same as Previous Page, but with $R_1 \parallel R_3$ and $R_2 \parallel R_4$

Top Source

$$v_1 = v_s \frac{R_1 \parallel R_3}{(R_1 \parallel R_3) + (R_0 \parallel R_2 \parallel R_4)}$$

$$v_2 = v_s \frac{R_0 \parallel R_2 \parallel R_4}{(R_1 \parallel R_3) + (R_0 \parallel R_2 \parallel R_4)}$$

Bottom Source

$$v_1 = -v_s \frac{R_1 \parallel R_3 \parallel R_0}{(R_2 \parallel R_4) + (R_0 \parallel R_1 \parallel R_3)}$$

$$v_2 = -v_s \frac{R_2 \parallel R_4}{(R_2 \parallel R_4) + (R_0 \parallel R_1 \parallel R_3)}$$

Total

$$v_1 = 101.4\text{V}$$

$$v_2 = 138.6\text{V}$$

$$\text{Check } v_1 + v_2 = 240\text{V}$$

$$v_A = 120\text{V}$$

$$v_B = -120\text{V}$$

$$v_0 = v_A - v_1 = 18.6\text{V}$$

Comparison

Stove Off

$$v_1 = 60.7\text{V} \quad v_2 = 179.3\text{V}$$

$$v_A = 120\text{V} \quad v_B = -120\text{V} \quad v_0 = v_A - v_1 = 59.3\text{V}$$

Lights Represented by R_1 Are Dim

Lights Represented by R_2 Are Too Bright

Stove On

$$v_1 = 101.4\text{V} \quad v_2 = 138.6\text{V}$$

$$v_A = 120\text{V} \quad v_B = -120\text{V} \quad v_0 = v_A - v_1 = 18.6\text{V}$$


Lights Represented by R_1 Become Brighter

Lights Represented by R_2 Become Dimmer

Better Balance

“Ground” Voltage, v_0 , Closer to Zero

Wheatstone Bridge

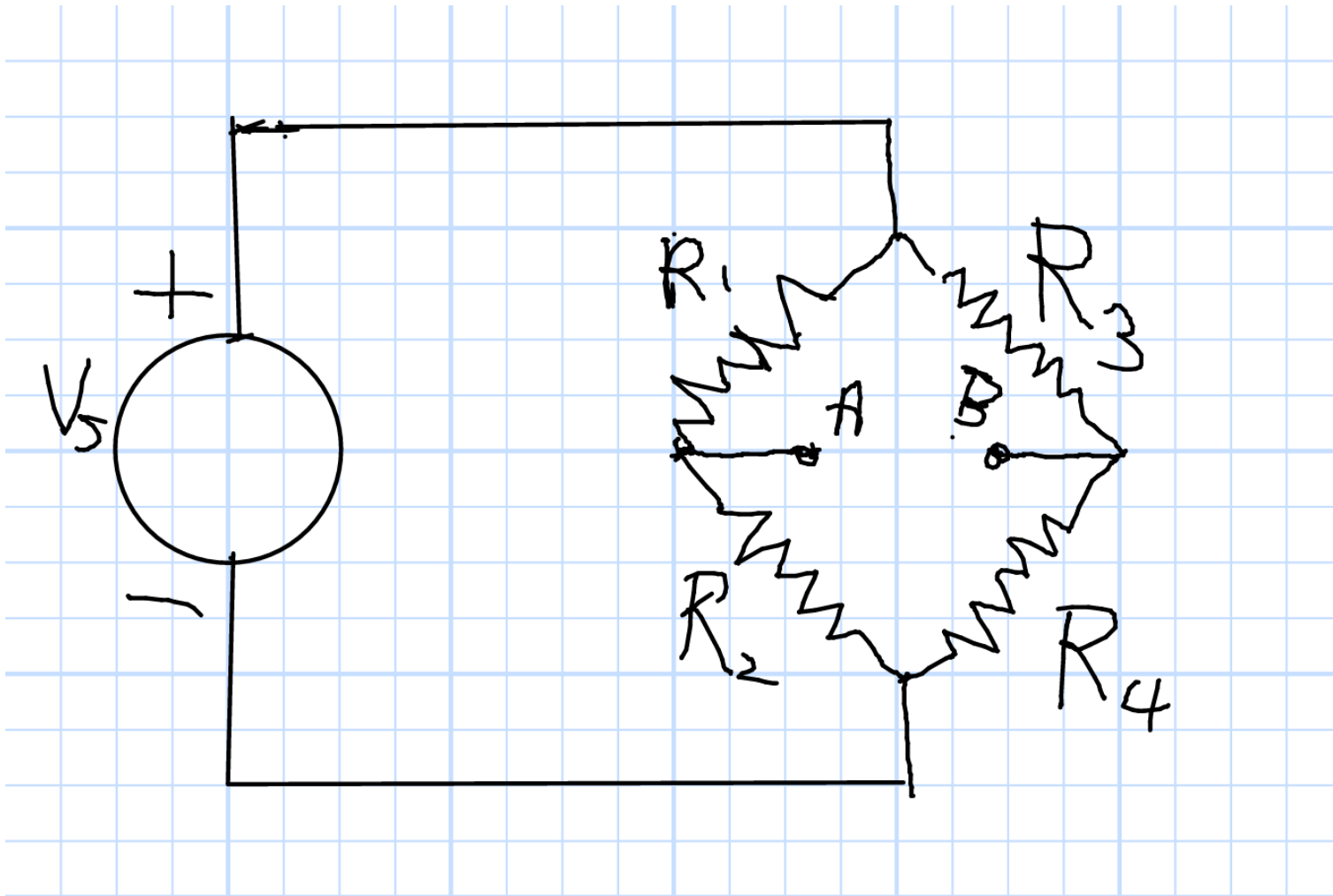

Balancing the Bridge


$$v_A = v_s \frac{R_2}{R_1 + R_2}$$

$$v_B = v_s \frac{R_3}{R_3 + R_4}$$

$$v_{BA} = v_s \left(\frac{R_2}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$$

Application:

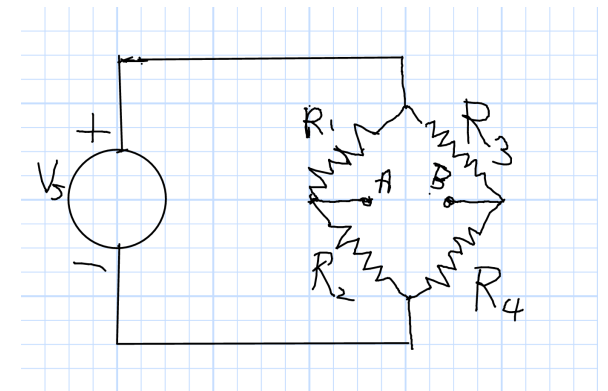- R_4 is Unknown
- R_2 is Variable and Calibrated
- R_1 and R_3 are Precision Resistors
- Adjust for $v_{BA} = 0$
- Solve for R_4



Strain Gauge


- R_4 is a Strain Gauge
- $R_4 = R_0 + \Delta R$
- $R_{1:3} = R_0$ Precision Resistors
- Calculate v_{AB}

$$v_{BA} = v_s \left(\frac{R_0}{2R_0} - \frac{R_0 + \Delta R}{2R_0 + \Delta R} \right)$$

$$v_{BA} = v_s \left(\frac{1}{2} - \frac{R_0 + \Delta R}{2R_0 + \Delta R} \right)$$

$$v_{BA} \approx v_s \left(\frac{1}{2} - \frac{R_0 + \Delta R}{2R_0} \right)$$
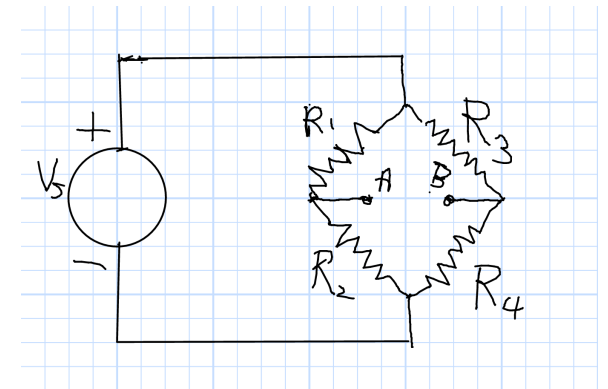
$$v_{BA} \approx -v_s \frac{\Delta R}{2R_0}$$




4 Balanced Strain Gauges

- $R_1 = R_4 = R_0 + \Delta R$ Are Strain Gauge
- $R_2 = R_3 = R_0 - \Delta R$ Measure Opposite Strain
- Calculate v_{AB}

$$v_{BA} = v_s \left(\frac{R_0 + \Delta R}{2R_0} - \frac{R_0 - \Delta R}{2R_0} \right)$$


$$v_{BA} = v_s \frac{2\Delta R}{2R_0}$$

$$v_{BA} = v_s \frac{\Delta R}{R_0}$$

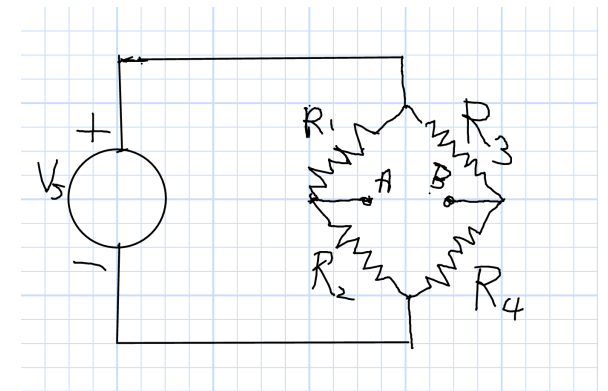

May Need a Variable to Get a Good Null

In-Class Exercise (1)

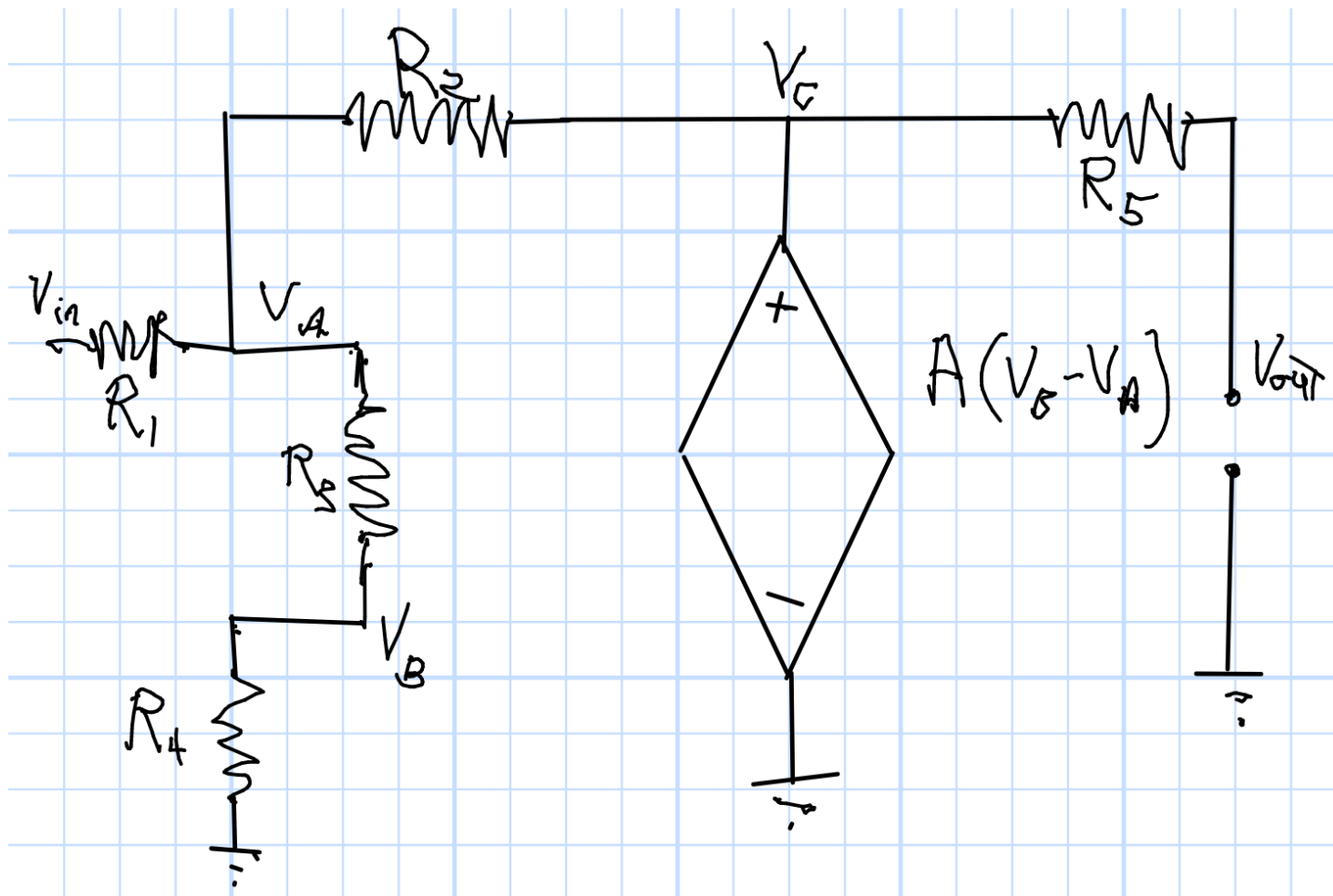

In-Class Exercise (2)

$$R_1 = 1\text{k}\Omega, R_2 = 10\text{k}\Omega, R_3 = 10\text{M}\Omega, R_4 = 10\Omega, R_5 = 50\Omega, \\ A = 10^5.$$

- Let $v_{in} = 1$
- Solve Symbolically for v_A, v_B, v_C with output open and shorted.
- Draw and label the Thévenin equivalent circuit for the output.
- What is the input resistance?
- Simplify the symbolic solution for the case where $R_3 \rightarrow \infty$ and $A \rightarrow \infty$.
- Next week we will see why this circuit is important.

Symbolic Solution

$$\frac{v_{in} - v_A}{R_1} + \frac{v_C - v_A}{R_2} + \frac{v_B - v_A}{R_3} = 0$$

$$v_A - v_B = v_A \frac{R_3}{R_3 + R_4} \quad v_C = A(v_B - v_A) = -v_A A \frac{R_3}{R_3 + R_4}$$

$$\frac{v_{in} - v_A}{R_1} + \frac{-v_A A \frac{R_3}{R_3 + R_4} - v_A}{R_2} + \frac{-v_A}{R_3 + R_4} = 0$$

$$\left[\frac{-1}{R_1} + \frac{-A \frac{R_3}{R_3 + R_4} - 1}{R_2} + \frac{-1}{R_3 + R_4} \right] v_A = \frac{-v_{in}}{R_1}$$

$$v_A = v_{in} \times \frac{1}{1 + R_1 \frac{A \frac{R_3}{R_3 + R_4} + 1}{R_2} + R_1 \frac{1}{R_3 + R_4}}$$

Numerical Solution

$$v_A = 9.9989 \times 10^{-5} \approx 0$$

$$v_B = v_A \frac{R_3}{R_3 + R_4} = 9.9989 \times 10^{-11} \approx 0$$

$$v_C = -v_A A \frac{R_3}{R_3 + R_4} = -9.9989$$

$$v_C \approx -\frac{R_2}{R_1} v_{in} \quad (\text{Interesting?})$$

$$R_{out} = R_5 = 50\Omega \quad \text{because} \quad i_{sc} = v_{oc}/R_5$$

$$R_{in} = R_1 = 1\text{k}\Omega \quad \text{because} \quad v_A \approx 0$$

Approximate Solution

- Let

$$R_3 \rightarrow \infty \quad A \rightarrow \infty$$

- Exact Equation

$$v_C = -A \frac{R_3}{R_3 + R_4} v_{in} \times \frac{1}{1 + R_1 \frac{A \frac{R_3}{R_3 + R_4} + 1}{R_2} + \frac{R_1}{R_3 + R_4}}$$

- Approximation


$$v_C \approx -A \frac{R_3}{R_3 + R_4} v_{in} \times \frac{1}{0 + R_1 \frac{A \frac{R_3}{R_3 + R_4} + 0}{R_2} + 0} = v_{in} \frac{-R_1}{R_2}$$

Using Thévenin Circuits

- Source: Thévenin Source, $v_s = 1\text{mV} \cos \omega t$, with $R_T = 150\Omega$
- First Amplifier: Voltage Gain of 10, 50Ω in and out, designed for 50Ω circuits.
- Second Amplifier: Voltage Gain of 20, 50Ω in and out, designed for 50Ω circuits.
- Measurement device: Your oscilloscope.
- What is the measured voltage?

Solution: First Amplifier

Gain of 10 with 50Ω resistances.

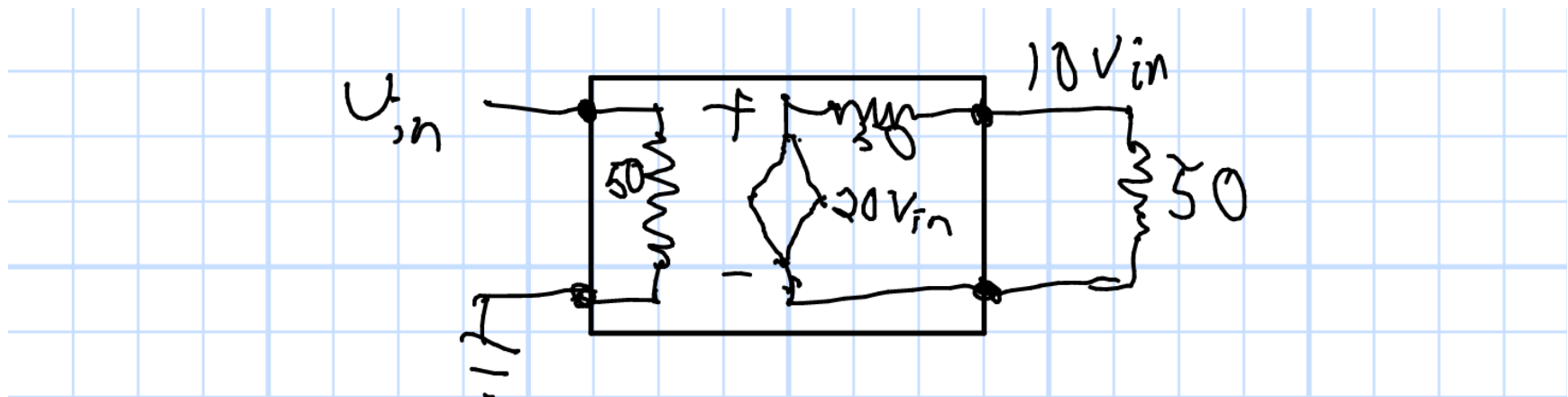

Solution

- First amplifier mismatch going in; $\frac{50}{200} = \frac{1}{4}$
- Amplifiers $10 * 20 = 200$
- But v_T of final amplifier is $40\times$ input to produce gain of 20 into 50Ω but scope is $1M\Omega$. Actual gain is 40 instead of 20.
- Total gain $\frac{1}{4} \times 10 \times 40 = 100$
- Output $0.1V \cos \omega t$
- $0.2V_{p-p}$

Solution (2)

