

Circuits and Signals: Biomedical Applications Week 8

Charles A. DiMarzio
EECE-2150
Northeastern University

Oct 2023

Week 8 Agenda: Circuits and Sine/Cosine Waves

- General Concepts of Sinusoidal Analysis
- C, L, Reactance and Impedance
- Eli the Ice Man
- Series and Parallel
- Voltage and Current Dividers
- One More Op–Amp Circuit
- Thévenin Equivalent
- Norton Equivalent

Solving Problems (1)

Real Quantity	Positive Freq.		Negative Freq.	Phasor
$A \cos \omega t$	$\frac{A}{2} e^{j\omega t}$	+	$\frac{A}{2} e^{-j\omega t}$	$A \angle 0$
$A \sin \omega t$	$\frac{-jA}{2} e^{j\omega t}$	+	$\frac{jA}{2} e^{-j\omega t}$	$A \angle 90$
$A \cos(\omega t + \phi)$	$\frac{Ae^{j\phi}}{2} e^{j\omega t}$	+	$\frac{Ae^{-j\phi}}{2} e^{-j\omega t}$	$A \angle \phi$
$A \cos \phi \cos \omega t - \dots$ $A \sin \phi \sin \omega t =$				
$a \cos \omega t + b \sin \omega t$	$\frac{a+jb}{2} e^{j\omega t}$	+	$\frac{a-jb}{2} e^{-j\omega t}$	$a + jb$

Problem Solution
Unknown = $x + jy$

$$2\text{Re} \left[\frac{x+jy}{2} e^{j\omega t} \right]$$

Pos. Freq. + C.C.

$$\text{Re} \left[(x + jy) e^{j\omega t} \right]$$

Solving Problems (2)

Known Sources: $i \cos(\omega t + \phi_s) = \frac{ie^{j\phi_s}}{2} e^{j\omega t} + \frac{ie^{-j\phi_s}}{2} e^{-j\omega t}$

Resistors

$$v = iR$$

$$V = IR$$

Capacitors

$$i = C \frac{dv}{dt}$$

$$I = j\omega CV$$

$$V = \frac{1}{j\omega C} I$$

Inductors

$$v = L \frac{di}{dt}$$

$$V = j\omega LI$$

Unknowns: $v \cos(\omega t + \phi_u) = \frac{ve^{j\phi_u}}{2} e^{j\omega t} + \frac{ve^{-j\phi_u}}{2} e^{-j\omega t}$

Easy? ...

Easy!

Capacitor (1)

- Capacitor Equation

$$i = C \frac{dv}{dt}$$

- Sinusoidal Voltage

$$v = V e^{j\omega t}$$

- Current

$$i = C \frac{dv}{dt} = C j\omega V e^{j\omega t}$$

$$i = I e^{j\omega t} = C j\omega V e^{j\omega t}$$

$$I = j\omega C V$$

- Impedance (New Concept)

$$Z = \frac{V}{I} = \frac{1}{j\omega C}$$

- Example $C = 1\mu\text{F}$

$$Z = \frac{1}{j\omega C} \quad \omega = 2\pi f$$

$$V = 10\text{V} \text{ at } f = 50\text{Hz}$$

- Current

$$I = \frac{V}{Z} \quad i = I e^{j\omega t}$$

```
>> C=1e-6;V=10;f=50;
```

```
>> Z=1/(1j*2*pi*f*C)
```

```
Z =
```

```
0.0000e+00 - 3.1831e+03i
```

```
>> I=V/Z
```

```
I =
```

```
0.0000 + 0.0031i
```


$$I = 3.1\text{mA} \angle 90^\circ$$

Capacitor (2); Current Leads

$$C = 1\mu\text{F} \quad V = 10\text{V at } f$$

f	Z	$ I $
50Hz	$-j3200\Omega$	3.1mA
500Hz	$-j320\Omega$	31mA
5kHz	$-j32\Omega$	310mA
50kHz	$-j3.2\Omega$	3.1A

Current Peak is Earlier

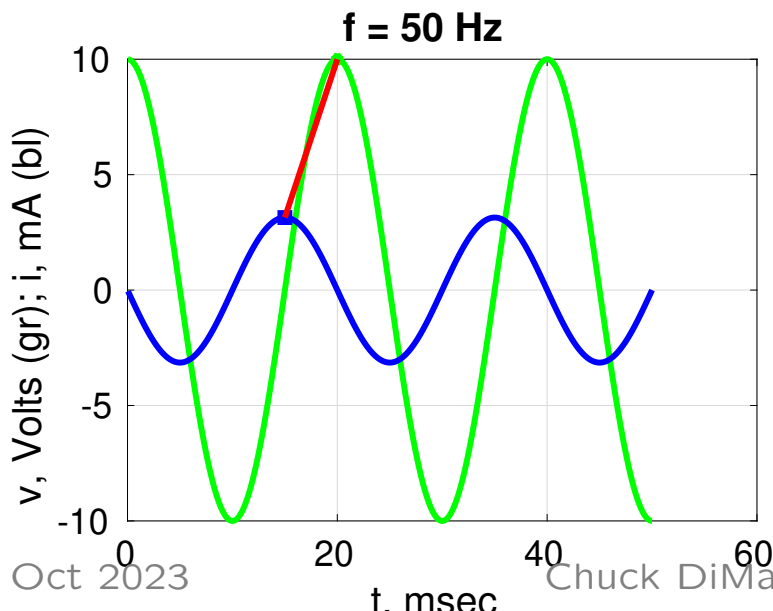

```
t=[0.001:0.001:1]*0.05;
C=1e-6;V=10;f=50;omega=2*pi*f;
Z=1/(1j*omega*C);I=V/Z;
vc=real(V*exp(1j*omega*t));
ic=real(I*exp(1j*omega*t));
fv=find(vc==max(vc),1);
fi=find(ic==max(ic),1);
figure;plot(t*1e3,vc,'g',...
    t*1e3,ic*1e3,'b',...
    t(fv)*1e3,vc(fv),'g*',...
    t(fi)*1e3,ic(fi)*1e3,'bs',...
    [t(fv),t(fi)]*1e3,...
    [vc(fv),ic(fi)*1e3],'r');
grid on;xlabel('t, msec');
ylabel('v, Volts (gr); i, mA (bl)');
title('f = 50 Hz');
```

Inductor: Current Lags

- Inductor Equation

$$v = L \frac{di}{dt}$$

- Sinusoidal Current

$$i = I e^{j\omega t}$$

- Voltage

$$v = L \frac{di}{dt} = L j\omega I e^{j\omega t}$$

$$v = V e^{j\omega t} = L j\omega I e^{j\omega t}$$

$$V = j\omega L I$$

- Impedance

$$Z = \frac{V}{I} = j\omega L$$

- Example $L = 5\text{H}$

$$Z = j\omega L$$

- Current

$$I = \frac{V}{Z} \quad i = I e^{j\omega t}$$

```
>> L=5;V=10;f=50;omega=2*pi*f;
```

```
>> Z=1j*omega*L
```

```
Z =
```

```
0.0000e+00 + 1.5708e+03i
```

```
>> I=V/Z
```


```
I =
```

```
0.0000 - 0.0064i
```


$$Z = 1600\Omega \angle 90^\circ$$

$$I = 6.4\text{mA} \angle -90^\circ$$


R, L, and C

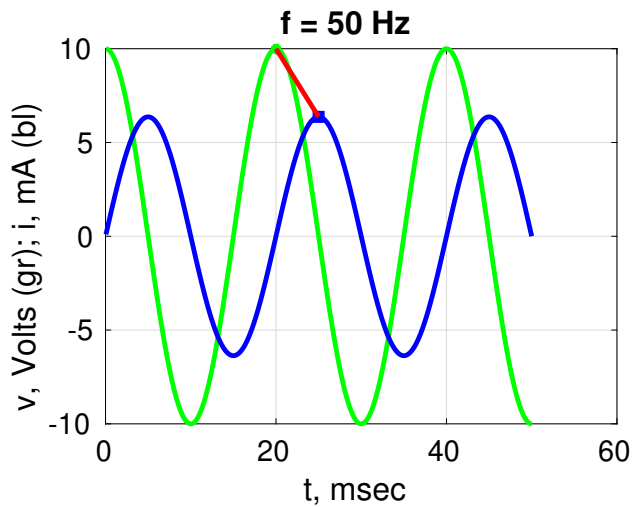

$L = 500\text{mH}$ (Peak v before i)

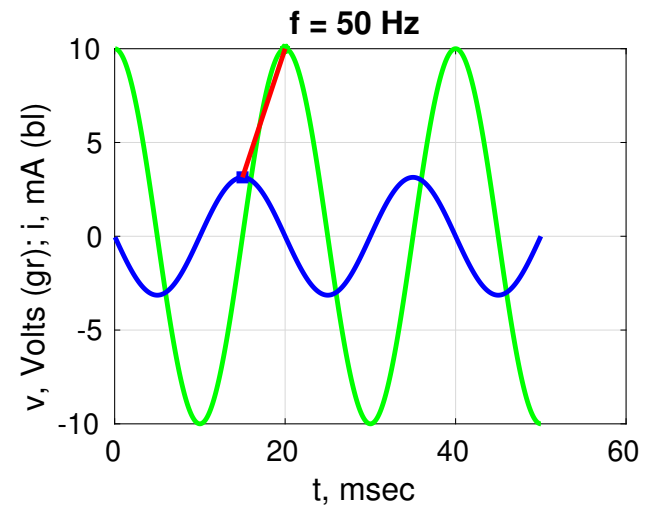

$C = 1\mu\text{F}$ (Peak v after i)

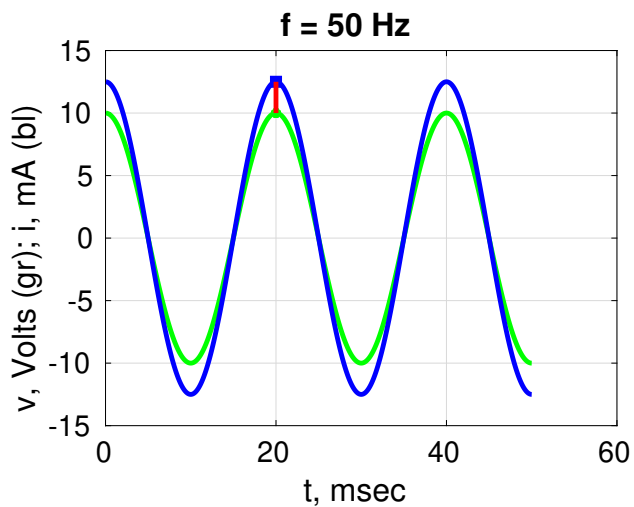

500Ω Resistor


Oct 2023

$$Z_C = 3200\Omega \angle -90^\circ$$


$$Z_L = 1600\Omega \angle +90^\circ$$

$$Z_R = 500\Omega \angle 0^\circ$$

Eli the Ice Man

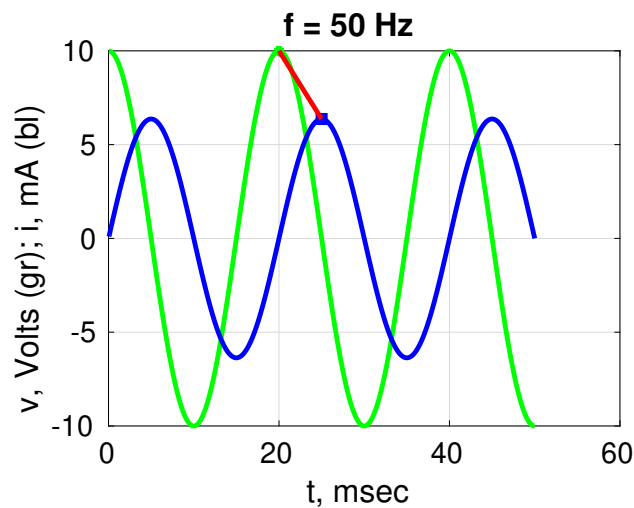

500mH Inductor

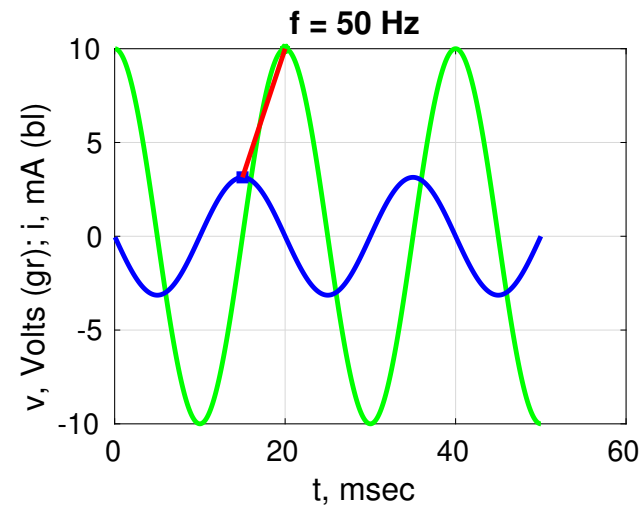

1 μ F Capacitor

- E for Electromotive Force (Voltage)
- Inductor (**E**LI)
E (Voltage) Leads I (Current):
Peak of Voltage (Green) Before Current (Blue)
- Capacitor (**I**CE)
I (Current) Leads E (Voltage):
Peak of Current (Blue) Before Voltage (Green)

Resistance, Reactance, Impedance

- Resistance, R

$$Z_R = R \quad \mathbf{V} = \mathbf{I}R$$

- Reactance, X **New Concept**

$$Z = jX \quad \mathbf{V} = \mathbf{I}jX$$

- Examples

$$Z_C = jX_C = \frac{1}{j\omega C} = \frac{-j}{\omega C} \quad Z_L = jX_L = j\omega L$$

- Impedance

$$Z = R + jX \quad \mathbf{V} = \mathbf{I}Z$$

AC Circuits & Steady–State Sinusoids

- Voltage Sources, Current Sources, Resistors

$$v = iR$$

- Voltage Sources, Current Sources, Impedances

$$\mathbf{V} = \mathbf{IZ} = \mathbf{IR} + j\mathbf{IX}$$

- Everything We Learned Before Works
 - Series and Parallel Circuits
 - Voltage and Current Dividers
 - Node and Mesh Analysis
 - Even Op–Amps

- Just Remember the Numbers are Complex

$$i = \operatorname{Re} \left(\mathbf{I}e^{j\omega t} \right) \quad v = \operatorname{Re} \left(\mathbf{V}e^{j\omega t} \right)$$

Series and Parallel

- Resistors in Series

$$R = R_1 + R_2$$

- Resistors in Parallel

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

- Inductors in Series

$$j\omega L = j\omega L_1 + j\omega L_2$$

- Inductors in Parallel

$$\frac{1}{j\omega L} = \frac{1}{j\omega L_1} + \frac{1}{j\omega L_2}$$

- Capacitors in Series

$$\frac{1}{j\omega C} = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}$$

- Capacitors in Parallel

$$\frac{1}{1/j\omega C} = \frac{1}{1/j\omega C_1} + \frac{1}{1/j\omega C_2}$$


- Impedances in Series

$$Z = Z_1 + Z_2$$

- Impedances in Parallel


$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

Voltage Divider

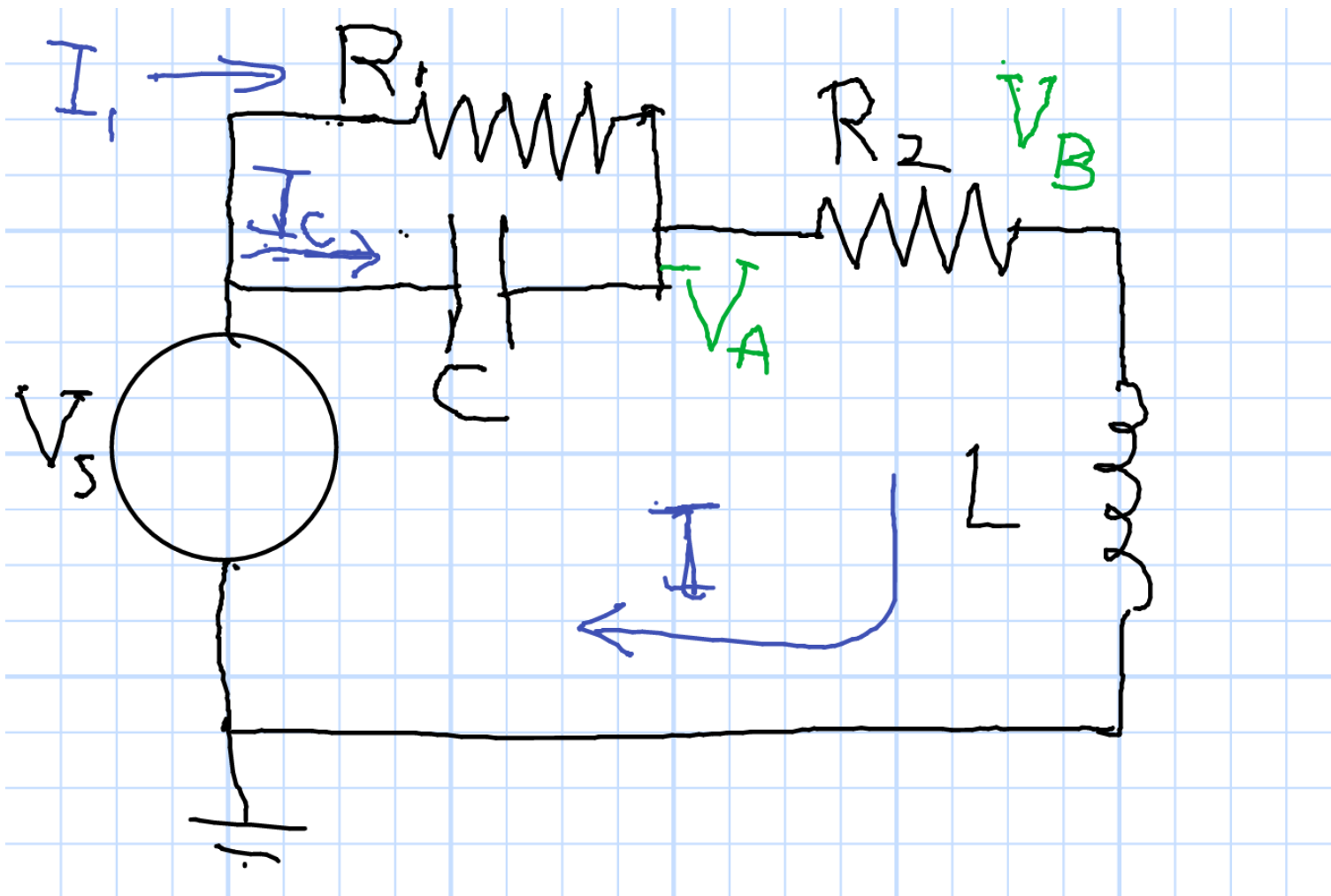

$$R_1 = 1\text{k}\Omega, R_2 = 2\text{k}\Omega, C = 470\text{pF}, L = 3\text{mH}, V_s = 20\text{V}, \\ f = 100\text{kHz}$$

Overall Impedance

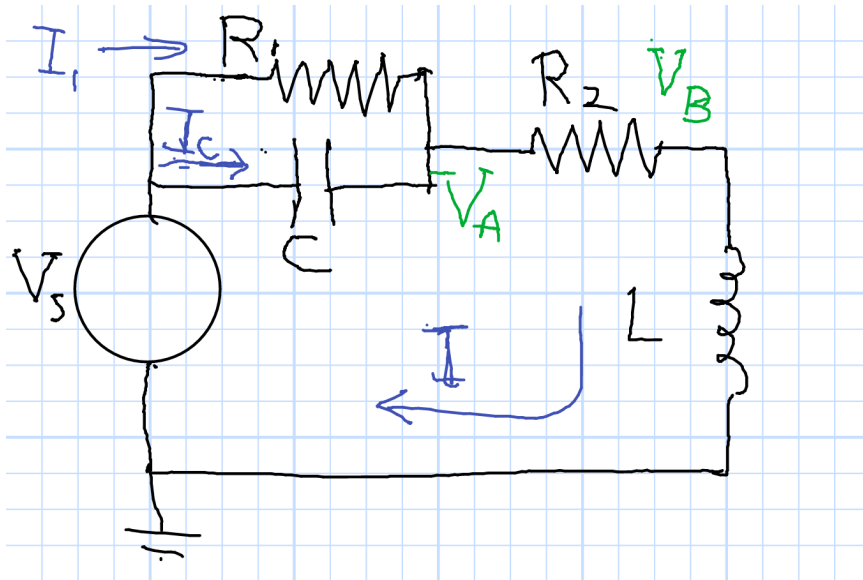

$$R_1 = 1\text{k}\Omega \quad R_2 = 2\text{k}\Omega$$

$$C = 470\text{pF} \quad L = 3\text{mH}$$

$$V_s = 20\text{V} \text{ at } f = 100\text{kHz}$$

$$Z = \left(R_1 \parallel \frac{1}{j\omega C} \right) + R_2 + j\omega L$$

$$V=20; \omega=2*\pi*1e5;$$

$$ZC=1/(1j*\omega*C);$$

$$ZL=1j*\omega*L;$$

$$Z1C=1/(1/R1+1/ZC);$$

$$\gg Z=Z1C+R2+ZL$$

$$Z =$$

$$2.9198e+03 + 1.6133e+03i$$

$$\gg \text{abs}(Z)$$

$$\text{ans} =$$

$$3.3359e+03$$


$$\gg \text{angle}(Z)*180/\pi$$

$$\text{ans} =$$

$$28.9229$$

$$Z = 3.3\text{k}\Omega \angle 29^\circ$$

Current

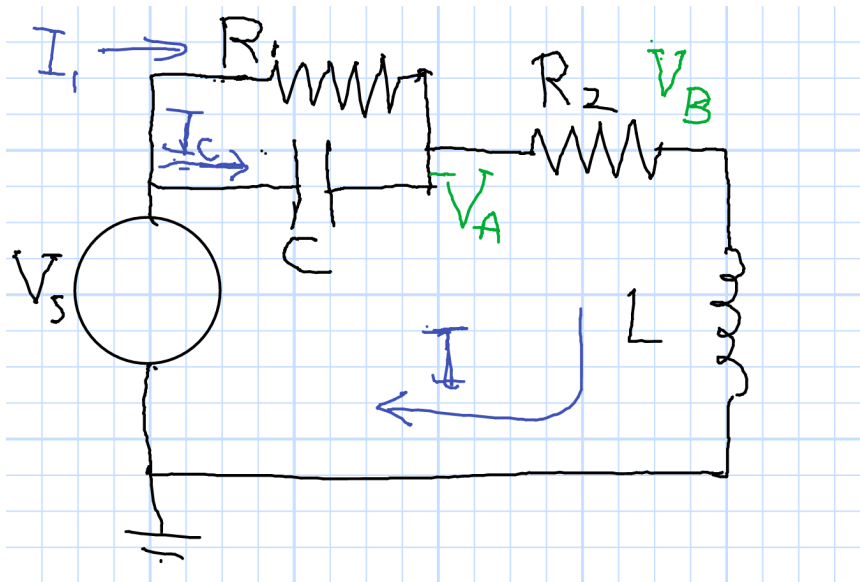

$$R_1 = 1\text{k}\Omega \quad R_2 = 2\text{k}\Omega$$

$$C = 470\text{pF} \quad L = 3\text{mH}$$

$$V_s = 20\text{V} \text{ at } f = 100\text{kHz}$$

$$I = \frac{V}{Z} = \frac{20\text{V}}{Z}$$

>> $I = V/Z$

$I =$

$$0.0052 - 0.0029i$$

>> $\text{abs}(I)$

ans =

$$0.0060$$


>> $\text{angle}(I) * 180 / \pi$

ans =

$$-28.9229$$

$$I = 6\text{mA} \angle -29^\circ$$

Current Divider

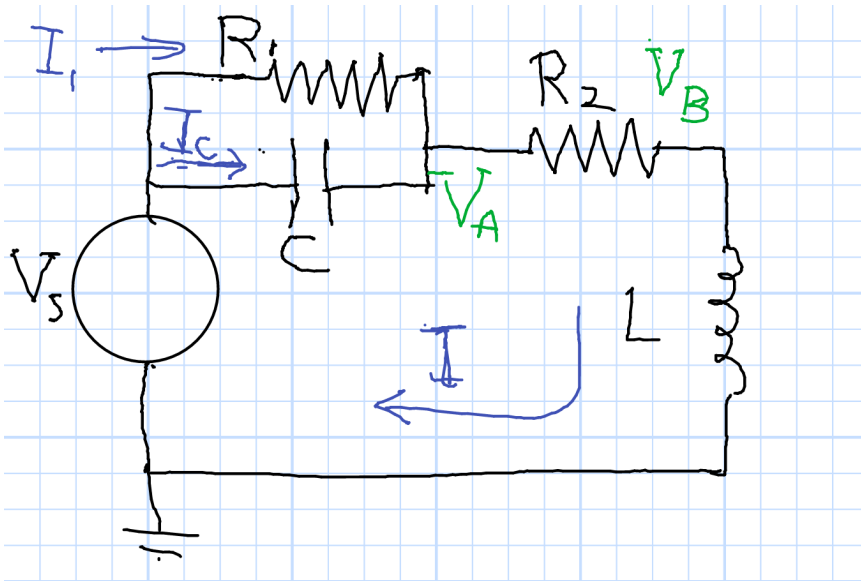

$$R_1 = 1\text{k}\Omega \quad R_2 = 2\text{k}\Omega$$

$$C = 470\text{pF} \quad L = 3\text{mH}$$

$$V_s = 20\text{V} \text{ at } f = 100\text{kHz}$$

$$I_C = I \frac{R_1}{R_1 + Z_C}$$

$$I_1 = I \frac{Z_C}{R_1 + Z_C}$$

$$I_C = I * R_1 / (R_1 + Z_C)$$

$$I_C =$$

$$0.0012 + 0.0012i$$

$$I_1 = I * Z_C / (R_1 + Z_C)$$

$$I_1 =$$

$$0.0040 - 0.0041i$$

$$I_{\text{check}} = I_C + I_1, \quad I$$


$$I_{\text{check}} =$$

$$0.0052 - 0.0029i$$

$$I =$$

$$0.0052 - 0.0029i$$

Voltage Divider

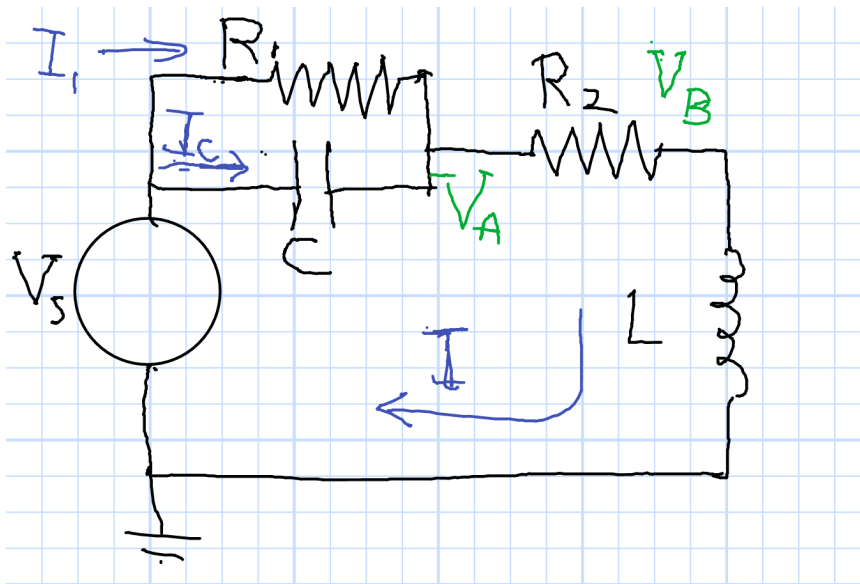

$$R_1 = 1\text{k}\Omega \quad R_2 = 2\text{k}\Omega$$

$$C = 470\text{pF} \quad L = 3\text{mH}$$

$$V_s = 20\text{V at } f = 100\text{kHz}$$

$$V_A = V \frac{R_2 + j\omega L}{Z}$$

$$\gg V_A = V * (R_2 + Z_L) / Z$$

$$V_A =$$

$$15.9609 + 4.0924i$$

$$\gg \text{abs}(V_A), \text{angle}(V_A) * 180 / \pi$$

$$\text{ans} =$$

$$16.4772$$

$$\text{ans} =$$

$$14.3809$$

$$V_A = 16.4\text{V} \angle 14^\circ$$


$$V_B = V \frac{j\omega L}{Z}$$

$$= 11.3\text{V} \angle 61^\circ$$

Questions


How much does all of this change in the current circuit if the input to the oscilloscope is $1\text{M}\Omega$?

How about if it is 50Ω ?

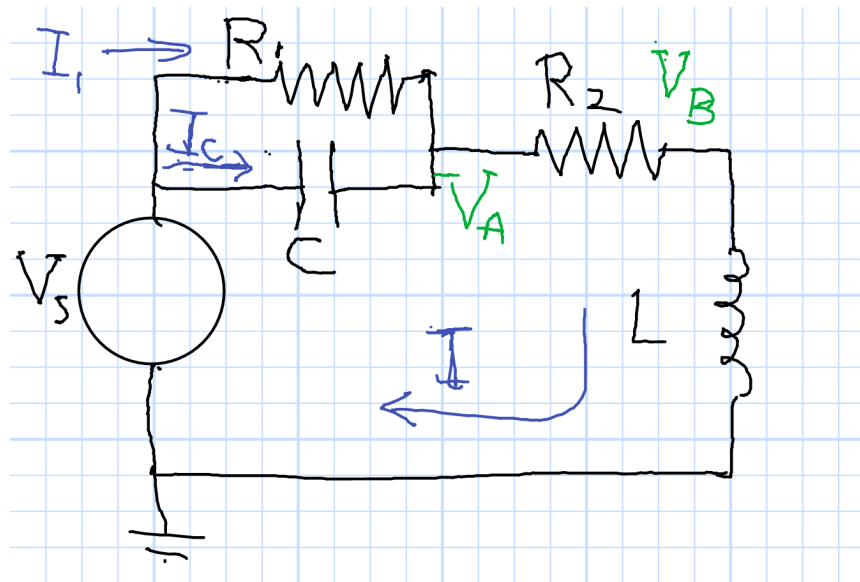


$$R_1 = 1\text{k}\Omega, R_2 = 2\text{k}\Omega, Z_C = -j3.4\text{k}\Omega, Z_L = j1.9\text{k}\Omega, \\ V = 20\text{V}, f = 100\text{kHz}$$

AC-Coupled Op-Amp Circuit

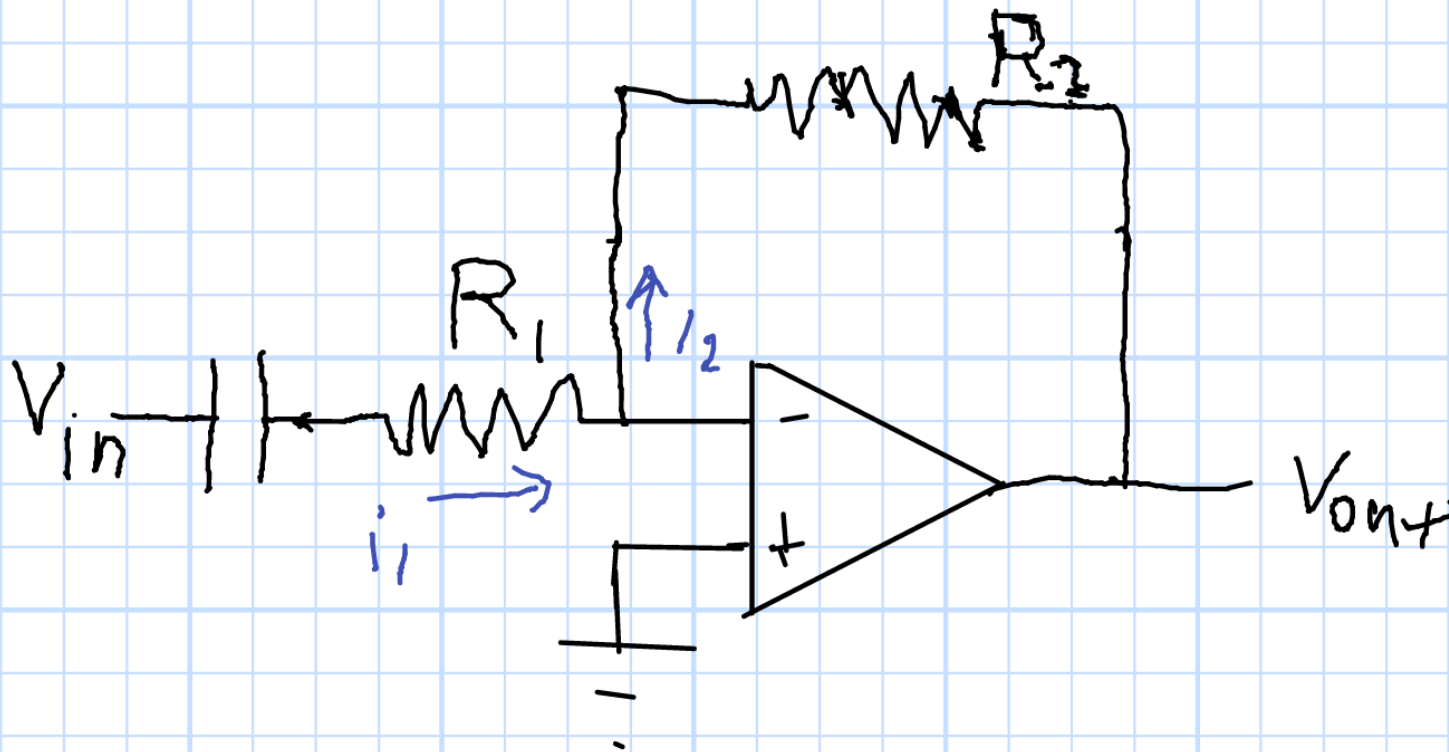

AC-Coupled Amplifier Solution

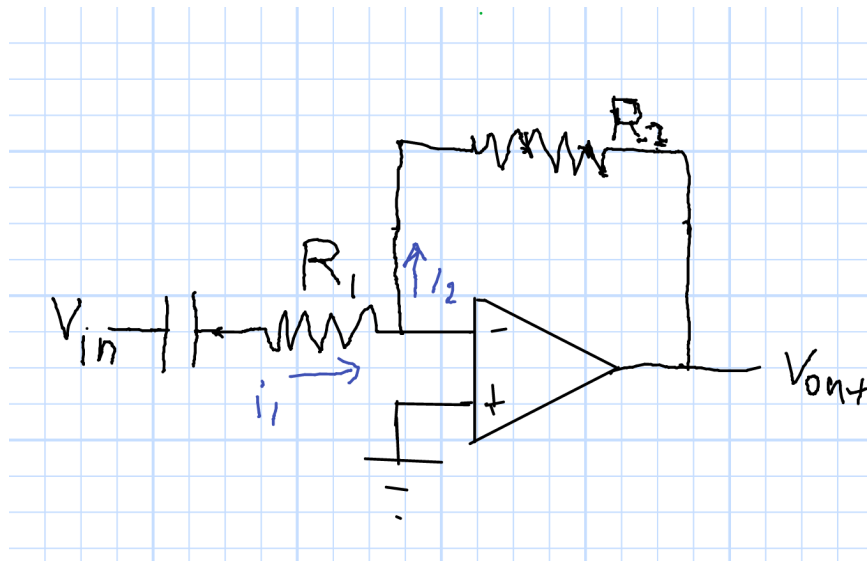


$$A_v = -\frac{R_2}{R_1 + \frac{1}{j\omega C}}$$

$$R_1 = 1\text{k}\Omega \quad R_2 = 10\text{k}\Omega$$

$$C = 1\mu\text{F} \quad X_C = \frac{1}{j2\pi fC}$$


$$X_C = -160\text{k}\Omega \text{ at } 1\text{Hz}$$
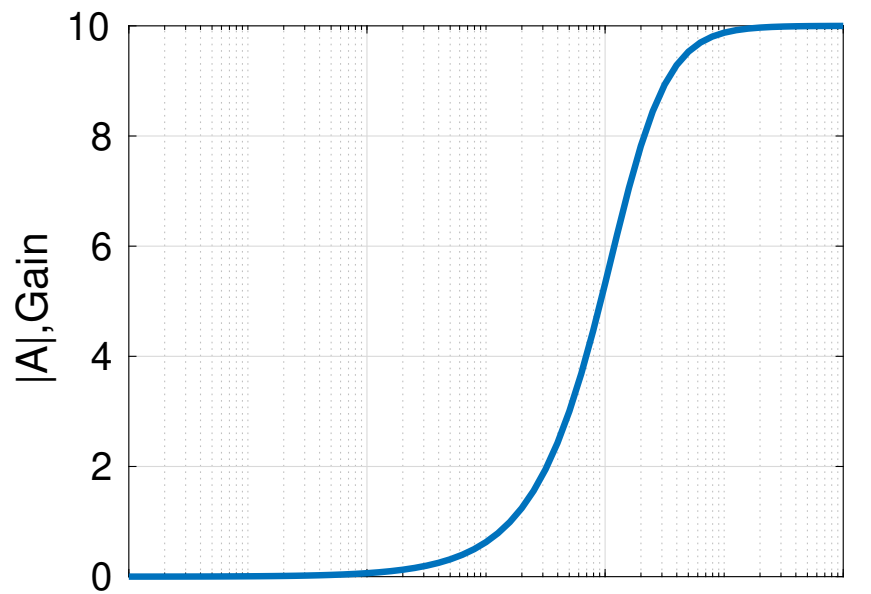
$$X_C = -160\Omega \text{ at } 1\text{kHz}$$



```
>> f=10.^[-2:0.1:4];
>> R1=1000;R2=10e3;C=1e-6;
>> A=-R2./(R1+1./(1j*2*pi*f*C));
>> figure;semilogx(f,abs(A));
grid on;
>> xlabel('f, Hz');
```

Cutoff

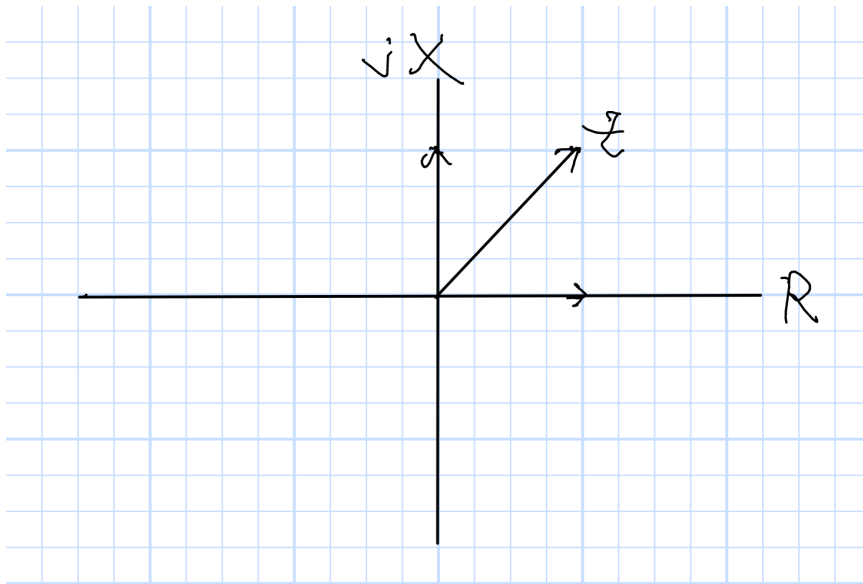

- Series Components

$$Z = R + jX$$

$$|X| = R \quad \rightarrow \quad |Z| = \sqrt{2}R$$

- Series Components

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{jX}$$

$$|X| = R \quad \rightarrow \quad |Z| = \sqrt{\frac{1}{2}}R$$

- Voltage Gain Changes by $\sqrt{2}$
- Power Gain Changes by 2