


Problem 3.60

$$I_L = V_L / R_L = 5 / 100 = 50 \text{ mA}$$

$$I_{\text{source}} = (8 - 5) / 20 = 150 \text{ mA}$$

$$I_{\text{QZener}} = I_{\text{source}} - I_L = 100 \text{ mA}$$

Small-signal equivalent circuit:

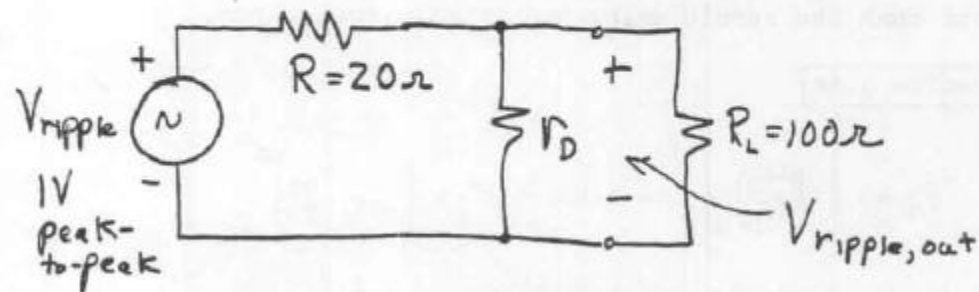

Let $R'_L = R_L || r_D$, then we can write:

$$V_{\text{ripple,out}} = 10 \text{ mV} = (1 \text{ V}) \times \frac{R'_L}{R'_L + R}$$

Solving we find $R'_L = 0.202 \Omega$. Thus we have $R'_L = 0.202 =$

$\frac{1}{1/r_D + 1/R_L}$ which yields $r_D = 0.202 \Omega$.

Problem 4.11

$$I_{B2} + I_{C1} + I_{B1} = 1 \text{ mA}$$

Because the transistors are identical and have equal V_{BE} , we conclude that $I_{B2} = I_{B1}$ and $I_{C2} = I_{C1}$. Furthermore $I_{C1} = \beta I_{B1}$.

$$I_{B1} + 100I_{B1} + I_{B1} = 1 \text{ mA} \quad \Rightarrow \quad I_{B1} = 9.804 \text{ } \mu\text{A}$$

$$I_{C1} = I_{C2} = \beta I_{B1} = 0.9804 \text{ mA}$$

$$I_{E1} = (\beta + 1)I_{B1} = 0.9902 \text{ mA}$$

Solving Equation 4.1 for V_{BE} we have

$$V_{BE} = V_T \ln(I_E/I_{ES} + 1)$$

$$= 0.026 \ln[(0.9902 \times 10^{-3})/10^{-14} + 1]$$

$$= 0.6583 \text{ V}$$

Problem 4.28

- (a) Active.
- (b) Cutoff.
- (c) Cutoff.
- (d) Saturation.

Problem 4.33

Circuit	β	Region	I_C (mA)	V_{CE} (V)
(a)	100	active	1.93	10.9
(a)	300	saturation	4.21	0.2
(b)	100	active	1.47	5.00
(b)	300	saturation	2.18	0.2
(c)	100	cutoff	0	15
(c)	300	cutoff	0	15
(d)	100	active	6.5	8.5
(d)	300	saturation	14.8	0.2