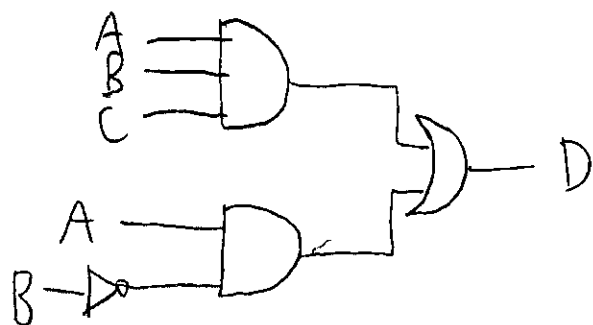


P.1

EECE 24/2- HW 10 Solutions


Problem 1

a) $D = ABC + AB$




A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

b) $E = AB + A\bar{B}C + \bar{C}D$

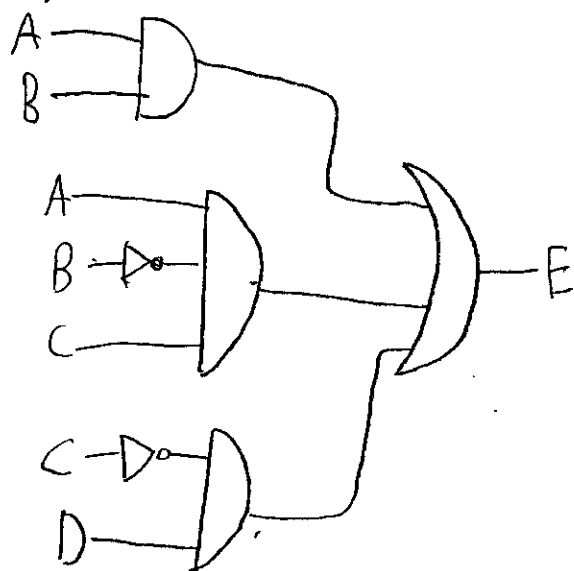

A	B	C	D	E
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

c) $Z = WX + \overline{(W+Y)}$

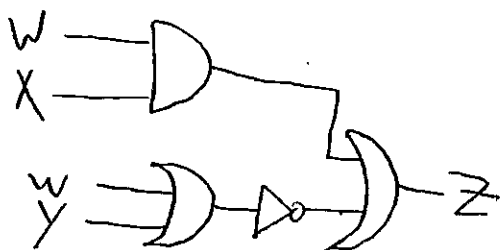

W	X	Y	Z
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Hint:

Find which inputs result in '1', then fill the rest with '0'

P.2

Problem 2

$$NM_H = V_{OH} - V_{IH} = 4.5V - 3V = 1.5V = NM_H$$

$$NM_L = V_{IL} - V_{OL} = 1.5V - 1V = 0.5V = NM_L$$

Problem 3

$$a) \quad t_{PHL} = \frac{C_L \cdot V_{DD}}{\left(\frac{W}{L}\right)_n \cdot K_{Pn} \cdot (V_{DD} - V_{tn})^2} = \frac{2 \times 10^{-12} \cdot 5}{\left(\frac{3}{1}\right) \cdot 50 \times 10^{-6} (5-1)^2}$$

$$t_{PHL} = 4.167 \times 10^{-9} s = 4.167 ns = t_{PHL}$$

$$t_{PLH} = \frac{C_L V_{DD}}{\left(\frac{W}{L}\right)_p \cdot K_{Pp} \cdot (V_{DD} - |V_{top}|)^2} = \frac{2 \times 10^{-12} \cdot 5}{\left(\frac{6}{1}\right) \cdot 25 \times 10^{-6} (5-1)^2}$$

$$t_{PLH} = 4.167 ns$$

b) same equations, but with $\left(\frac{W}{L}\right)_n = 3$ (no change)
 $\left(\frac{W}{L}\right)_p = 60$ (new)

$$t_{PHL} = 4.167 ns$$

$$t_{PLH} = 0.4167 ns$$

c) same equations with $\left(\frac{W}{L}\right)_n = 30$
 $\left(\frac{W}{L}\right)_p = 6$

$$t_{PHL} = 0.4167 ns$$


$$t_{PLH} = 4.167 ns$$

Problem 4

a) Conditions at the trip point:

$$V_I = \frac{V_{DD}}{2} = 0.6 \text{ V}$$

$$V_{GSN} = V_I - 0 = 0.6 \text{ V}$$

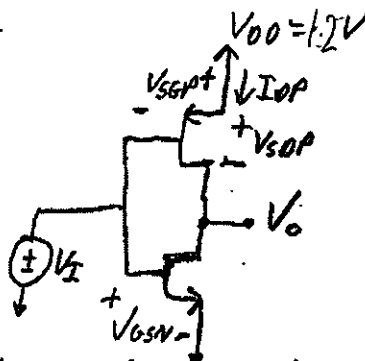

It is required that $V_o = \frac{V_{DD}}{2} = 0.6 \text{ V}$, which implies that $I_{op} = I_{on}$

$$V_{DSN} = V_o - 0 \text{ V} = 0.6 \text{ V} > V_{GSN} - V_{thn} = 0.6 \text{ V} - 0.3 \text{ V} = 0.3 \text{ V}$$

$V_{GSN} > V_{GSN} - V_{thn}$ & $V_{GSN} > V_{thn} \rightarrow$ The NMOS is in saturation at the trip point

$$V_{SGP} = 1.2 \text{ V} - V_I = 0.6 \text{ V} > |V_{thp}| = 0.4 \text{ V}$$

$$V_{SGP} - |V_{thp}| = 0.6 \text{ V} - (0.4 \text{ V}) = 0.2 \text{ V}$$

$V_{SDP} = 1.2 \text{ V} - V_o = 0.6 \text{ V} > V_{SGP} - |V_{thp}| \rightarrow$ The PMOS is in saturation

Equating the currents at the trip point, using the equations for the saturation region:

$$I_{op} = I_{on}$$

$$\left(\frac{W_p}{L_{min}}\right) \cdot \left(\frac{K_{Pp}}{2}\right) \cdot (V_{SGP} - |V_{thp}|)^2 \cdot (1 + \lambda \cdot V_{SDP})$$

$$= \left(\frac{W_n}{L_{min}}\right) \cdot \left(\frac{K_{Pn}}{2}\right) \cdot (V_{GSN} - V_{thn})^2 \cdot (1 + \lambda \cdot V_{DSN})$$

$$W_p \cdot (30 \times 10^{-6}) \cdot (0.6 - 0.4)^2 \cdot (1 + 0.05 \cdot 0.6)$$

$$= W_n \cdot (90 \times 10^{-6}) \cdot (0.6 - 0.3)^2 \cdot (1 + 0.05 \cdot 0.6)$$

$$\boxed{\frac{W_p}{W_n} = 6.75}$$


P.4 ... Probl. conti.:

b) The peak current occurs at the trip point
(Fig. 6.33 in the textbook)

$$I_{DN} = 0.05 \times 10^{-3} = \left(\frac{W_N}{L_{min}} \right) \cdot \left(\frac{K_P}{2} \right) \cdot (V_{GSN} - V_{TON})^2 \cdot (1 + \lambda \cdot V_{GSN})$$
$$0.05 \times 10^{-3} = \left(\frac{W_N}{0.12 \times 10^{-6}} \right) \cdot \left(\frac{90 \times 10^{-6}}{2} \right) \cdot (0.6 - 0.3)^2 \cdot (1 + 0.05 \cdot 0.6)$$

$$\hookrightarrow \boxed{W_N = 1.44 \mu m}$$

$$W_P = \left(\frac{W_P}{W_N} \right) \cdot W_N = 6.75 \cdot 1.44 \times 10^{-6} = \boxed{9.72 \mu m = W_P}$$

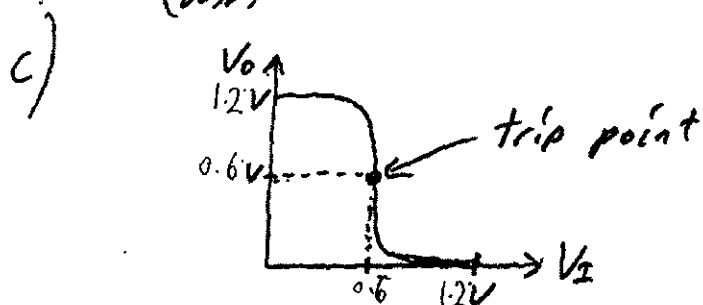

Problem 5

Using equation 6.7 in the textbook:

$$P_{dynamic} = f \cdot C_L \cdot (V_{DD})^2 = (100 \times 10^6 \text{ Hz}) \cdot (100 \times 10^{-15} \text{ F}) \cdot (3V)^2$$


$$\boxed{P_{dynamic} = 90 \mu W}$$

P.5

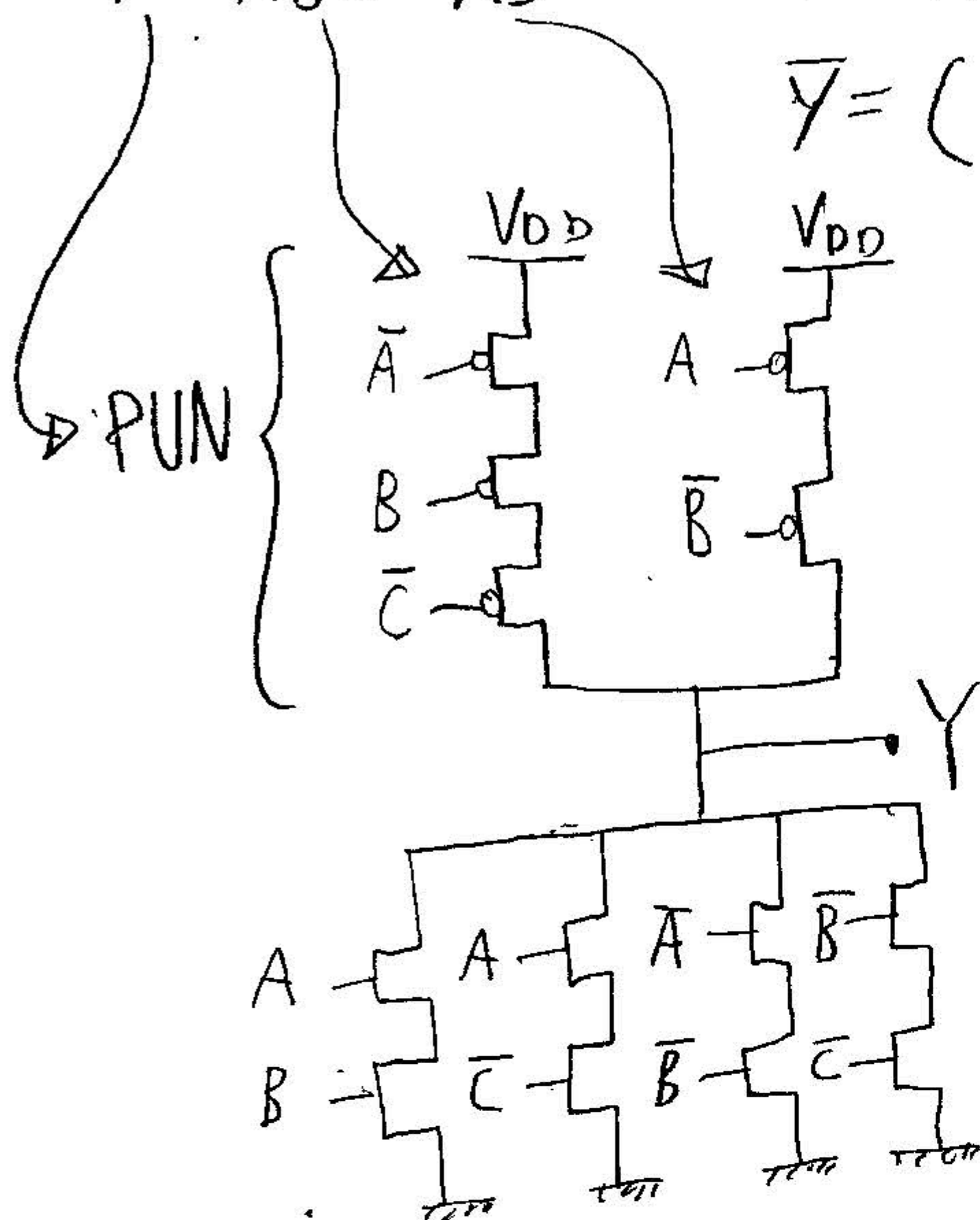Problem 6

$$Y = A\bar{B}C + \bar{A}B \rightarrow \bar{Y} = \overline{A\bar{B}C + \bar{A}B} = \overline{A\bar{B}C} \cdot \overline{\bar{A}B}$$


$$\bar{Y} = (\bar{A} + B + \bar{C}) \cdot (A + \bar{B}) = \underline{AB + A\bar{C} + \bar{B}\bar{A} + \bar{B}\bar{C}}$$



(other solutions are possible)

Problem 7

basic inverter

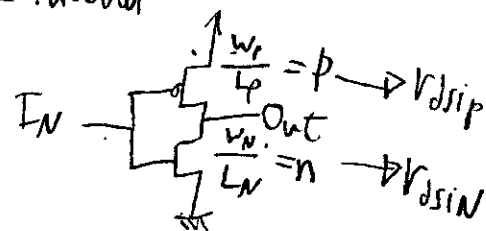

$$\left. \begin{array}{l} t_{PHL}, t_{PLH} \propto r_{ds} \\ r_{ds} \propto \frac{1}{(\frac{w}{L})} \end{array} \right\} t_{PHL}, t_{PLH} \propto \frac{1}{(\frac{w}{L})}$$

the series resistance of the transistors in the gate should sum up to an equivalent resistance $\leq r_{dsip}$ (or $\leq r_{dsin}$) for all input combinations, where the series resistances of the transistors between the output V_{out} and V_{DD} (or ground) are added when the transistors are "turned on".
 $\Downarrow$ $\frac{w}{L}$ ratios of the transistor in the gate

$$M_1 = \frac{w}{L} = p, \quad M_2, M_3, M_4: \frac{w}{L} = 2p$$

$\hookrightarrow$ when "on": Two transistors in series each having a resistance $r_{ds2,3,4} = \frac{r_{dsip}}{2}$

$$M_5, M_6: \frac{w}{L} = 2n$$

$$M_7, M_8: \frac{w}{L} = 4n$$

$\hookrightarrow$ worst case M_5 and (M_6 or (M_7 and M_8)) are "on":

$$\text{if } M_5, M_6 \text{ on} \rightarrow t = \frac{r_{dsin}}{2} + \frac{r_{dsin}}{2} = r_{dsin}$$

$$\text{if } M_5, M_7, M_8 \text{ on} \rightarrow t = \frac{r_{dsin}}{2} + \frac{r_{dsin}}{4} + \frac{r_{dsin}}{4} = r_{dsin}$$

$\hookrightarrow$ ALL are ON:

$$\frac{r_{dsin}}{2} + \left(\frac{r_{dsin}}{2} \parallel \left(\frac{r_{dsin}}{4} + \frac{r_{dsin}}{4} \right) \right) = \frac{3}{4} r_{dsin} < r_{dsin}$$

$$M_5 + (M_6 \parallel (M_7 + M_8))$$