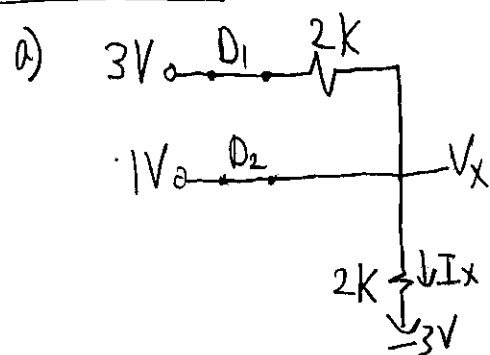


① EECE 2412: HW3 Solutions

Problem 1:




$$I_x = \frac{1V - (-3V)}{2K} = \boxed{2mA = I_x}$$

$$\boxed{V_x = 1V}$$

checks:

$$I_{D1} = \frac{3V - 1V}{2K} = 1mA > 0 \rightarrow D1 \text{ is forward-biased (FB)}$$
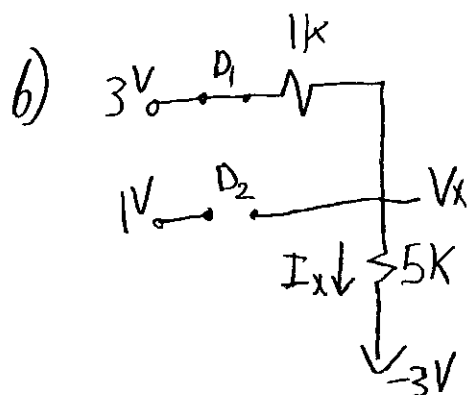
$$I_{D2} = I_x - I_{D1} = 1mA \rightarrow D2 \text{ is forward-biased (FB)}$$




$$I_x = \frac{3V - (-3V)}{5K + 1K} = \boxed{1mA = I_x}$$

$$V_x = 3V - I_x * 1K = \boxed{2V = V_x}$$

checks:

$$V_{D2} = 1V - 2V = -1V < 0 \rightarrow D2 \text{ is reverse-Biased (RB)}$$
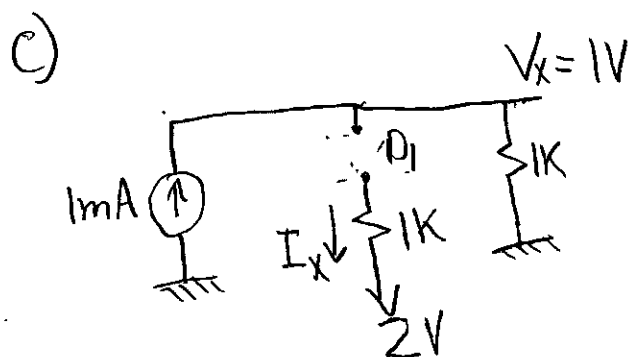
$$I_{D1} = I_x = 1mA > 0 \rightarrow D1 \text{ is Forward-Biased (FB)}$$



$$V_x = 1mA \times 1K\Omega = \boxed{1V = V_x}$$

$$\boxed{I_x = 0A}$$


checks:

$$V_{D1} = 1V - 2V = -1V < 0$$

$\rightarrow D1 \text{ is reverse-biased (RB)}$

②

Problem 2:

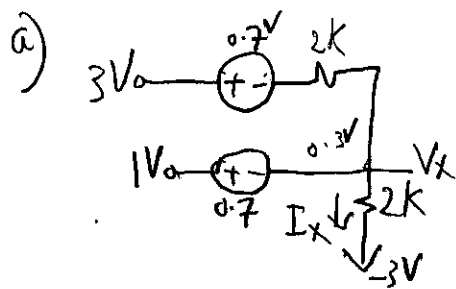

$$V_x = 1 - 0.7 = 0.3V = V_x$$

$$I_x = \frac{0.3V - (-3V)}{2K} = 1.65mA = I_x$$

Checks:


$$I_{D1} = \frac{3V - 0.7V - 0.3V}{2K} = 1mA > 0$$

→ D_1 is Forward-biased

(FB)

$$I_{D2} = I_x - I_{D1} = 0.65mA > 0$$

→ D_2 is Forward-biased
(FB)

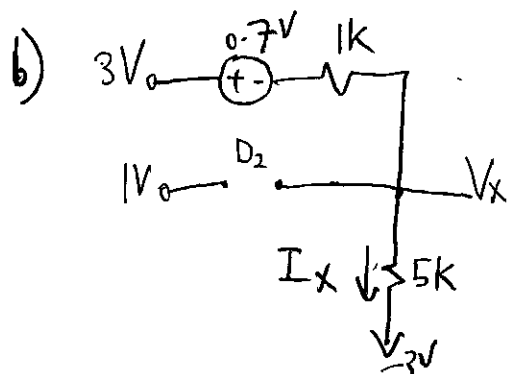


$$I_x = \frac{3V - 0.7V - (-3V)}{1K + 5K} = 0.883mA = I_x$$

$$V_x = 3V - 0.7V - 1K * I_x = 1.4167mV = V_x$$

checks:

$$V_{D2} = 1V - V_x = 0.4V > 0 \rightarrow D_2 \text{ is reverse-biased (RB)}$$
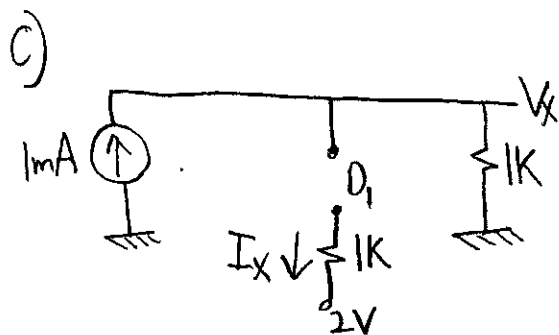
$$I_{D1} = I_x = 0.883mA > 0 \rightarrow D_1 \text{ is Forward-biased (FB)}$$



$$V_x = 1mA * 1K = 1V = V_x$$

$$I_x = 0mA$$


checks:

$$V_{D1} = V_x - 2V = -1V < 0$$

→ D_1 is reverse-biased
(RB)

3

Problem 3

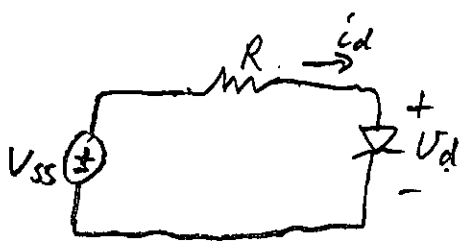

KVL: $0 = -V_{ss} + R \cdot i_d + V_d$


$\hookrightarrow i_d = \frac{V_{ss} - V_d}{R} = \frac{V_{ss}}{R} - \frac{V_d}{R}$

With $V_{ss} = 1V$ and $R = 500\Omega$: $i_d = \frac{1V}{500\Omega} - \frac{V_d}{500\Omega} = 2mA - V_d \cdot 2 \frac{mA}{V}$

With $V_{ss} = 0.5V$ and $R = 500\Omega$: $i_d = 1mA - 2 \frac{mA}{V} V_d$

$\hookrightarrow$ slope of the load line in both cases: $- \frac{2mA}{V} = - \frac{1}{R}$

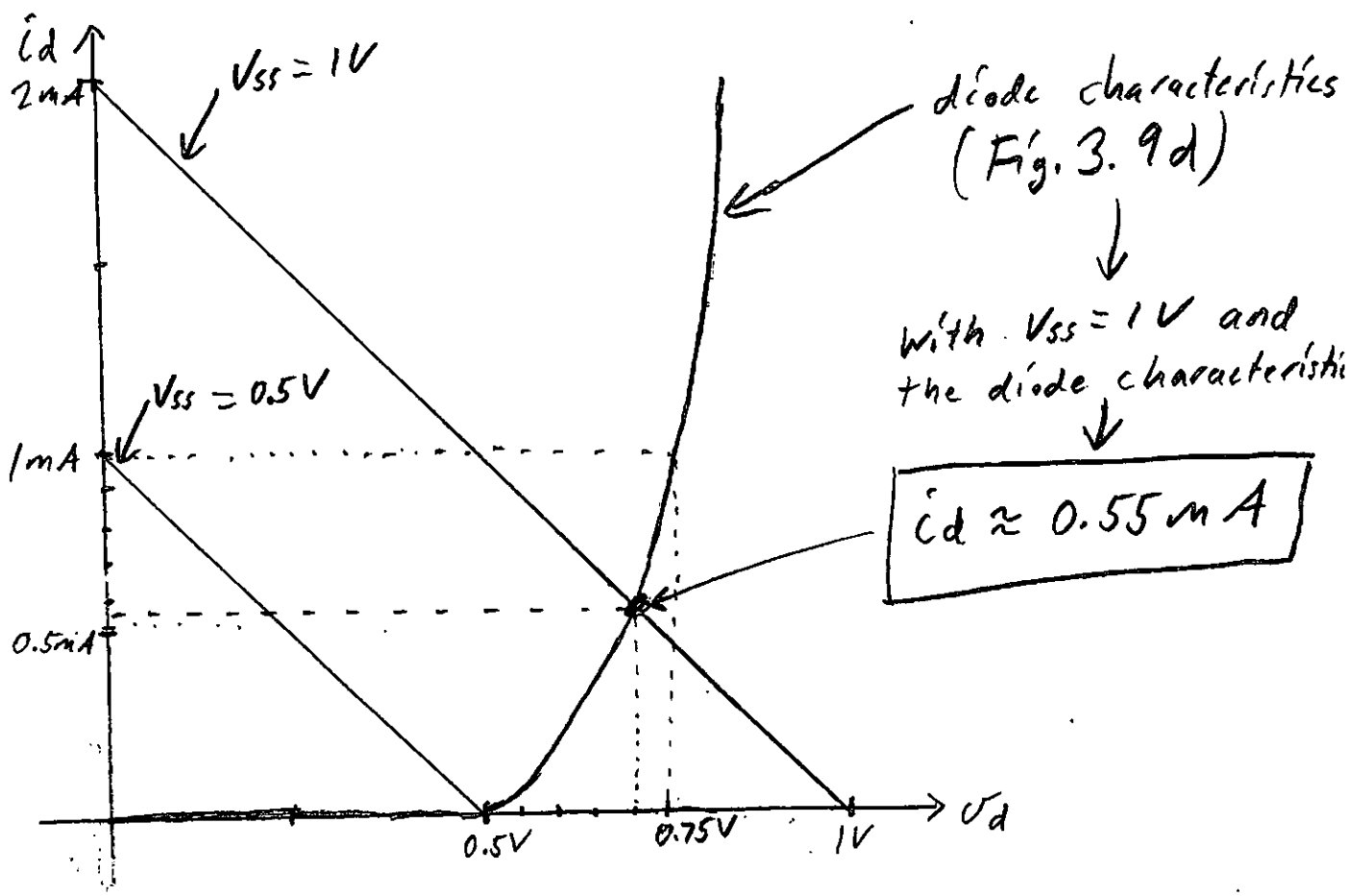$\hookrightarrow$ No, the slope does not change when V_{ss} changes.



④

Prob. 4

a) $50^\circ\text{C} = 323\text{ K}$

equation 3.16 in the book:

$$V_T = \frac{k \cdot T}{q} = \frac{(1.38 \times 10^{-23}) \cdot (323)}{1.60 \times 10^{-19}} = 27.86 \text{ mV}$$

equation 3.15 in the book:

$$I_0 = I_s \cdot \left[e^{\left(\frac{V_D}{n \cdot V_T} \right)} - 1 \right] \rightarrow V_D = n \cdot V_T \cdot \ln \left(\frac{I_D}{I_s} + 1 \right)$$

Since $\frac{I_D}{I_s} \gg 1$ is assumed here:

①: $V_D \approx n \cdot V_T \cdot \ln \left(\frac{I_D}{I_s} \right)$

Using the two given measurement results to determine the emission coefficient:

$$V_{D2} - V_{D1} = n \cdot V_T \cdot \ln \left(\frac{I_{D2}}{I_s} \right) - n \cdot V_T \cdot \ln \left(\frac{I_{D1}}{I_s} \right)$$

$$V_{D2} - V_{D1} = n \cdot V_T \cdot \ln \left(\frac{I_{D2}}{I_{D1}} \right)$$

$$0.6 - 0.5 = n \cdot (27.86 \times 10^{-3}) \cdot \ln \left(\frac{120 \times 10^{-6}}{7 \times 10^{-6}} \right)$$

$$\rightarrow \boxed{n = 1.263}$$

b) Rearranging equation ① above:


$$I_s = \frac{I_0}{e^{\frac{V_D}{n \cdot V_T}}} = \frac{\times 10^{-6}}{e^{\frac{0.5}{(1.263) \cdot (27.86 \times 10^{-3})}}}$$

$$\boxed{I_s = 4.728 \times 10^{-12} \text{ A} = 4.728 \text{ pA}}$$

⑤

Problem 5!

a)

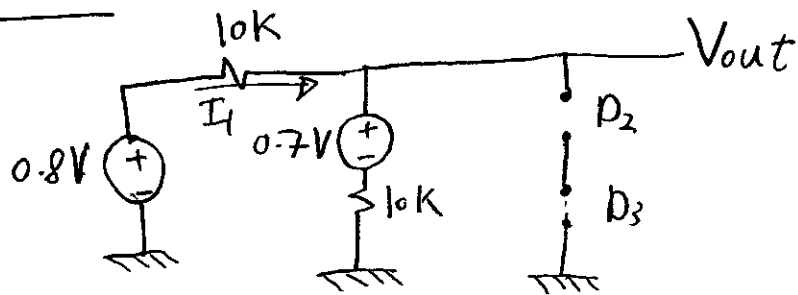

Using KVL

$$0.8V - I_1 \times 10K - 0.7V - I_1 \times 10K = 0$$

$$I_1 = 5\mu A$$

$$V_{out} = 0.8V - I_1 \times 10K = \boxed{0.75V = V_{out}}$$

Checks:


$$I_{D1} = I_1 > 0 \rightarrow D_1 \text{ is Forward-biased (FB)}$$

$$V_{D1} + V_{D2} = 0.75V < 1.4V \rightarrow D_2, D_3 \text{ are reverse-biased (RB)}$$

6

Problem 5, Part b)

Verification with $V1 = 0.8V$:

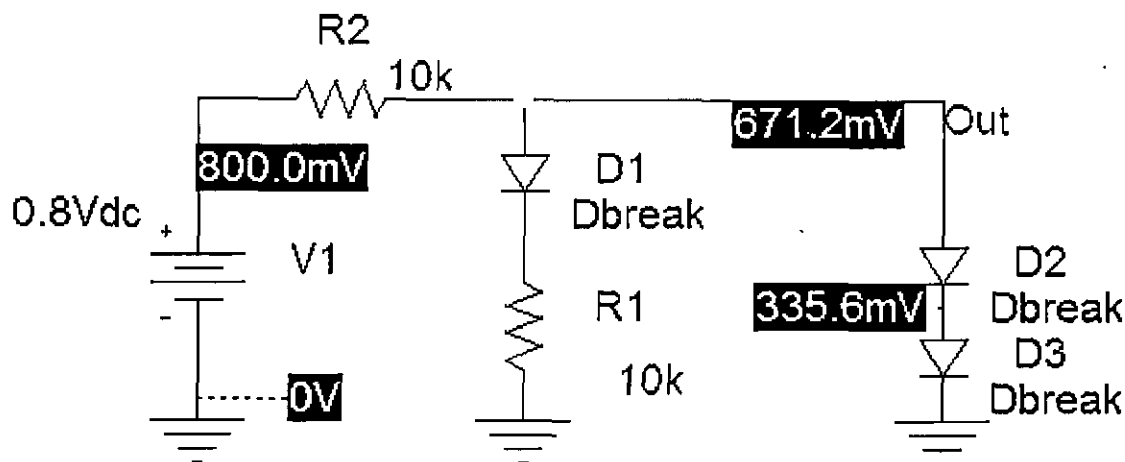

Part c) Transfer characteristic:

