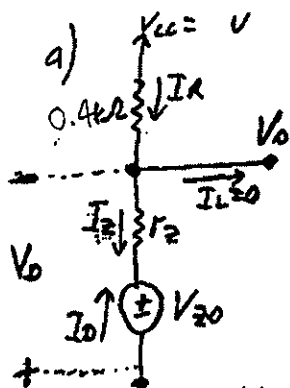


①

Prob. 1



assuming the diode is in the breakdown region

$$I_Z = \frac{V_{CC} - V_{Z0}}{0.4k\Omega + r_Z} = \frac{9V - 6.7V}{0.4k\Omega + 20\Omega} = 5.48mA$$

$I_Z > I_{ZK} = 0.2mA \rightarrow$ The Zener is in breakdown.

$$V_O = I_Z \cdot r_Z + V_{Z0} = (5.48mA) \cdot (20\Omega) + 6.7V$$

$$\boxed{V_O = 6.8V}$$

b) Repeating the calculations in part a) with $V_{CC} = 8V$ and $V_{CC} = 10V$:


$$V_{O(max)} = 6.86V$$

$$V_{O(min)} = 6.76V$$

$$\Delta V_{O(max)} = V_{O(max)} - V_O \approx 47.6mV$$

$$\Delta V_{O(min)} = V_{O(min)} - V_O \approx -47.6mV$$
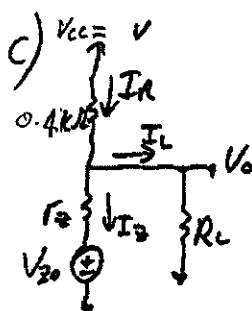
$$\boxed{\Delta V_{CC} \text{ of } \pm 1V \text{ results in } \Delta V_O \text{ of } \pm 47.6mV}$$



$$I_R = \frac{9V - V_O}{k\Omega}$$

$$I_L = \frac{V_O}{R_L}, \quad I_Z = \frac{V_O - V_{Z0}}{r_Z}$$

$$I_R = I_L + I_Z$$

$$\hookrightarrow \frac{9V - V_O}{0.4k\Omega} = \frac{V_O}{2k\Omega} + \frac{V_O - 6.7V}{20\Omega}$$

(solving for V_O) $\rightarrow \boxed{V_O = 6.75V}$

$$\Delta V_O = 6.75V - 6.8V = -64.2mV = \Delta V_O$$

check: $I_Z = \frac{6.75V - 6.7V}{20\Omega} = 2.5mA > I_{ZK} \rightarrow$ The Zener is in breakdown.

d) Repeating the analysis in c) with $R_L = 0.5k\Omega$ results in:

$$V_O = 6.56V$$

Diode assumption check: $I_Z = \frac{6.56V - 6.7V}{20\Omega} = -7.02mA < I_{ZK}$

$\rightarrow$ does not satisfy the breakdown region condition

Assuming that the diode is reverse-biased ("off"):

$$V_O = V \cdot \left(\frac{R_L}{R_L + 0.4k\Omega} \right) = 9V \cdot \left(\frac{0.5k\Omega}{0.5k\Omega + 0.4k\Omega} \right) = \boxed{5V \approx V_O}$$

check: reverse bias requires that $-V_{Z0} = -6.7V < V_O < V_{D0} \approx 0.7V$

$$\Delta V_O = 5V - 6.8V = -1.8V$$

$\hookrightarrow$ Satisfied because $V_O = -V_O = V$

② ... Prob. 1 cont.:

e) Using the same diagram as in part c):

$I_{ZK} = 0.2 \text{ mA}$ at the edge of the breakdown region

$$I_{ZK} = 0.2 \text{ mA} = \frac{V_0 - V_{Z0}}{r_z} = \frac{V_0 - 6.7 \text{ V}}{20}$$

$$\rightarrow V_0 = 6.704 \text{ V}$$

$$I_{ZK} = 0.2 \text{ mA} = I_R - I_L$$

$$0.2 \text{ mA} = \frac{V_{CC} - V_0}{0.4 \text{ k}\Omega} - \frac{V_0}{R_{L(\text{min.})}} = \frac{V_{CC} - 6.704}{400} - \frac{6.704}{R_{L(\text{min.})}}$$

$$\text{with } V_{CC} = 10 \text{ V} \rightarrow R_{L(\text{min.})} = 833.8 \Omega$$


$$\text{with } V_{CC} = 8 \text{ V} \rightarrow R_{L(\text{min.})} = 2.2 \text{ k}\Omega$$

$$\boxed{R_{L(\text{min.})} = 2.2 \text{ k}\Omega}$$

ensures $I_Z > 0.2 \text{ mA} = I_{ZK}$
(over the complete range of V_{CC})

③ Prob. 2

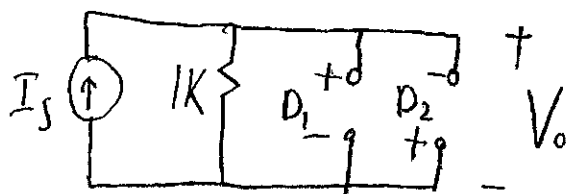Let $-0.7 \text{ mA} < I_S < 0.7 \text{ mA}$



KVL:

$$V_o = I_S \times 1K$$

$$V_{D1} = V_o \rightarrow -0.7V < V_{D1} < 0.7V$$


$\therefore D_1$ is off

$$V_{D2} = -V_o \rightarrow -0.7V < V_{D2} < 0.7V$$

$\therefore D_2$ is off

Let

$$I_S > 0.7 \text{ mA}$$

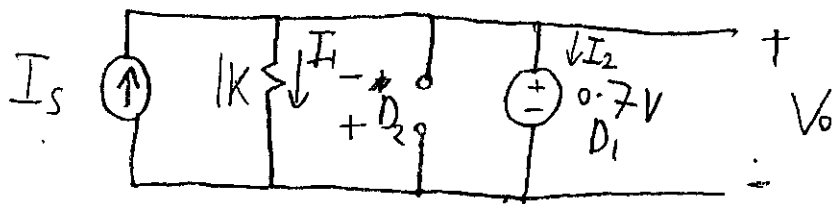

$$V_o = 0.7V = V_{D1}$$

$$I_1 = \frac{V_o}{1K} = 0.7 \text{ mA}, I_2 = I_S - I_1 = I_S - 0.7 \text{ mA} > 0 \rightarrow D_1 \text{ on}$$

$$V_{D2} = -0.7V < 0.7V \rightarrow \therefore D_2 \text{ is off}$$

④ for $I_s < -0.7 \text{ mA}$




$$V_o = -0.7 \text{ V} = -V_{D_2}$$

$$I_1 = \frac{V_o}{1\text{k}} = -0.7 \text{ mA}$$


$$I_2 = I_s - I_1 = I_s + 0.7 \text{ mA} < 0 \rightarrow D_2 \text{ is on}$$
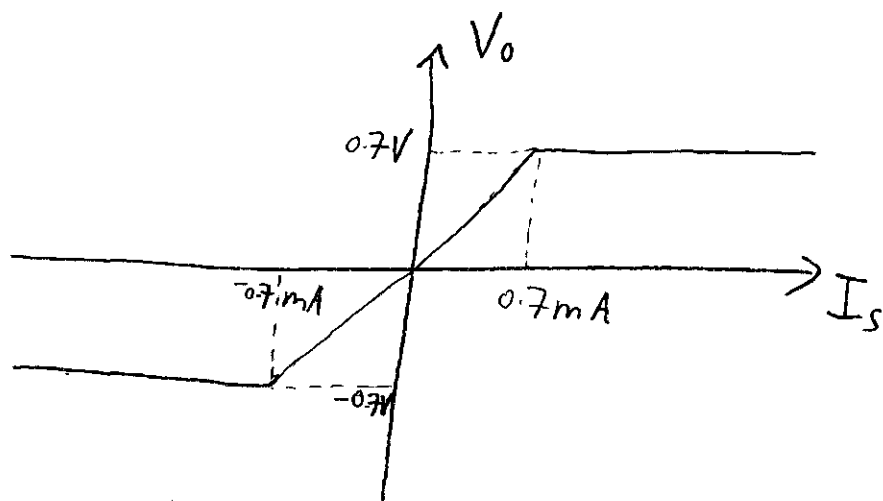
$$V_{D_1} = V_o = -0.7 \text{ V} < 0.7 \text{ V} \rightarrow \therefore D_1 \text{ is off}$$



(5)

Prob. 3

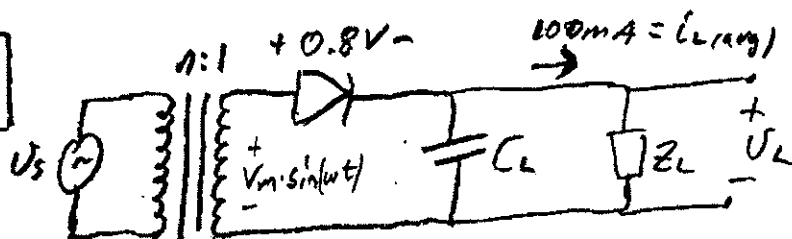

1.) $V_L(avg) = 9V \pm 1V$ ripple
(2V peak-peak) $\rightarrow$

$V_L(min) = 8V$

$V_L(max) = 10V$

2.) KVL:

$V_L(peak) = -0.8V + V_m = 10V \rightarrow$

$V_m = 10.8V$

3.) $V_s(peak) = V_s(RMS) \cdot \sqrt{2} = 110V \cdot \sqrt{2} = 155.563V$

$n = \frac{V_s(peak)}{V_m} = \frac{155.563V}{10.8V} = 14.4 = n$

4.) Using equation 3.4 in the book:

$C = \frac{I_{L(avg)} \cdot T}{V_r} = \frac{(100mA) \cdot (\frac{1}{60Hz})}{2V}$

$C = 833.3 \mu F$

6

Problem 4:

a) DC equivalent circuit:



$$I_{DQ} = \frac{15V - 0.6V}{1k\Omega} = 14.4mA$$

AC equivalent circuit:

$$r_d = \frac{n \cdot V_T}{I_{DQ}} = \frac{1 \cdot 26mV}{14.4mA}$$

$$r_d = 1.806\Omega$$

total output voltage:

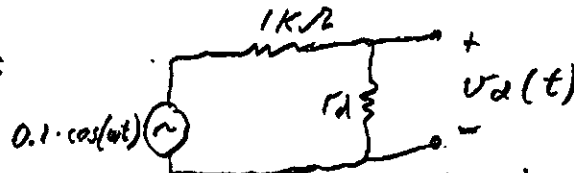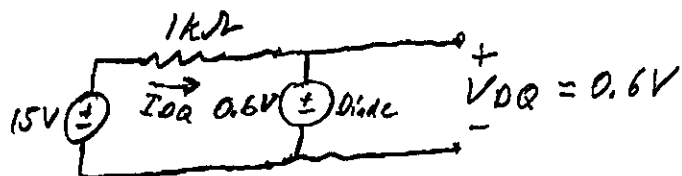

$$v_d(t) = 0.1 \cos(\omega t) \times \left(\frac{r_d}{r_d + 1k\Omega} \right) = 0.18 \times 10^{-3} V \cdot \cos(\omega t)$$

$$V_D(t) = V_{DQ} + v_d(t) = 0.6V + 0.18 \times 10^{-3} V \cdot \cos(\omega t)$$

b) Source regulation = $\frac{\Delta V_o}{\Delta V_{SS}} \times 100\%$


In part a), the change of the source voltage is $\Delta V_{SS} = 0.1V \cos(\omega t)$,

while $\Delta V_o = v_d(t) = 0.18 \times 10^{-3} V \cdot \cos(\omega t)$.


Thus, source regulation = $\frac{0.18 \times 10^{-3} V \cdot \cos(\omega t)}{0.1 V \cdot \cos(\omega t)} \times 100\% = \boxed{0.18\%}$

7

Problem 5

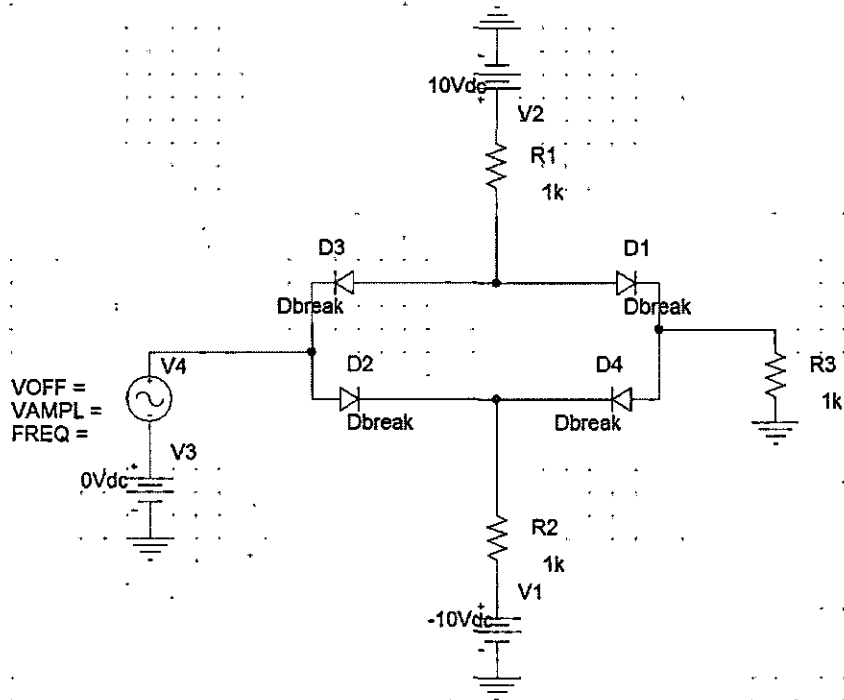


DC Sweep

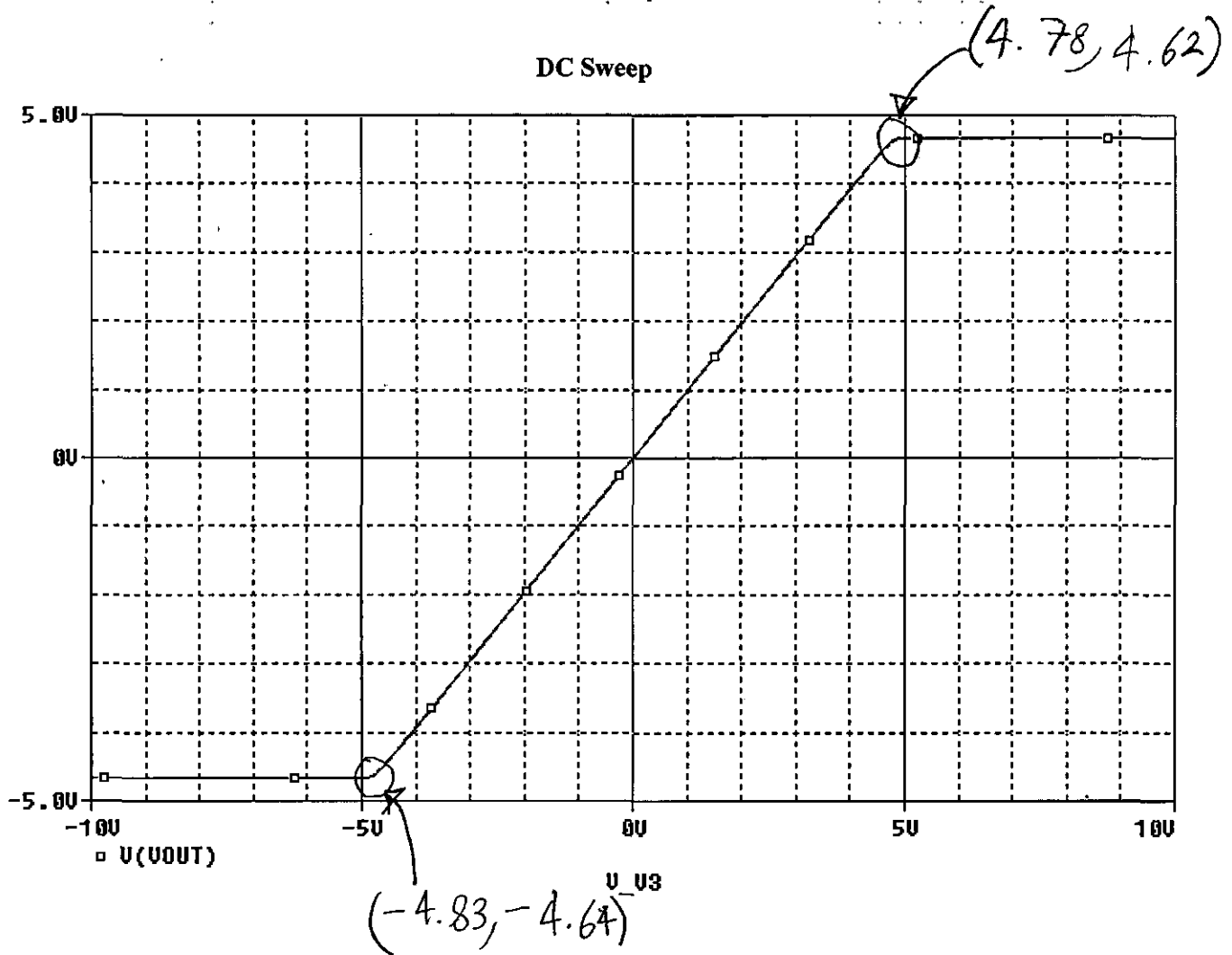

2.96V (8)

Transient analysis at amplitude = 3V.

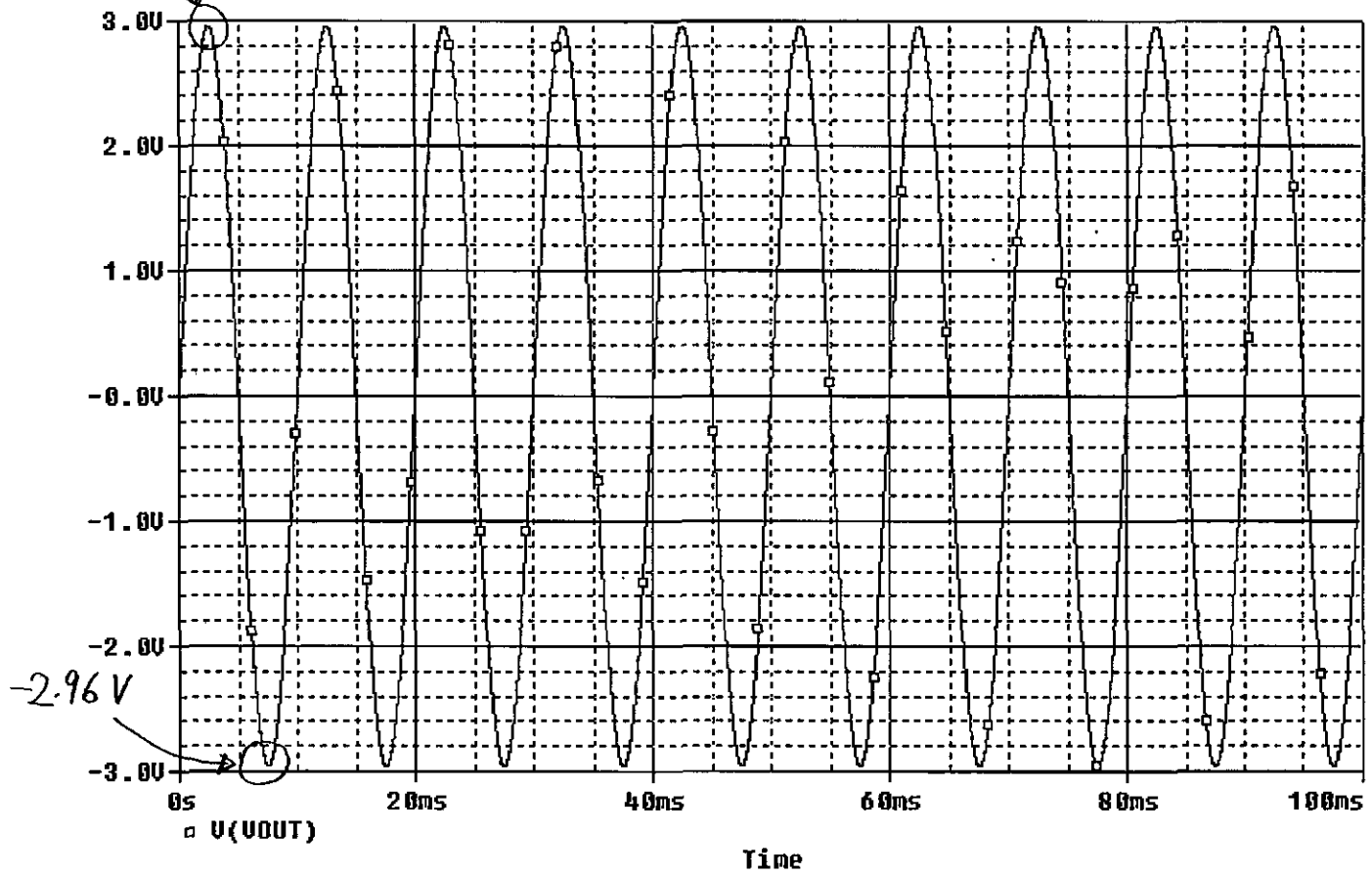

Transient analysis at amplitude = 10V.

