

(P.1)

EECE - HW 5 SolutionsProblem 1:

a) $n \gg p$, therefore: $n + N_A = p + N_D \approx N_D$.

$$\rightarrow n \approx N_D - N_A = 10^{18} \text{ cm}^{-3} - 10^{16} \text{ cm}^{-3} = \boxed{9.9 \times 10^{17} \text{ cm}^{-3} = n}$$

$$p = \frac{n_i^2}{n} = \frac{(1.45 \times 10^{10} \text{ cm}^{-3})^2}{9.9 \times 10^{17} \text{ cm}^{-3}} = \boxed{2.124 \times 10^2 \text{ cm}^{-3} = p}$$

b) $N_A = N_D \rightarrow \boxed{n = p = n_i = 1.45 \times 10^{10} \text{ cm}^{-3}}$

Problem 2:

equation 4.1: $i_E = I_{ES} \cdot \left(e^{\frac{V_{BE}}{V_T}} - 1 \right)$

$$V_{BE} = V_T \cdot \ln \left(\frac{i_E}{I_{ES}} + 1 \right) = 26 \times 10^{-3} \cdot \ln \left(\frac{10 \times 10^{-3}}{10^{-13}} + 1 \right)$$

$$\boxed{V_{BE} = 658.54 \text{ mV}}$$

From page 212 in the book:

$$V_{BC} = V_{BE} - V_{CE} = 0.65854 \text{ V} - 10 \text{ V} = \boxed{-9.341 \text{ V} = V_{BC}}$$

The transistor operates in the active region because $V_{CE} > 0.2 \text{ V}$

and $i_B = (1 - \alpha) \cdot i_E > 0$, where $\alpha = \frac{\beta}{1 + \beta} = \frac{100}{101} = \boxed{0.990099 = \alpha}$

$$i_B = (1 - 0.990099) \cdot 10 \times 10^{-3} \text{ A} = \boxed{99.0099 \mu\text{A} = i_B}$$

$$i_C = \alpha \cdot i_E = 0.990099 \times 10 \text{ mA} = \boxed{9.90099 \text{ mA} = i_C}$$

Problem 3

(2)

a) $\beta = 100$


equivalent circuit assuming operation in active:-

$$I_B = \frac{10 - 0.7}{390 \text{ K}\Omega} = 23.8462 \mu\text{A}$$

$$I = \beta I_B = 2.38 \text{ mA} > 0$$

$$V = V_C = 2.38 \times 2.2 = 5.25 \text{ V}$$
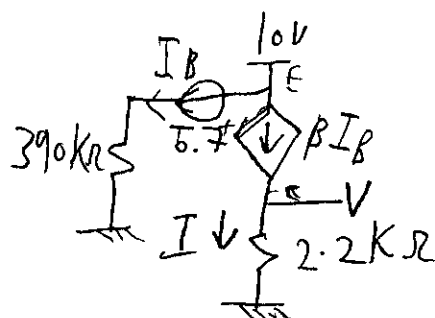
$$V_{EC} = 10 - 5.25 = 4.75 \text{ V} > 0.2 \text{ V} \rightarrow \text{active.}$$




$\beta = 300$

assume saturation

$$I_C = \frac{10 - 0.2}{2.2} = 4.45455 \text{ mA}$$

$$V = 10 - 0.2 = 9.8 \text{ V}$$

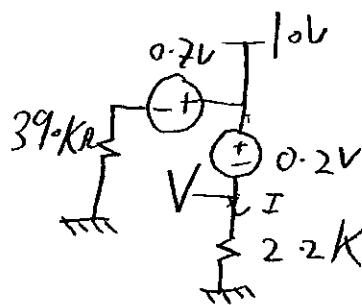

$$\beta I_B > I_C > 0 \rightarrow I_B = \frac{10 - 0.7}{390 \text{ K}\Omega} = 23.8462 \mu\text{A}$$

$$\beta I_B = 7.15385 \text{ mA} > I_C \rightarrow \text{saturation}$$

b) $\beta = 100$

assume cutoff


$$V = 10 \text{ V} = V_C$$

$$V_B = 0 \text{ V}$$

$$I = 0 \text{ A}$$

$$V_{BE} = 0 - 0 = 0 \text{ V} < 0.5 \text{ V} \rightarrow \text{Cond 1}$$
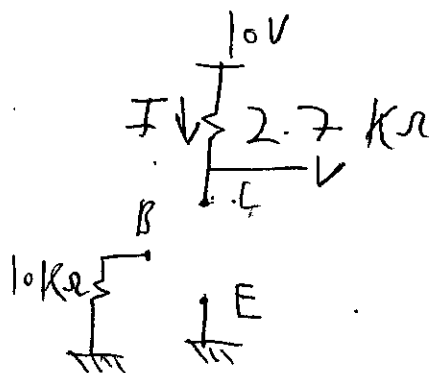
$$V_{BC} = 0 - 10 = -10 \text{ V} < 0.5 \text{ V} \rightarrow \text{Cond 2} \rightarrow \text{cutoff.}$$



Cont. Problem 3

(3)

b) $\beta = 300$

assume cutoff.

$$V_B = 0V$$

$$V_C = 10V$$


$$V_E = 0V$$

$$\therefore I = I_C = 0A$$

$$V = V_C = 10V$$

$$V_{BE} = 0 - 0 = 0V < 0.5V \rightarrow \text{Cond 1} \rightarrow \text{cutoff.}$$

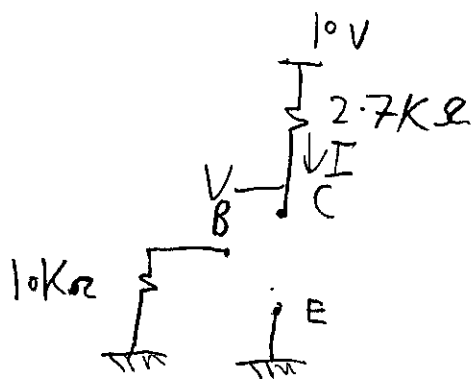
$$V_{BC} = 0 - 10 = -10V < 0.5V \rightarrow \text{Cond 2} \rightarrow \text{cutoff.}$$



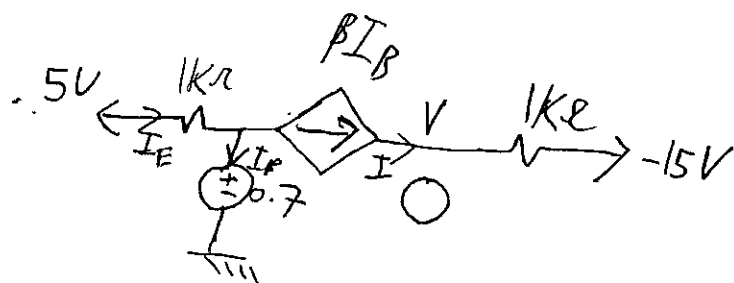c) $\beta = 100$ assume active

$$I_E = I_B + I_C$$

$$\frac{5V - 0.7V}{1K} = I_B + \beta I_B \rightarrow I_B = 42.5743 \mu A$$



$$I = I_C = \beta I_B = 4.25743 \text{ mA} > 0A$$

$$V = -15V + I \times 1K = -10.7426V$$

$$V_{EC} = 0.7 - (-10.7426) = 11.4426V > 0.2V \rightarrow \text{active}$$

$\beta = 300$ assume Active


$$I_E = I_B + I_C$$

$$\frac{5 - 0.7}{1K} = I_B + \beta I_B \rightarrow I_B = 14.2857 \mu A$$

$$I = I_C = \beta I_B = 4.28571 \text{ mA} > 0A$$

$$V = -15V + I \times 1K = -10.7143V$$
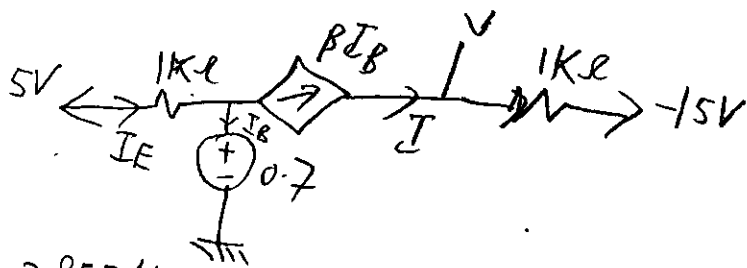
$$V_{EC} = 0.7 - (-10.7143) = 11.4143V > 0.2V \rightarrow \text{active}$$



Cont. problem 3

(4)

a) $\beta = 100$


assume Q_1 active, Q_2 active

$$I_{B1} = \frac{15 - 0.7}{15M\Omega} = 0.95333 \mu A$$

$$I_{B2} = \beta I_{B1} = 95.3333 \mu A$$

$$I = I_{C2} = \beta I_{B2} = 9.5333 \text{ mA}$$

$$V = I \times 1K = 9.5333 \text{ V}$$

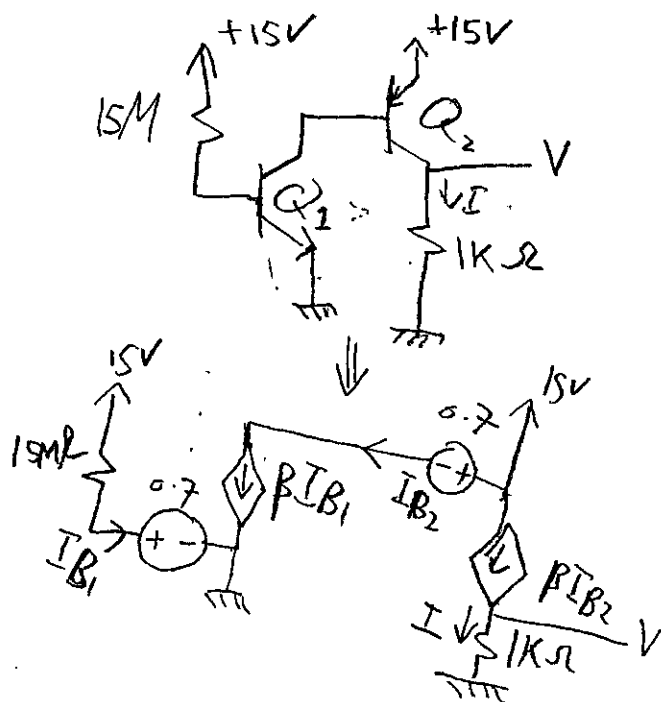

$$15 - 0.7 = V_{CE1} > 0.2 \text{ V} \rightarrow \text{active}$$

$$I_{C1} = \beta I_{B1} = 95.3333 \mu A > 0 \rightarrow \text{active}$$

$$V_{CE2} = 15 - I \times 1K = 5.4667 \text{ V} > 0.2 \text{ V} \rightarrow \text{active}$$

$$I_{C2} = I = 9.53 \text{ mA} > 0 \rightarrow \text{active}$$


$\beta = 300$ assume Q_1 active, Q_2 in saturation

$$I_{B1} = \frac{15 - 0.7}{15M\Omega} = 0.95333 \mu A$$

$$I_{B2} = \beta I_{B1} = 286 \mu A$$

$$I = \frac{15 - 0.2}{1K} = 14.8 \text{ mA}$$

$$V = 15 - 0.2 = 14.8 \text{ V}$$

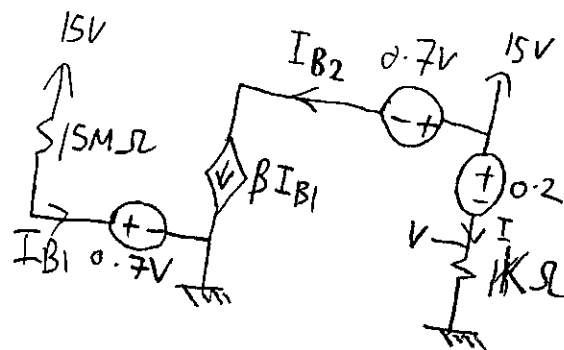

$$V_{CE1} = 15 - 0.7 = 14.3 \text{ V} > 0.2 \text{ V} \rightarrow \text{Active}$$

$$I_{C1} = \beta I_{B1} = 286 \mu A > 0 \rightarrow \text{Active}$$


$$I = I_{C2} > 0, \beta I_{B2} = 85.8 \text{ mA} > I_{C2} \rightarrow \text{Saturation}$$

5

Problem 4:

$$I_B = \frac{4.3V - 2.3V}{20k\Omega} = 100\mu A$$

$$I_x = \frac{2.3V}{230\Omega} = 10mA$$

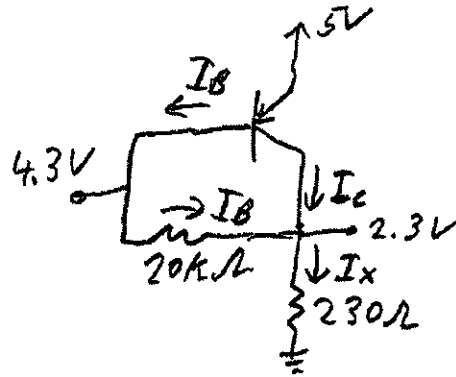


KCL: $I_x = I_B + I_c$

$$\hookrightarrow I_c = I_x - I_B = 10mA - 100\mu A = 9.9mA$$

$$\beta = \frac{I_c}{I_B} = \frac{9.9mA}{100\mu A} = 99 = \beta$$

Problem 5:

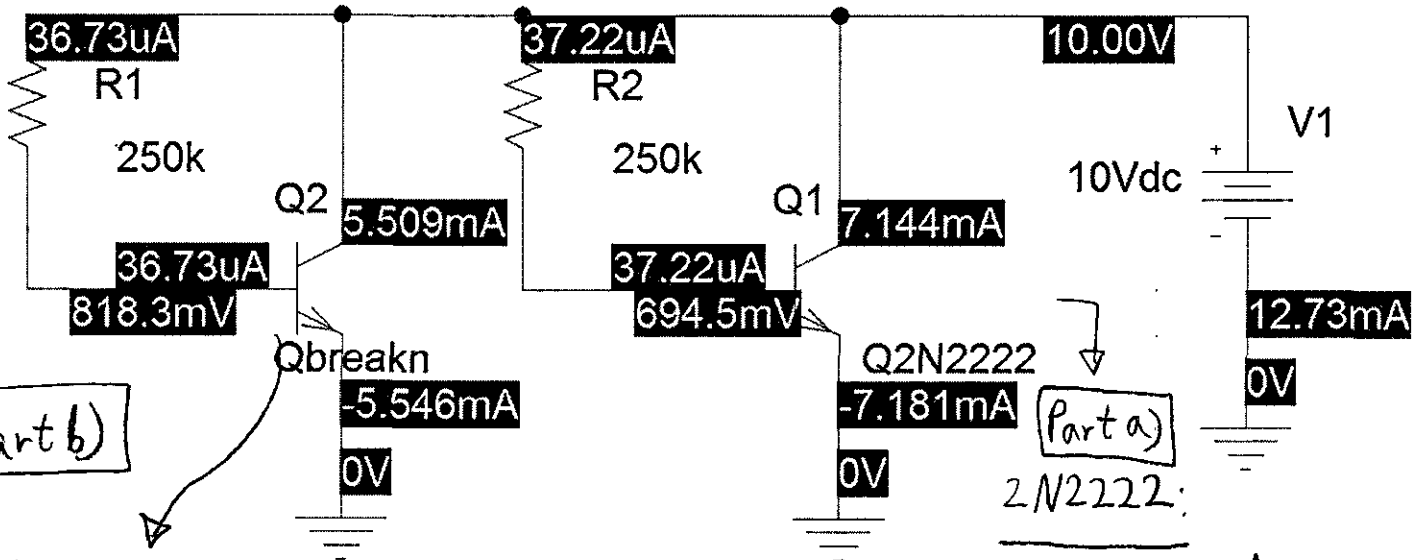

Part b)

Q_{breakN} :

$$\beta_{DC} = \frac{5.509mA}{36.73\mu A}$$

$$\beta_{DC} = 149.986$$

$$\beta_{DC} = \frac{7.144mA}{37.22\mu A}$$

$$\beta_{DC} = 191.94$$

6

**** BJT MODEL PARAMETERS

	Qbreakn	Q2N2222
	NPN	NPN
IS	100.000000E-18	14.340000E-15
BF	150	255.9
NF	1	1
VAR		74.03
IKF		.2847
ISE		14.340000E-15
NE		1.307
BR	1	6.092
NR	1	1
RB		10
RC		1
CJE		22.010000E-12
MJE		.377
CJC		7.306000E-12
MJC		.3416
TF		411.100000E-12
XIF		3
VIF		1.7
ITF		.6
IR		46.910000E-09
XTB		1.5
CN	2.42	2.42
D	.87	.87

Problem 5 Part c)

**** OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C

**** BIPOLAR JUNCTION TRANSISTORS

NAME	Q_Q1	Q_Q2
MODEL	Q2N2222	Qbreakn
IB	3.72E-05	3.67E-05
IC	7.14E-03	5.51E-03
VBE	6.95E-01	8.18E-01
VBC	-9.31E+00	-9.18E+00
VCE	1.00E+01	1.00E+01
BETAAC	1.92E+02	1.50E+02
GM	2.70E-01	2.13E-01
RPI	7.51E+02	7.04E+02
RX	1.00E+01	0.00E+00
RO	1.17E+04	1.00E+12
CBE	1.49E-10	0.00E+00
CBC	3.01E-12	0.00E+00
CJS	0.00E+00	0.00E+00
BETAAC	2.03E+02	1.50E+02
CBX/CBX2	0.00E+00	0.00E+00
FI/FT2	2.83E+08	3.39E+18

(7)

Problem 5, Part d)

Philips Semiconductors

Product specification

NPN switching transistors

2N2222; 2N2222A

CHARACTERISTICS

 $T_J = 25^\circ\text{C}$ unless otherwise specified.

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
I_{CBO}	collector cut-off current 2N2222	$I_E = 0; V_{CB} = 50\text{ V}$	—	10	nA
		$I_E = 0; V_{CB} = 50\text{ V}; T_{amb} = 150^\circ\text{C}$	—	10	μA
I_{CBO}	collector cut-off current 2N2222A	$I_E = 0; V_{CB} = 60\text{ V}$	—	10	nA
		$I_E = 0; V_{CB} = 60\text{ V}; T_{amb} = 150^\circ\text{C}$	—	10	μA
I_{EBO}	emitter cut-off current	$I_C = 0; V_{EB} = 3\text{ V}$	—	10	nA
h_{FE}	DC current gain β_{DC}	$I_C = 0.1\text{ mA}; V_{CE} = 10\text{ V}$	35	—	
		$I_C = 1\text{ mA}; V_{CE} = 10\text{ V}$	50	—	
		$I_C = 10\text{ mA}; V_{CE} = 10\text{ V}$	75	—	
		$I_C = 150\text{ mA}; V_{CE} = 1\text{ V}; \text{note 1}$	50	—	
		$I_C = 150\text{ mA}; V_{CE} = 10\text{ V}; \text{note 1}$	100	300	
h_{FE}	DC current gain 2N2222A	$I_C = 10\text{ mA}; V_{CE} = 10\text{ V}; T_{amb} = -55^\circ\text{C}$	35	—	
h_{FE}	DC current gain 2N2222 2N2222A	$I_C = 500\text{ mA}; V_{CE} = 10\text{ V}; \text{note 1}$	30 40	—	
V_{CEsat}	collector-emitter saturation voltage 2N2222	$I_C = 150\text{ mA}; I_B = 15\text{ mA}; \text{note 1}$	—	400	mV
		$I_C = 500\text{ mA}; I_B = 50\text{ mA}; \text{note 1}$	—	1.6	V
V_{CEsat}	collector-emitter saturation voltage 2N2222A	$I_C = 150\text{ mA}; I_B = 15\text{ mA}; \text{note 1}$	—	300	mV
		$I_C = 500\text{ mA}; I_B = 50\text{ mA}; \text{note 1}$	—	1	V
V_{BEsat}	base-emitter saturation voltage 2N2222	$I_C = 150\text{ mA}; I_B = 15\text{ mA}; \text{note 1}$	—	1.3	V
		$I_C = 500\text{ mA}; I_B = 50\text{ mA}; \text{note 1}$	—	2.6	V
V_{BEsat}	base-emitter saturation voltage 2N2222A	$I_C = 150\text{ mA}; I_B = 15\text{ mA}; \text{note 1}$	0.6	1.2	V
		$I_C = 500\text{ mA}; I_B = 50\text{ mA}; \text{note 1}$	—	2	V
C_c	collector capacitance	$I_E = I_C = 0; V_{CB} = 10\text{ V}; f = 1\text{ MHz}$	—	8	pF
C_e	emitter capacitance 2N2222A	$I_C = I_E = 0; V_{EB} = 500\text{ mV}; f = 1\text{ MHz}$	—	25	pF
f_T	transition frequency 2N2222 2N2222A	$I_C = 20\text{ mA}; V_{CE} = 20\text{ V}; f = 100\text{ MHz}$	250 300	—	MHz MHz
F	noise figure 2N2222A	$I_C = 200\text{ }\mu\text{A}; V_{CE} = 5\text{ V}; R_S = 2\text{ k}\Omega;$ $f = 1\text{ kHz}; B = 200\text{ Hz}$	—	4	dB