

①

EECE 2412 - HW 6 SolutionsProb. 1

For the circuit in Fig. 4.10 on page 224, the equation for the load line at the input is:

$$V_{BB} + v_{in}(t) = R_B \cdot i_B(t) + V_{BE}(t)$$

Substituting the given values:

$$0.8V + 0.2 \sin(2000\pi t) = 40 \times 10^3 \cdot i_B(t) + V_{BE}(t)$$

Observing the relevant cases:

$$1) V_{in}(t) = 0 : i_B = 0 \rightarrow V_{BE} = 0.8V$$

$$V_{BE} = 0 \text{ when } i_B = \frac{0.8V}{40000} = 20\mu A$$


$$2) V_{in}(t) = 0.2V : i_B = 0 \rightarrow V_{BE} = 1V$$

$$V_{BE} = 0 \text{ when } i_B = \frac{1V}{40000} = 25\mu A$$

$$3) V_{in}(t) = -0.2V : i_B = 0 \rightarrow V_{BE} = 0.6V$$


$$V_{BE} = 0 \text{ when } i_B = \frac{0.6V}{40000} = 15\mu A$$

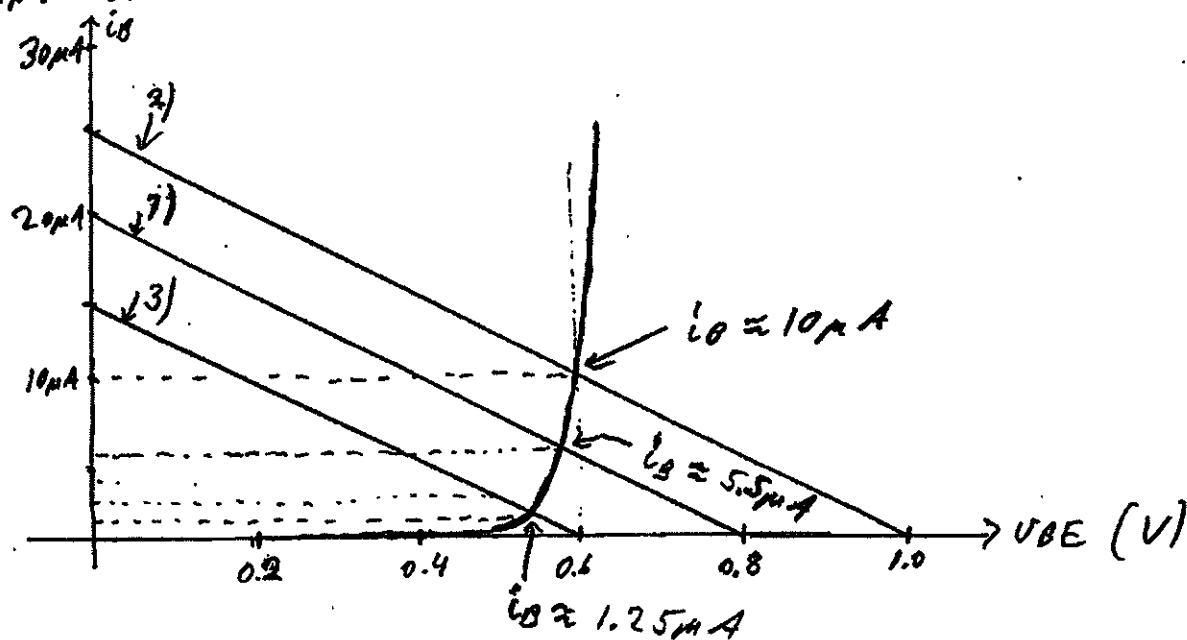Plotting the three load line cases on top of the input characteristic curve:



② ... Problem 1 continued:

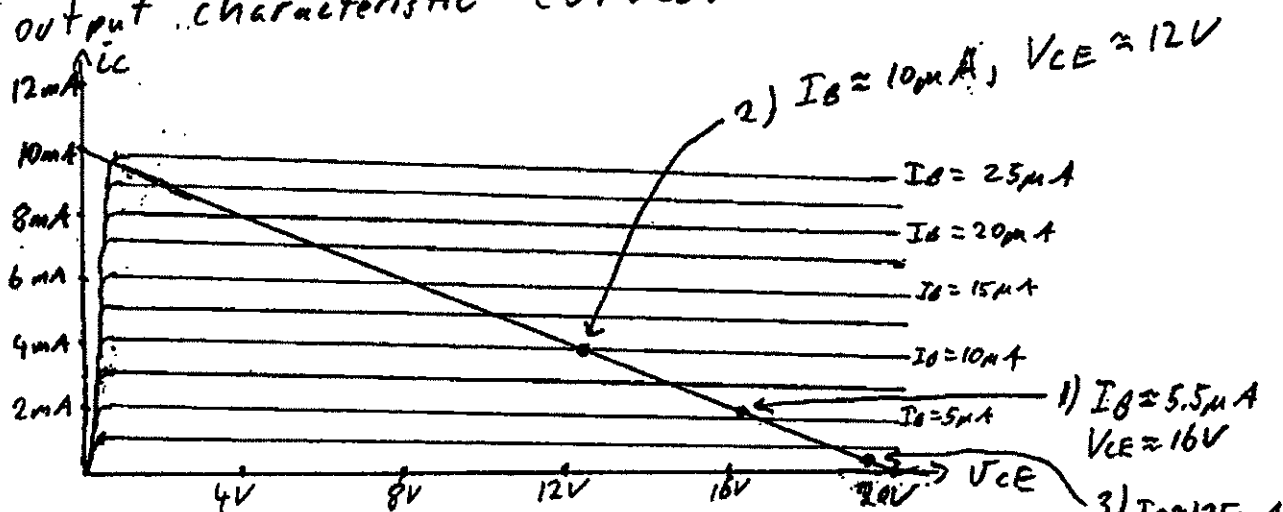Output load line equation: $V_{CC} = R_C \cdot i_C + V_{CE}$
 Substituting the given values: $20 = 2000 \cdot i_C + V_{CE}$
 Plotting this equation on top of the
 output characteristic curves:



Identify the points at which the load line intersects with the curves for the i_B values that were found on the previous page:

The min. and max. instantaneous operating points are:

$$V_{CE} \approx 12 \text{ V}, I_B \approx 10 \mu\text{A}, I_C \approx 4 \text{ mA}$$

$$V_{CE} \approx 19 \text{ V}, I_B \approx 1.25 \mu\text{A}, I_C \approx 0.5 \text{ mA}$$

The output signal is not clipped.

(Clipping would occur if $V_{CE} < 0.2 \text{ V}$ ← BJT would enter the saturation region
 or $V_{CE} > 20 \text{ V}$ for this case
 ↳ not possible due to the supply voltage limit)

③

Prob. 2

$$I_C = 4 \text{ mA}$$

$$\beta = 80$$

a)

$$I_E = \frac{1+\beta}{\beta} \cdot I_C = \frac{81}{80} \cdot 4 \text{ mA} = 4.05 \text{ mA}$$

$$V_E = I_E \cdot R_E = (4.05 \times 10^{-3}) \cdot 200 = 0.81 \text{ V}$$

$$V_B = V_E + V_{BE} = 0.81 + 0.5 = 1.31 \text{ V}$$

$$I_{R2} = \frac{V_B}{R_2} = \frac{1.31}{5000} = 262 \mu\text{A}$$

$$I_B = \frac{I_C}{\beta} = \frac{4 \text{ mA}}{80} = 50 \mu\text{A}$$

$$I_{R1} = I_{R2} + I_B = 312 \mu\text{A}$$


$$V_C = V_B + I_{R1} \cdot R_1 = 1.31 + (312 \times 10^{-6}) \cdot 4000 = 2.558 \text{ V}$$

$$I_X = I_C + I_{R1} = 4 \text{ mA} + 312 \mu\text{A} = 4.312 \text{ mA}$$

$$R_C = \frac{20 \text{ V} - V_C}{I_X} = \frac{20 - 2.558}{4.312 \times 10^{-3}} = \boxed{4.045 \text{ k}\Omega = R_C}$$


b) $V_{CE} = V_C - V_E = 2.558 \text{ V} - 0.81 \text{ V}$

$$\boxed{V_{CE} = 1.748 \text{ V}}$$

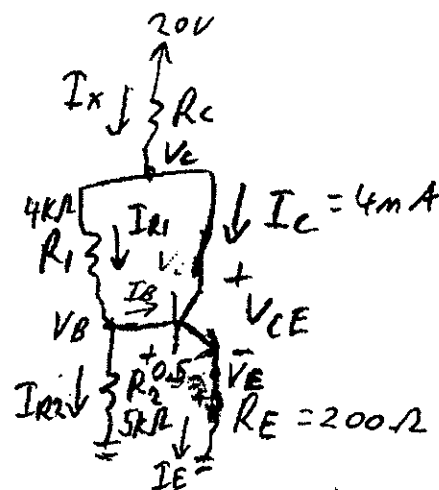

4 Problem 3

a) DC circuit:

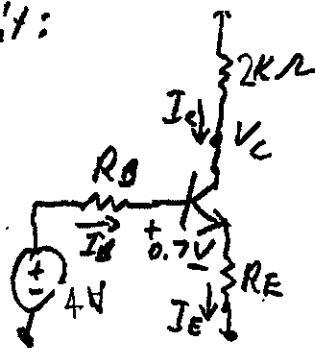

Assuming active mode (by design):

$$①: I_E = \frac{I_C}{\alpha} = \left(\frac{\beta+1}{\beta}\right) \cdot I_C$$

$$②: I_B = \frac{I_C}{\beta}$$

FYI:

for DC analysis:

Capacitor → open-circuit

Inductor → short-circuit

AC voltage source → short-circuit

AC current source → open-circuit

KVL: $0 = -4V + I_B \cdot R_B + 0.7V + I_E \cdot R_E$

Sub. ① and ②: $3.3V = \left(\frac{I_C}{\beta}\right) \cdot R_B + \left(\frac{\beta+1}{\beta}\right) \cdot I_C \cdot R_E$

Case 1: Sub. $\beta = 100$, $I_C = 4mA$ into the above eqn.:

$$3.3V = \left(\frac{4mA}{100}\right) R_B + \left(\frac{100+1}{100}\right) \cdot (4mA) \cdot R_E$$

$$③: 3.3V = (40 \times 10^{-6}) \cdot R_B + (4.04 \times 10^{-3}) \cdot R_E$$

Case 2: Sub. $\beta = 300$, $I_C = 5mA$ into the eqn.:

$$④: 3.3V = (16.67 \times 10^{-6}) \cdot R_B + (5.0167 \times 10^{-3}) \cdot R_E$$

Solving ③ and ④ simultaneously:

$$R_B = 24.1728k\Omega$$

$$R_E = 577.5\Omega$$

b) eqn. 4.42 in the book:

$$g_m = \frac{I_{CQ}}{V_T} \rightarrow g_{m(max)} = \frac{5mA}{26mV} = 0.192 \frac{A}{V} = 192 \frac{mS}{V} \quad (\text{milli-Siemens})$$

$$g_{m(min)} = \frac{4mA}{26mV} = 153.8 \text{ mS}$$

$$153.8mS < g_m < 192mS$$

eqn. 4.37 in the book: $r_{\pi} = \frac{\beta \cdot V_T}{I_{CQ}}$

$$r_{\pi 1} = \frac{300 \times 26mV}{5mA} = 1.56k\Omega$$

$$r_{\pi 2} = \frac{100 \times 26mV}{4mA} = 650\Omega$$

$$650\Omega < r_{\pi} < 1560\Omega$$

Lecture slides: $r_{ce} = \frac{V_A}{I_{CQ}}$

$$r_{ce(max)} = \frac{100V}{4mA} = 25k\Omega$$


$$r_{ce(min)} = \frac{100V}{5mA} = 20k\Omega$$

$$20k\Omega < r_{ce} < 25k\Omega$$

⑤

... Problem 3 continued :

c) Small-signal equivalent circuit:

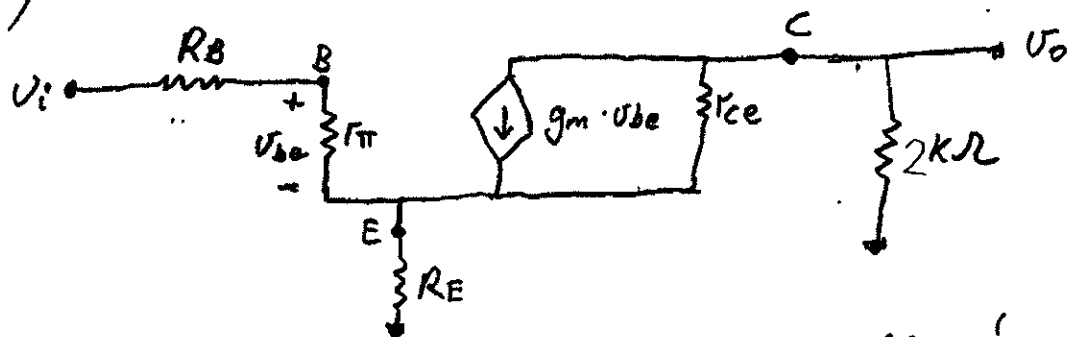


(FYI: In the AC analysis (small-signal equivalent circuit), replace:
 DC voltage sources $\rightarrow$ short-circuits
 DC current sources $\rightarrow$ open-circuits)

d) PSpice: see next page


6

d)

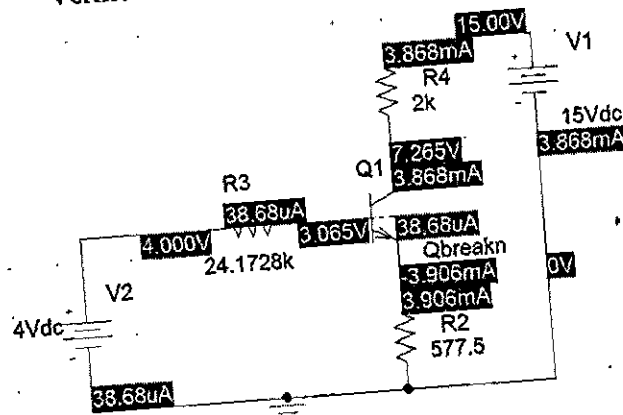
Verification with $\beta=100$ (I_c is close to 4mA)



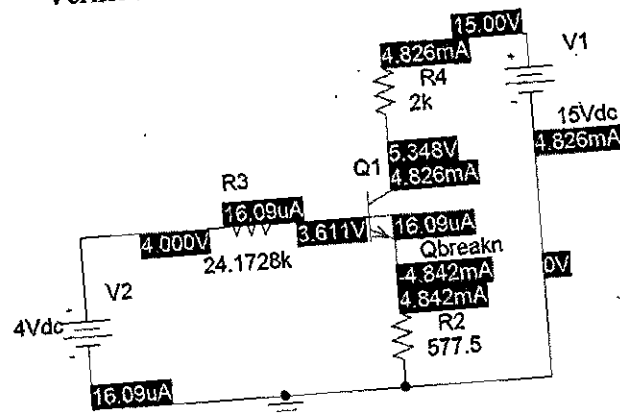Verification with $\beta=300$ (I_c is close to 5mA)



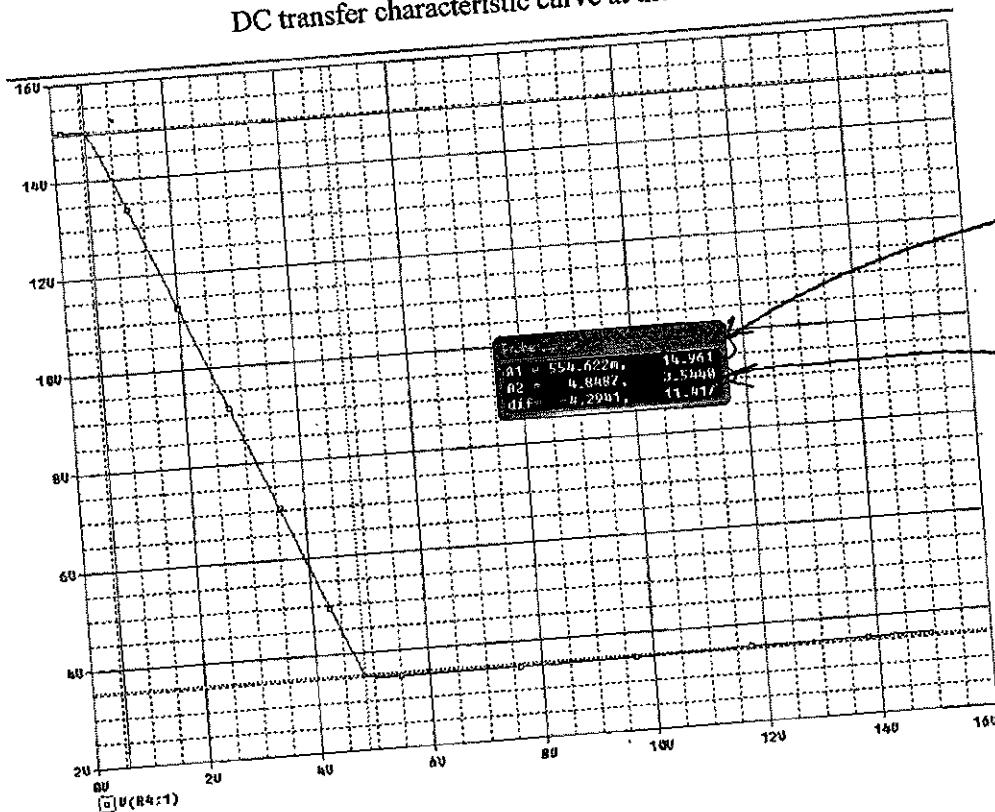DC transfer characteristic curve at the collector (V_c vs. V_{BB}) ith QN222 BJT model



$V_o(max)$
 $V_o(max) - V_o(min) = 11.417V$
 $= V_o(p-p)$
 $V_o(min)$

When:
 $V_{BB} = \left(0.555 + \frac{4.294}{2} \right)$
 $= 2.70205V$


P.7 Problem 4

a) with $\beta = \infty \rightarrow I_B = 0$

$$\hookrightarrow I_E = I_C = 3 \text{ mA}$$

$$\text{KVL: } 0 = -3\text{V} + I_C \cdot R_C + V_C$$
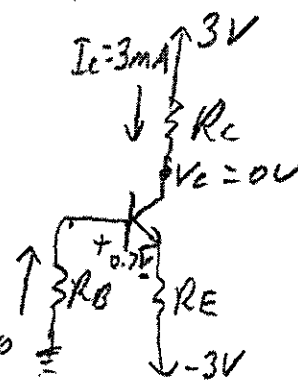
$$V_C = 0\text{V} \hookrightarrow R_C = \frac{3\text{V}}{I_C} = \frac{3\text{V}}{3\text{mA}} = \boxed{1\text{k}\Omega = R_C}$$



$$\text{KVL: } 0 = I_B \cdot R_B + 0.7\text{V} + I_E \cdot R_E - 3\text{V}$$


$$\hookrightarrow R_E = \frac{(3\text{V} - 0.7\text{V})}{3 \times 10^{-3}\text{A}} = \boxed{766.67\Omega = R_E}$$

b) $\beta = 90$, constraint: $\frac{V_{RE}}{10} = V_{RB}$

$$\frac{I_E \cdot R_E}{10} = I_B \cdot R_B \rightarrow \frac{I_E R_E}{10} = \frac{I_E \cdot R_B}{\beta + 1}$$

$$\rightarrow \textcircled{1}: R_B = \frac{\beta + 1}{10} \cdot R_E$$
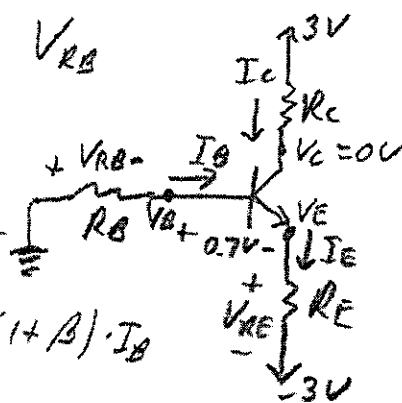
$$\text{using } I_E = (1 + \beta) \cdot I_B$$



$$\text{KVL: } 0 = V_{RB} + 0.7\text{V} + V_{RE} - 3\text{V}$$

$$2.3\text{V} = \frac{V_{RE}}{10} + V_{RE} \rightarrow V_{RE} = 2.0909\text{V}$$

$$I_E = \frac{I_C}{\alpha} = \frac{\beta + 1}{\beta} \cdot I_C = \frac{90 + 1}{90} \cdot 3\text{mA} = 3.0333\text{mA}$$

$$R_E = \frac{V_{RE}}{I_E} = \frac{2.0909\text{V}}{3.0333\text{mA}} = \boxed{689.3\Omega = R_E}$$

Substituting the value of R_E into equation $\textcircled{1}$:

$$R_B = \frac{90 + 1}{10} \cdot 689.3\Omega = \boxed{6272\Omega = R_B}$$

$$R_C = \frac{3\text{V} - V_C}{I_C} = \frac{3\text{V} - 0\text{V}}{3\text{mA}} = \boxed{1\text{k}\Omega = R_C}$$

p.8) ... Problem 4 cont.:

c) Standard 5% - resistor values for the results in part b):

$$R_C = 1k\Omega$$

$$R_E = 680\Omega$$

$$R_B = 6.2k\Omega$$

d) With $\beta = \infty$: $I_B = 0$, $I_C = I_E$

$$\text{KVL: } 0 = I_B \cdot R_B + V_B \rightarrow V_B = 0$$

$$\text{KVL: } 0 = I_B \cdot R_B + 0.7V + V_E \rightarrow V_E = -0.7V$$

$$\text{KVL: } 0 = I_B \cdot R_B + 0.7V + I_E \cdot R_E - 3V$$

$$\hookrightarrow I_E = \frac{3V - 0.7V}{R_E} = \frac{2.3V}{680\Omega} = 3.382 \text{ mA}$$

$$I_C = I_E = 3.382 \text{ mA}$$

With $\beta = 90$:

$$\text{KVL: } 0 = I_B \cdot R_B + 0.7V + I_E \cdot R_E - 3V$$

$$0 = \frac{I_E}{\beta + 1} \cdot R_B + I_E \cdot R_E - 2.3V$$

$$2.3V = \frac{I_E}{91} \cdot 6200 + I_E \cdot 680 \rightarrow I_E = 3.074 \text{ mA}$$

$$I_C = \alpha \cdot I_E = \frac{\beta}{\beta + 1} \cdot I_E = \frac{90}{91} \cdot I_E = 3.041 \text{ mA} = I_C$$

$$\text{KVL: } 0 = I_B \cdot R_B + V_B \rightarrow V_B = -I_B \cdot R_B = -\frac{I_C}{\beta} \cdot R_B = -\frac{3.041 \text{ mA}}{90} \cdot 6200\Omega$$

$$V_B = -0.209V$$


$$V_E = V_B - 0.7V = -0.909V = V_E$$

$$V_C = 3V - I_C \cdot R_C = 3V - 3.041 \text{ mA} \cdot 1k\Omega = -0.0405V = V_C$$

P-7

Problem 4, Part e)

with $\beta=90$:

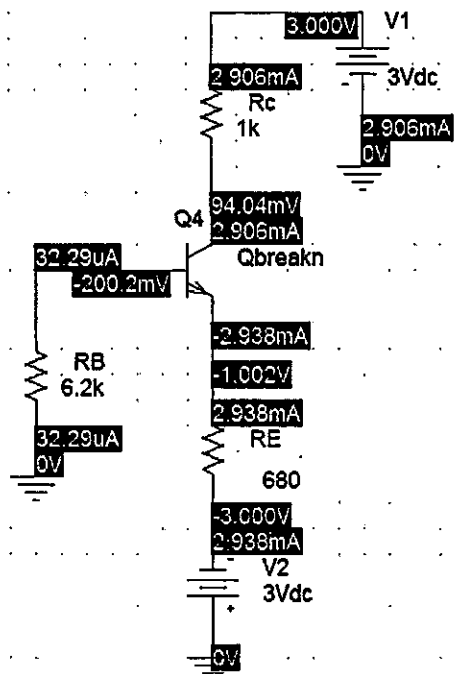

with $\beta=400$:

