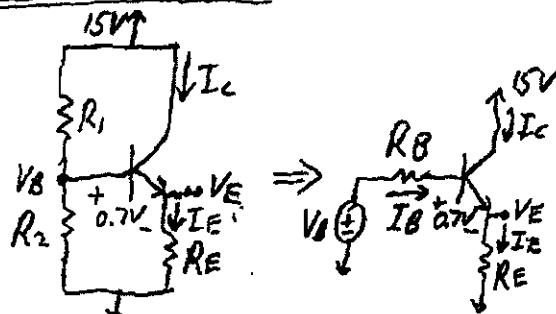


1

EECE 2412: HW 7 Solutions

Prob. 1

DC circuit:



$$V_B = 15V \cdot \left(\frac{R_1}{R_1 + R_2} \right) = 15V \cdot \left(\frac{10k\Omega}{20k\Omega} \right)$$

$$V_B = 7.5V$$

$$R_B = R_1 || R_2 = 5k\Omega$$

$$KVL: -V_B + I_B \cdot R_B + 0.7V + I_E \cdot R_E = 0$$

$$\hookrightarrow 0 = -V_B + \left(\frac{I_C}{\beta} \right) \cdot R_B + 0.7V + \left(\frac{\beta+1}{\beta} \right) \cdot I_C \cdot R_E$$

$$0 = -7.5V + \left(\frac{I_{CQ}}{100} \right) \cdot (5000) + 0.7V + \left(\frac{101}{100} \right) \cdot I_{CQ} \cdot (1000)$$

$$\hookrightarrow \boxed{I_{CQ} = 6.42 \text{ mA}}$$

$$r_{\pi} = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{100 \cdot (26 \text{ mV})}{6.42 \text{ mA}} = \boxed{405 \Omega = r_{\pi}} \quad (\text{at room temp.})$$

Small-signal equivalent circuit: see Fig. 4.36 in the book
Using the small-signal analysis results in section 4.8 of the book:

$$R_L' = R_L || R_E = 1k\Omega || 500\Omega = 333\Omega$$

$$A_v = \frac{R_L' (\beta+1)}{r_{\pi} + R_L' (\beta+1)} = \frac{333(101)}{405 + 333(101)} = \boxed{0.988 = A_v}$$

$$Z_{in} = R_B || \left[r_{\pi} + R_L' (\beta+1) \right] = \frac{1}{\frac{1}{5000} + \frac{1}{405 + 333(101)}} = \boxed{4.36k\Omega = Z_{in}}$$

$$A_i = A_v \cdot \frac{Z_{in}}{R_L} \leftarrow \text{equation 1.4 on page 20} = (0.988) \cdot \frac{4360}{500} = \boxed{8.62 = A_i}$$

$$R_s' = R_B || R_s = 5k\Omega || 1k\Omega = 833\Omega$$

$$Z_o = R_E || \left[\frac{R_s' + r_{\pi}}{\beta+1} \right] = 1k\Omega || \left(\frac{833 + 405}{101} \right) = \boxed{12.1\Omega = Z_o}$$

$$G = A_v \cdot A_i = (0.988) \cdot (8.62) = \boxed{8.52 = G}$$


P2

Problem 2

a) DC equivalent circuit:

$$V_{B0} = 9V \cdot \frac{R_2}{R_1 + R_2} = 4.17V$$

$$R_B = R_1 // R_2 = 57.4 k\Omega$$

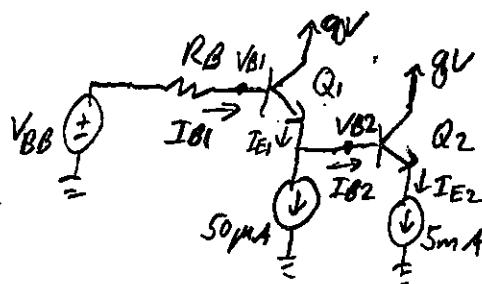

$$I_{E2} = 5mA$$

$$I_{E2} = (1 + \beta) \cdot I_{B2} \rightarrow I_{B2} = \frac{I_{E2}}{1 + \beta_2} = \frac{5mA}{1 + 100}$$

$$I_{B2} = 49.50 \mu A$$

$$I_{E1} = 50 \mu A + I_{B2} = 99.50 \mu A = I_{E1}$$

$$I_{B1} = \frac{I_{E1}}{1 + \beta_1} = \frac{99.50 \mu A}{1 + 50} = 1.951 \mu A$$


$$V_{B1} = V_{BB} - I_{B1} \cdot R_B = 4.17V - (1.951 \times 10^{-6}) \cdot (57.4 \times 10^3) = 3.05V = V_{B1}$$

$$V_{B2} = V_{B1} - V_{BE1} = 3.05V - 0.7V = 2.35V = V_{B2}$$

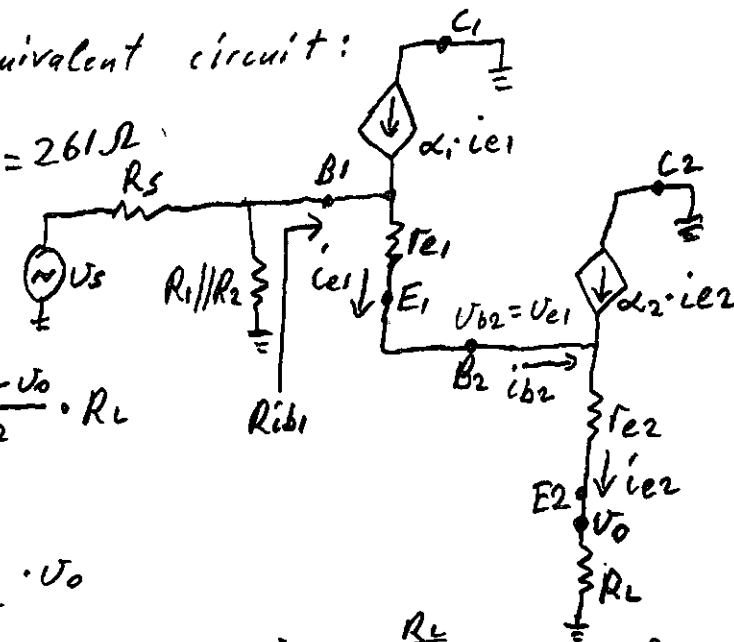b) Small-signal equivalent circuit:

$$r_{e1} = \frac{V_T}{I_{EQ1}} = \frac{26 \times 10^{-3}V}{99.5 \times 10^{-6}A} = 261 \Omega$$

$$r_{e2} = \frac{V_T}{I_{EQ2}} = \frac{26mV}{5mA} = 5.2 \Omega$$



$$V_o = i_{e2} \cdot R_L = \frac{V_{B2} - V_o}{r_{e2}} \cdot R_L$$

$$i_{e2} = \frac{V_{B2} - V_o}{r_{e2}} \quad \text{Sub.}$$

$$V_o = \frac{R_L}{r_{e2}} \cdot V_{B2} - \frac{R_L}{r_{e2}} \cdot V_o$$

$$V_o \cdot \left(1 + \frac{R_L}{r_{e2}}\right) = \frac{R_L}{r_{e2}} \cdot V_{B2} \rightarrow \frac{V_o}{V_{B2}} = \frac{\frac{R_L}{r_{e2}}}{1 + \frac{R_L}{r_{e2}}} = \frac{R_L}{r_{e2} + R_L}$$

$$\frac{V_o}{V_{e1}} = \frac{V_o}{V_{B2}} = \frac{R_L}{r_{e2} + R_L} = \frac{2000}{5.2 + 2000} = 0.9974$$

P3) ... Problem 2 b) continued:

$$i_{b2} = i_{e2} - \alpha \cdot i_{e2} = (1 - \alpha) \cdot i_{e2} = (1 - \alpha) \cdot \left(\frac{V_{b2}}{r_{e2} + R_L} \right)$$

$i_{e2} = \frac{V_{b2}}{r_{e2} + R_L}$ Sub.

$$R_{ib2} = \frac{V_{b2}}{i_{b2}} = \frac{r_{e2} + R_L}{1 - \alpha_2} = \frac{r_{e2} + R_L}{1 - \frac{\beta_2}{\beta_2 + 1}} = \frac{(1 + \beta_2) \cdot (r_{e2} + R_L)}{\beta_2 + 1 - \beta_2} = (1 + \beta_2) \cdot (r_{e2} + R_L)$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$R_{ib2} = (1 + \beta_2) \cdot (r_{e2} + R_L)$$

$$R_{ib2} = (1 + 100) \cdot (5.2 \Omega + 2000 \Omega) = 202.5 \text{ k}\Omega = R_{ib2}$$


c)

$$V_{e1} = i_{e1} \cdot R_{ib2} = \frac{V_{b1} - V_{e1}}{r_{e1}} \cdot R_{ib2}$$

($r_{e1} = 261 \Omega$ [from part b])

$$\frac{V_{e1}}{V_{b1}} = \frac{R_{ib2}}{r_{e1} + R_{ib2}} = \frac{202.5 \times 10^3}{261 + 202.5 \times 10^3}$$
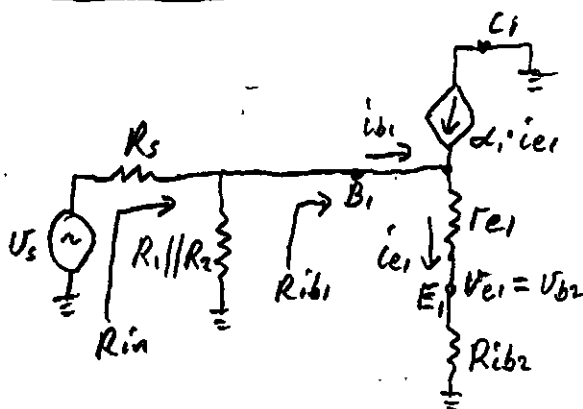
$$\frac{V_{e1}}{V_{b1}} = \frac{V_{b2}}{V_{b1}} = 0.9987$$



$$i_{b1} = i_{e1} - \alpha_1 i_{e1} = (1 - \alpha_1) \cdot \frac{V_{b1}}{r_{e1} + R_{ib2}}$$

$$R_{ib1} = \frac{V_{b1}}{i_{b1}} = \frac{r_{e1} + R_{ib2}}{(1 - \alpha_1)} = (1 + \beta_1) \cdot (r_{e1} + R_{ib2})$$

$$R_{ib1} = (1 + 50) \cdot (261 \Omega + 202.5 \text{ k}\Omega) = 10.34 \text{ M}\Omega = R_{ib2}$$

$$R_{in} = R_{ib1} \parallel R_1 \parallel R_2 = \frac{1}{\frac{1}{10.34 \text{ M}\Omega} + \frac{1}{1.1 \text{ M}\Omega} + \frac{1}{12 \text{ M}\Omega}} = 544 \text{ k}\Omega = R_{in}$$



$$\frac{V_{b1}}{V_s} = \frac{R_{in}}{R_s + R_{in}} = \frac{544}{10 + 544} = 0.819 \text{ V/V}$$


e)

$$\frac{V_o}{V_s} = \frac{V_{b1}}{V_s} \cdot \frac{V_{e1}}{V_{b1}} \cdot \frac{V_o}{V_{e1}} = 0.819 \times 0.9987 \times 0.9974 = 0.816 \text{ V/V} = \frac{V_o}{V_s}$$

(p.4)

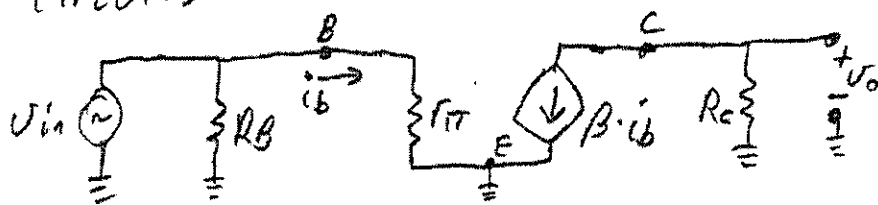Problem 3


The equivalent circuit is identical for both circuits when $V_{hum} = 0$ during small-signal analysis.



$$i_b = \frac{V_{in}}{r_{\pi}}$$

$$V_o = -\beta \cdot i_b \cdot R_c = -\beta \cdot \frac{V_{in}}{r_{\pi}} \cdot R_c \rightarrow \boxed{\frac{V_o}{V_{in}} = -\frac{\beta \cdot R_c}{r_{\pi}}}$$


(a) With $V_{in} = 0$:

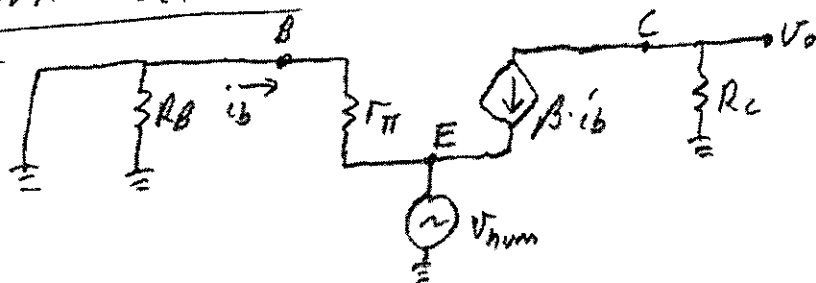

$$i_b = -\frac{V_{hum}}{r_{\pi}}$$

$$V_o = -\beta \cdot i_b \cdot R_c = \beta \cdot \frac{V_{hum}}{r_{\pi}} \cdot R_c \rightarrow \boxed{\frac{V_o}{V_{hum}} = \frac{\beta \cdot R_c}{r_{\pi}}}$$

(b) With $V_{in} = 0$:

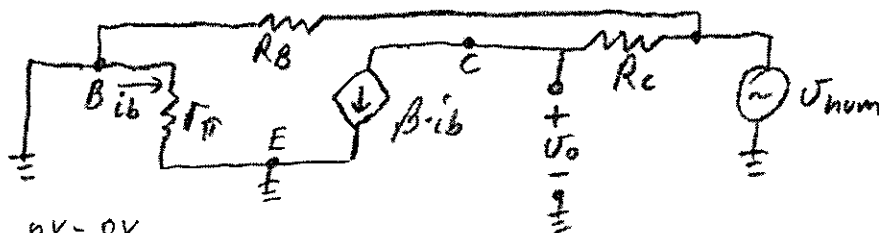


$$i_b = \frac{0V - 0V}{r_{\pi}} = 0 \rightarrow \beta \cdot i_b = 0$$

$$\text{KVL: } 0 = -V_o - \beta \cdot i_b + V_{hum} \rightarrow V_o = V_{hum} \rightarrow \boxed{\frac{V_o}{V_{hum}} = 1}$$

(p.5)

... Prob. 3 cont.:

DC analysis:

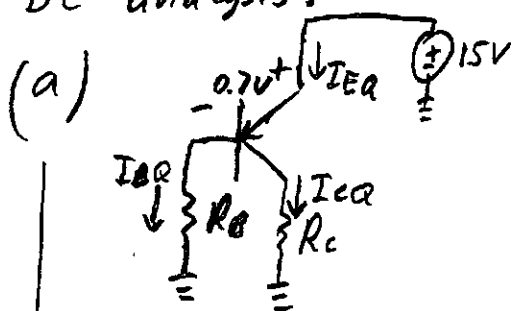

$$0 = -15V + 0.7V + I_{BQ} \cdot R_B$$


$$\hookrightarrow I_{BQ} = \frac{14.3V}{1 \times 10^6 \Omega} = 14.3 \mu A$$

$$I_{CQ} = \beta \cdot I_{BQ} = 1.43 mA$$

$$r_{\pi} = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{100 \cdot 26mV}{1.43mA} = 1.82 k\Omega$$

$$\frac{V_o}{V_{in}} = \frac{-\beta \cdot R_C}{r_{\pi}} = -258.5$$
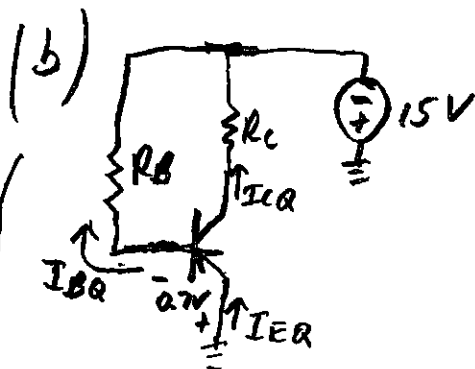
$$\frac{V_o}{V_{hum}} = \frac{\beta R_C}{r_{\pi}} = 258.5$$



$$0 = 0.7V + I_{BQ} \cdot R_B - 15V$$

$$\hookrightarrow I_{BQ} = \frac{14.3V}{R_B} = 14.3 \mu A$$

$$I_{CQ} = \beta \cdot I_{BQ} = 1.43 mA$$

$$r_{\pi} = \frac{\beta \cdot V_T}{I_{CQ}} = 1.82 k\Omega$$


$$\frac{V_o}{V_{in}} = \frac{-\beta \cdot R_C}{r_{\pi}} = -258.5$$

$$\frac{V_o}{V_{hum}} = 1$$

Circuit (b) is better because it has a lower gain from V_{hum} to V_o , while having the same gain from V_{in} to V_o .

Problem 4

a)

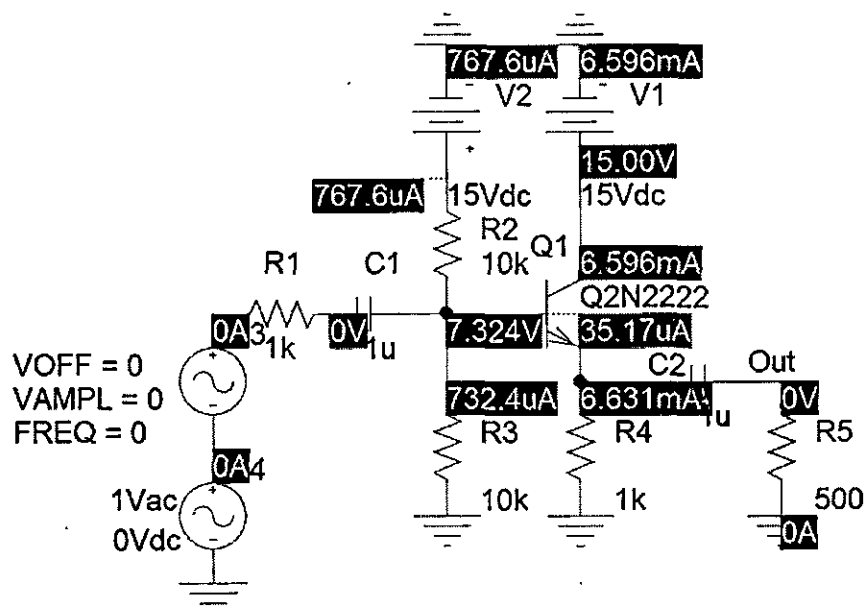

**** OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C

**** BIPOLAR JUNCTION TRANSISTORS

NAME	Q_Q1
MODEL	Q2N2222
IB	3.52E-05
IC	6.60E-03
VBE	6.93E-01
VBC	-7.68E+00
VCE	8.37E+00
BETADC	1.88E+02
GM	2.50E-01
RPI	7.96E+02
RX	1.00E+01
RO	1.24E+04
CBE	1.40E-10
CBC	3.20E-12
CJS	0.00E+00
BETAAC	1.99E+02
CBX/CBX2	0.00E+00
FI/FT2	2.77E+08


$$R'_L = R_L // R_E = 333 \Omega$$

$$A_v = \frac{R'_L (\beta + 1)}{r_{\pi} + R'_L (\beta + 1)} = 0.988 V/V$$


7

b)
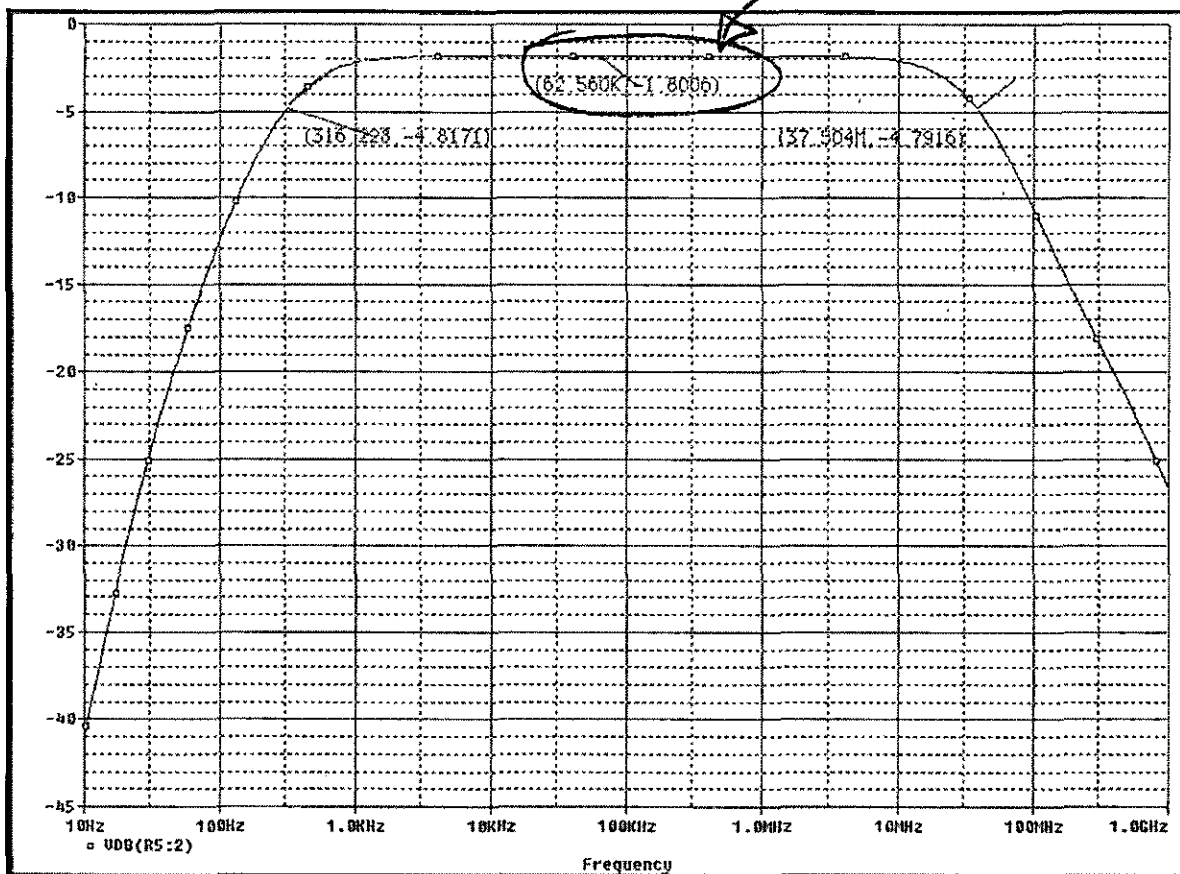
$$-1.8006 \text{ dB} = 0.81277 \text{ V/V}$$



c)

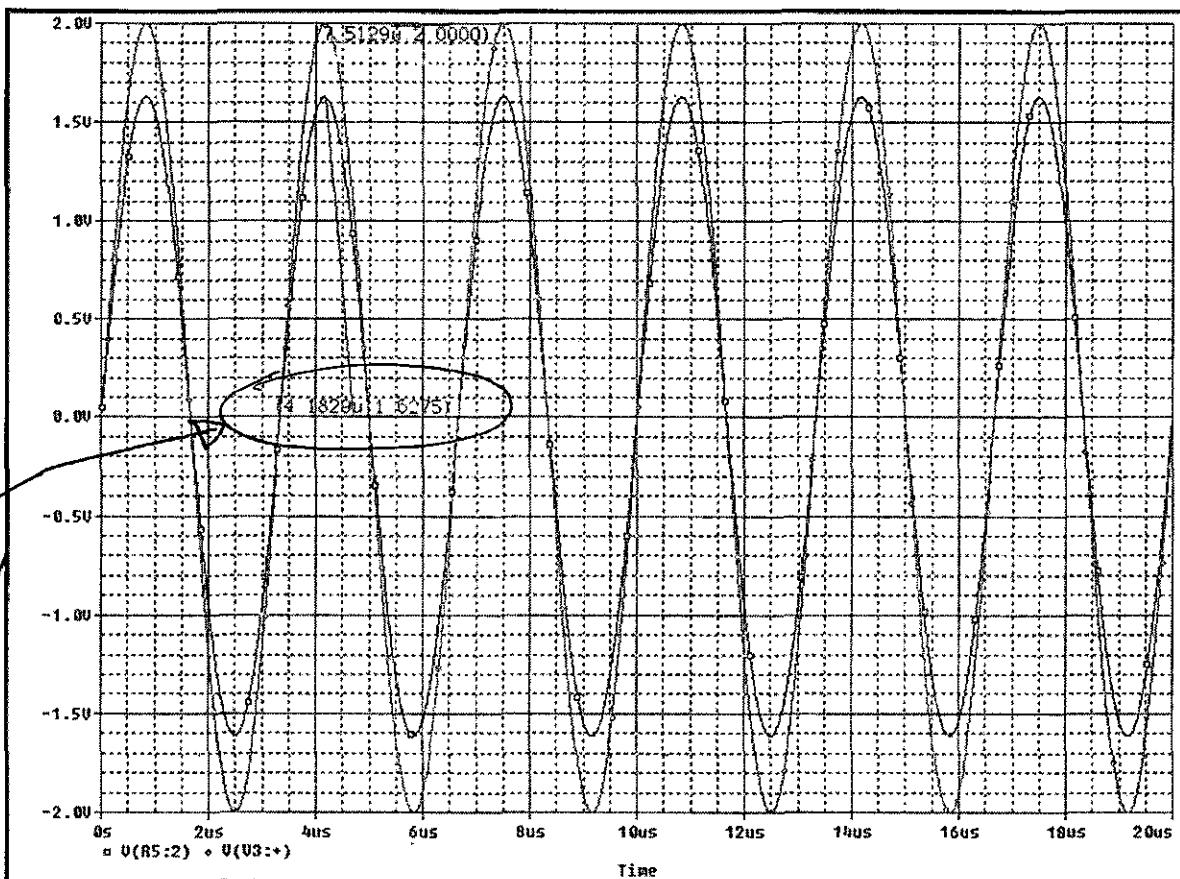


$$g_{ain} = \frac{1.62}{2} = 0.81 \text{ V/V}$$

it agrees with Part B

8

d)

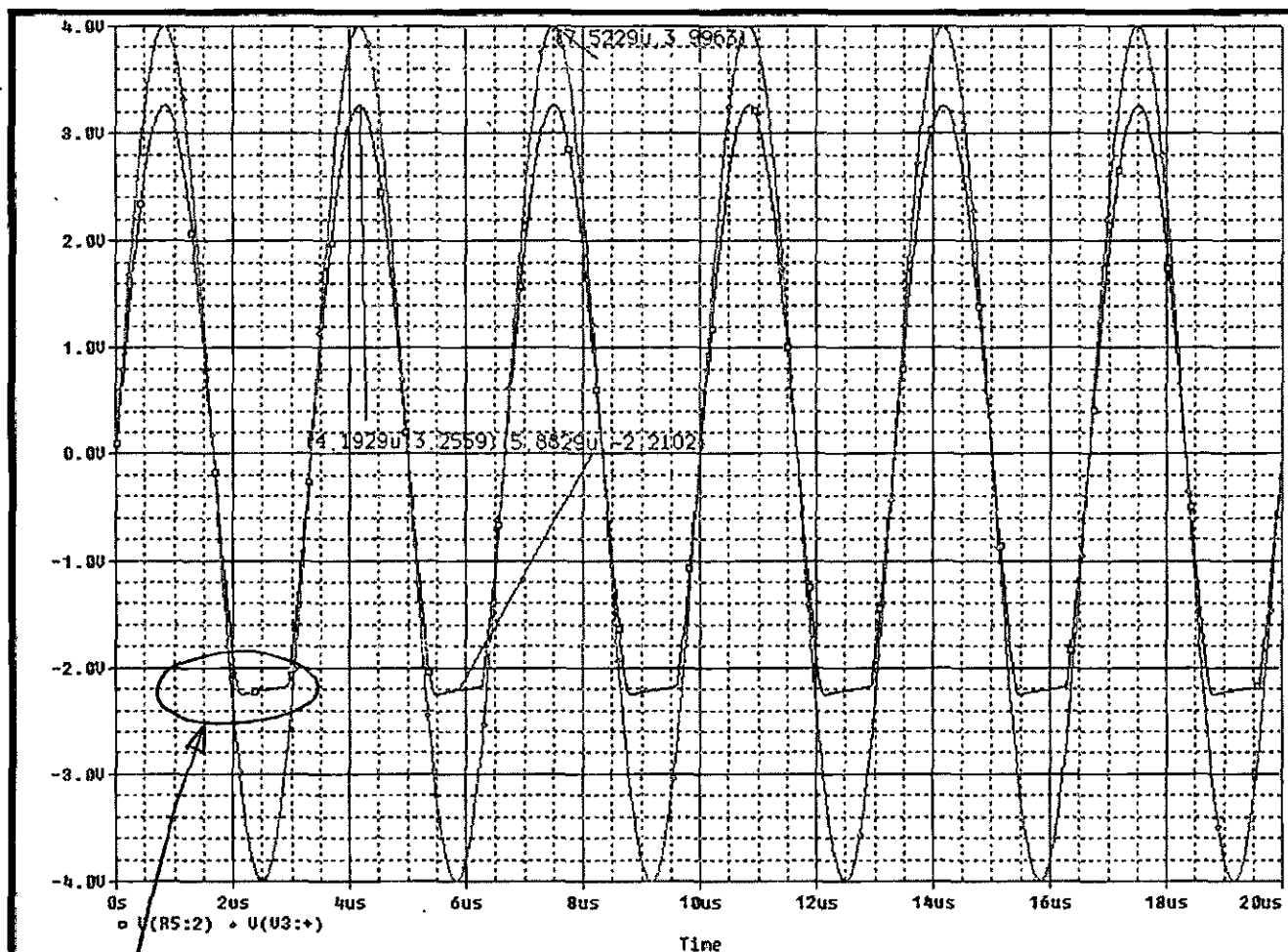

distortion

happens due to limiting the currents in the load resistance (R_4) leading to decrease in gain.