

Problem 1

Part (a), (b), (c).

Small signal analysis "midband Freq".

$\frac{V_o}{V_{in}}$

$$V_o = -\beta i_b (R_L \parallel R_C)$$

$$V_{in} = i_b r_{\pi} + i_b (\beta + 1) R_E$$

$$i_b (r_{\pi} + (\beta + 1) R_E) = V_{in}$$

$$i_b = \frac{V_{in}}{r_{\pi} + (\beta + 1) R_E}$$


$$V_o = \frac{-\beta (R_L \parallel R_C) V_{in}}{r_{\pi} + (\beta + 1) R_E}$$

$$\therefore \frac{V_o}{V_{in}} = \frac{-\beta (R_L \parallel R_C)}{r_{\pi} + (\beta + 1) R_E}$$


$$\frac{V_o}{V_s} = \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_s}$$

$$\frac{V_{in}}{V_s} = \frac{R_{in}}{R_{in} + R_s}$$
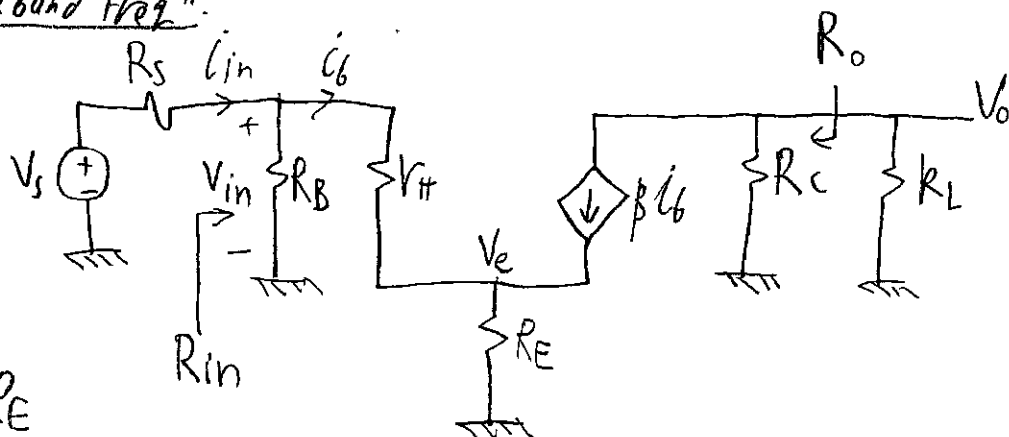
$$\frac{V_o}{V_s} = \frac{-\beta (R_L \parallel R_C)}{r_{\pi} + (\beta + 1) R_E} \times \frac{R_{in}}{R_{in} + R_s}$$



R_{in}

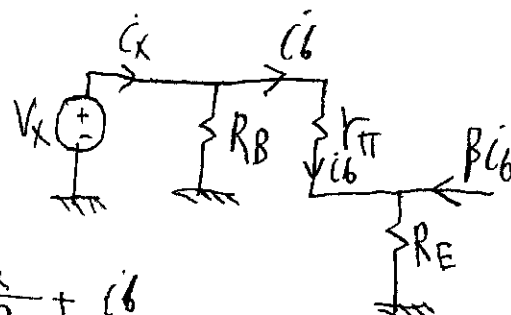

$$i_x = \frac{V_x}{R_B} + i_b$$


$$V_x = i_b r_{\pi} + i_b (\beta + 1) R_E$$

$$i_b = \frac{V_x}{r_{\pi} + (\beta + 1) R_E}$$

$$\therefore i_x = \frac{V_x}{R_B} + \frac{V_x}{r_{\pi} + (\beta + 1) R_E}$$

$$\therefore \frac{V_x}{i_x} = R_{in} = \frac{R_B (r_{\pi} + (\beta + 1) R_E)}{r_{\pi} + R_B + (\beta + 1) R_E}$$

R_{out}

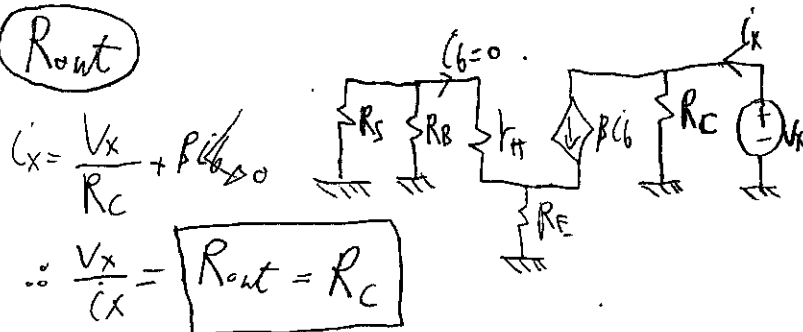

$$i_x = \frac{V_x}{R_C} + \beta i_b$$

$$\therefore \frac{V_x}{i_x} = R_{out} = R_C$$

P. 2

Problem 1 Cont.

DC Analysis:

$$15 - I_B R_B - 0.7 - (\beta + 1) I_B R_E = 0$$

$$14.3 = \frac{I_C}{\beta} (R_B + (\beta + 1) R_E)$$

$$I_C = \frac{14.3 \beta}{R_B + (\beta + 1) R_E} \leq 8 \times 10^{-3}$$

$$\therefore R_B + 201 R_E \geq 357.5 \text{ k}\Omega \quad (1)$$

$$|A_{VS}| = \left| \frac{V_o}{V_s} \right| = |20|$$

$$\frac{V_o}{V_i} \times \frac{V_i}{V_s} = 20$$

$$\frac{\beta (R_C \parallel R_L)}{r_{\pi} + (\beta + 1) R_E} \times \frac{5000}{5000 + 500} = 20$$

$$\therefore \frac{\beta (R_C \parallel R_L)}{r_{\pi} + (\beta + 1) R_E} \geq 22 \quad (2)$$

$$r_{\pi} = \frac{\beta V_T}{I_C} \rightarrow I_C = \frac{\beta V_T}{r_{\pi}} \leq 8 \times 10^{-3}$$

$$\therefore r_{\pi} \geq 650 \Omega \quad (3)$$

$$R_{in} = \frac{((\beta + 1) R_E + r_{\pi}) R_B}{r_{\pi} + R_B + (\beta + 1) R_E} \geq 5000 \quad (4)$$

$$\text{Let } R_C = 1000 \Omega$$

$$\therefore R_C \parallel R_L = 937.5 \Omega$$

$\therefore$ From (2)

$$r_{\pi} + 201 R_E \leq 8.5227 \text{ k}\Omega$$

$$\text{Let } r_{\pi} = 700 \Omega \rightarrow \text{From (3)}$$

$$\therefore R_E \leq 39 \Omega \rightarrow \text{Let } R_E = 37.5 \Omega$$

From (1)

$$R_B + 201 R_E \geq 357.5 \text{ k}\Omega$$

$$\therefore R_B \geq 349 \text{ k}\Omega \rightarrow \text{Let } R_B = 350 \text{ k}\Omega$$


check R_i from (4)

$$R_i = 8.04 \text{ k}\Omega \text{ (satisfied)}$$

P.3

Problem 1

Part d

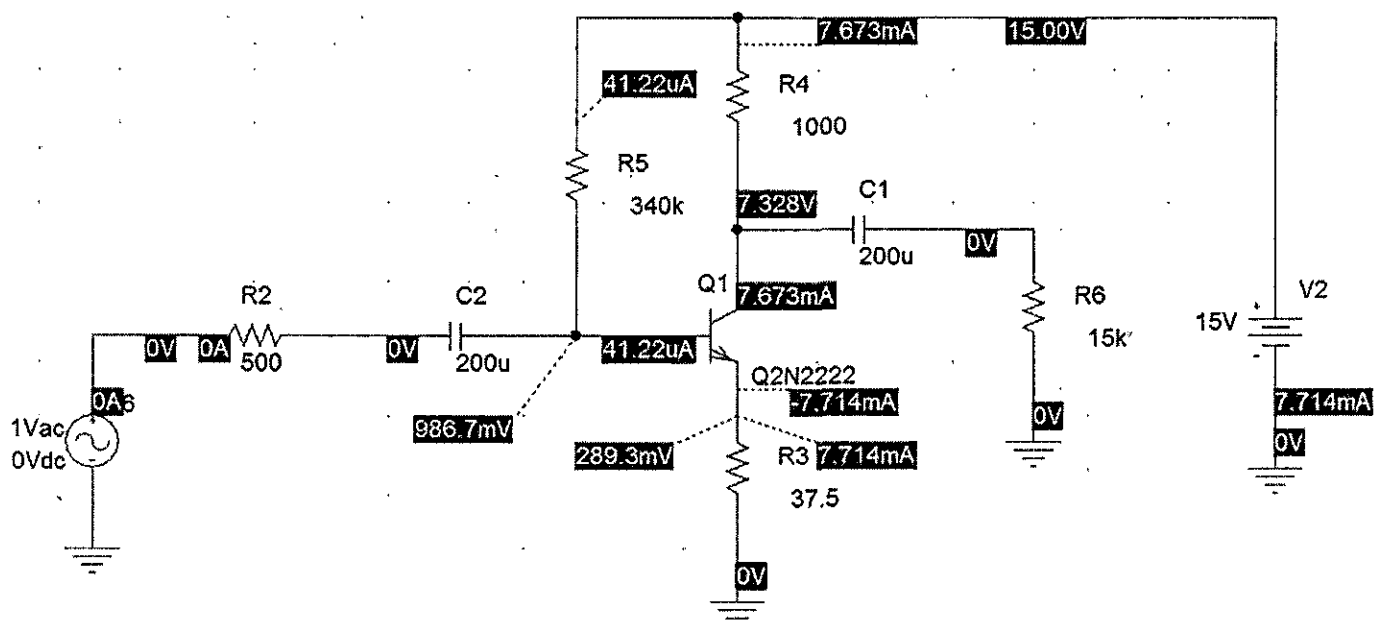


NAME	Q_Q1
MODEL	Q2N2222
IB	4.12E-05
IC	7.67E-03
VBE	6.97E-01
VBC	-6.34E+00
VCE	7.04E+00
BETADC	1.86E+02
GM	2.90E-01
RPI	6.77E+02
RX	1.00E+01
RO	1.05E+04
CBE	1.57E-10
CBC	3.39E-12
CJS	0.00E+00
BETAC	1.96E+02
CBX/CBX2	0.00E+00
FT/FT2	2.87E+08

(P. 4)

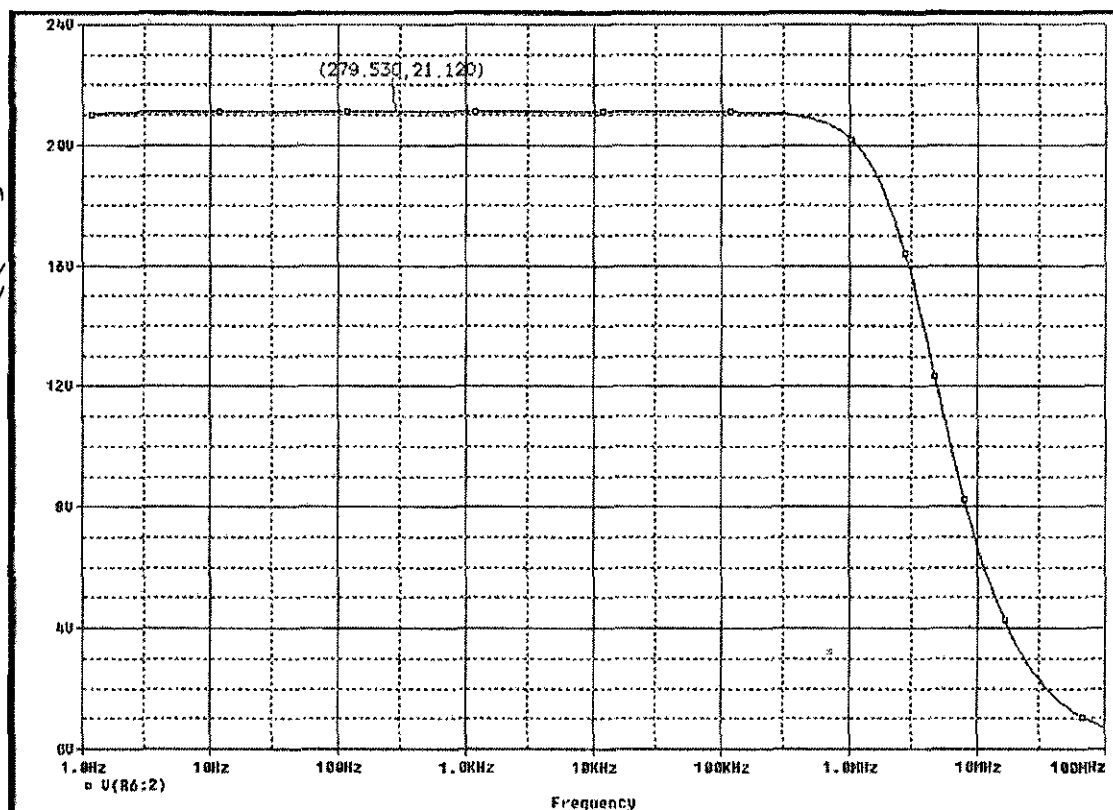
Part e

The A_{vs} from
AC simulation
is $21.12 \approx 20\%$



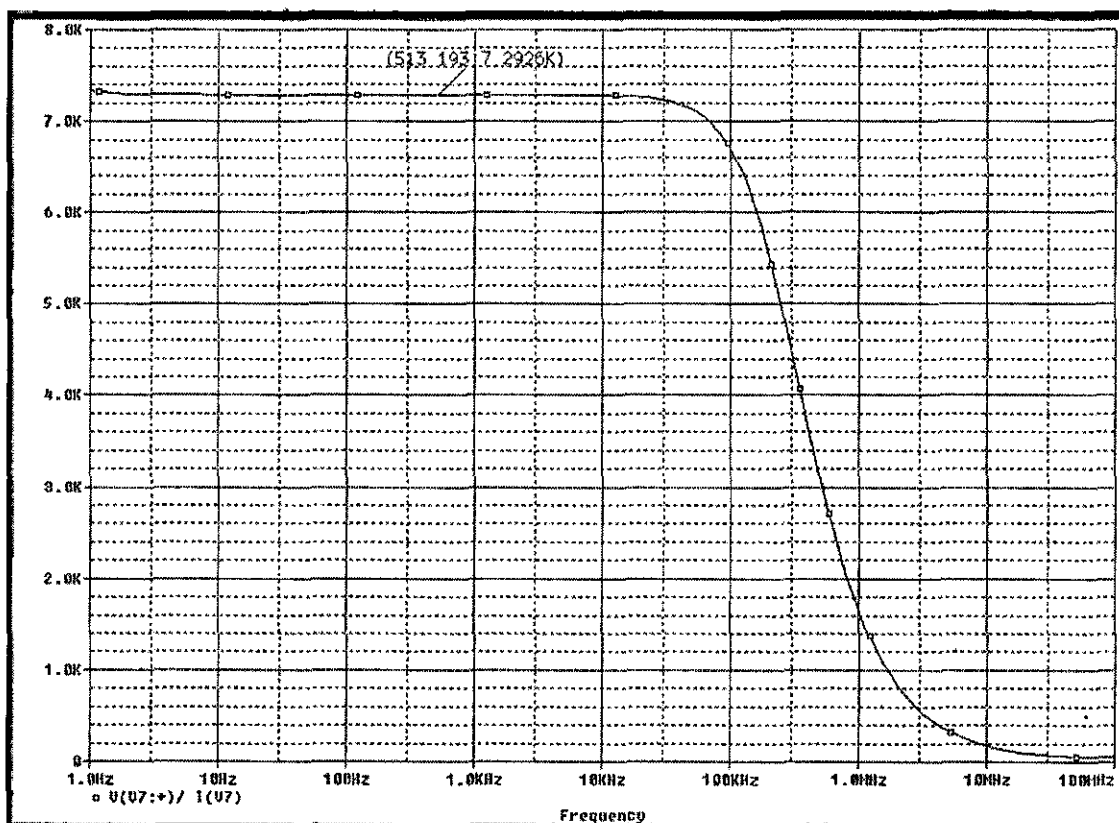Part f

R_{in} (Simulated)
= 7.2926K Ω
 R_{in} (calculated)
= 8.04K Ω
 $R_{in} < R_{in,calc}$




P.5

Part g


$$R_{out} \text{ (simulated)} = 986.566 \Omega$$

$$R_{out} \text{ (calculated)} = 937.5 \Omega$$

$$\therefore R_{sim} > R_{calc.}$$

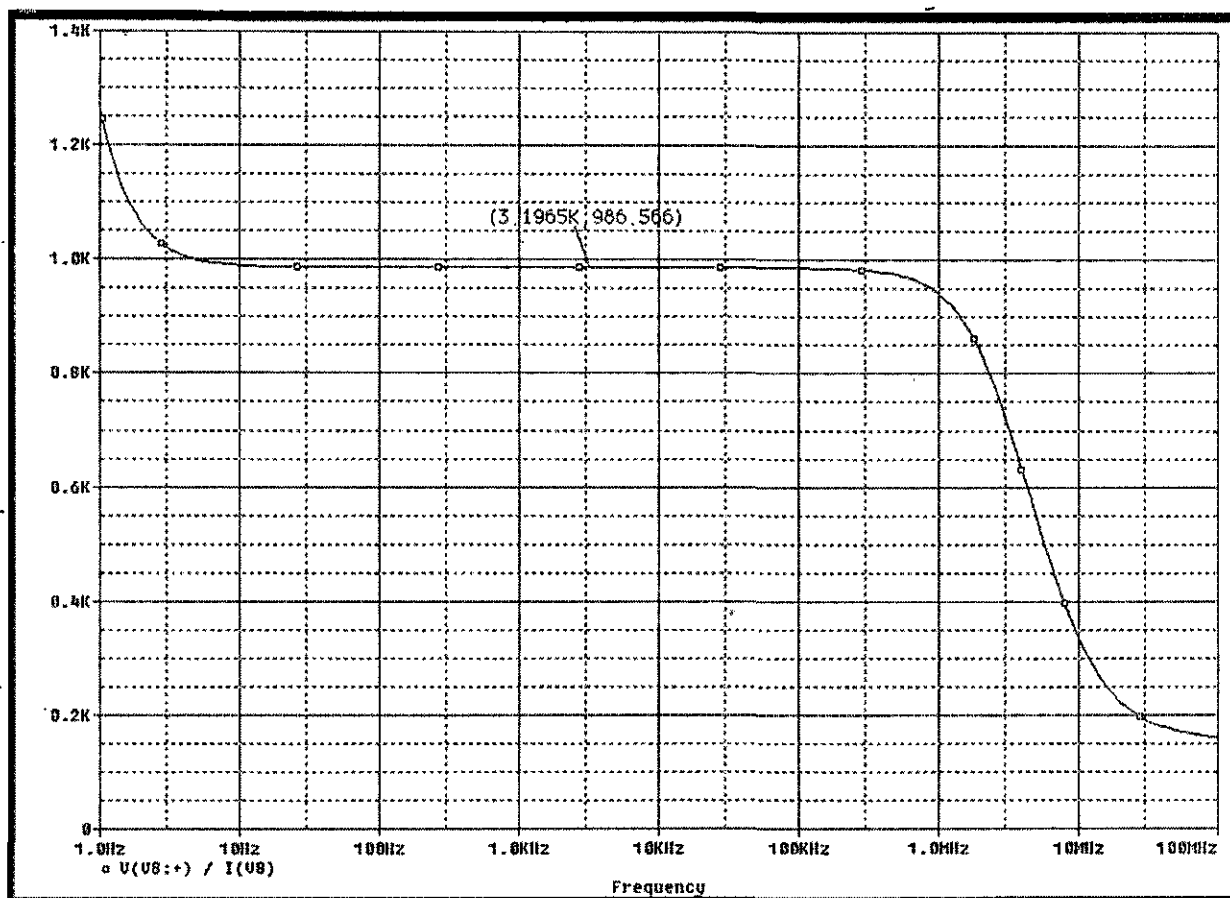

Part h

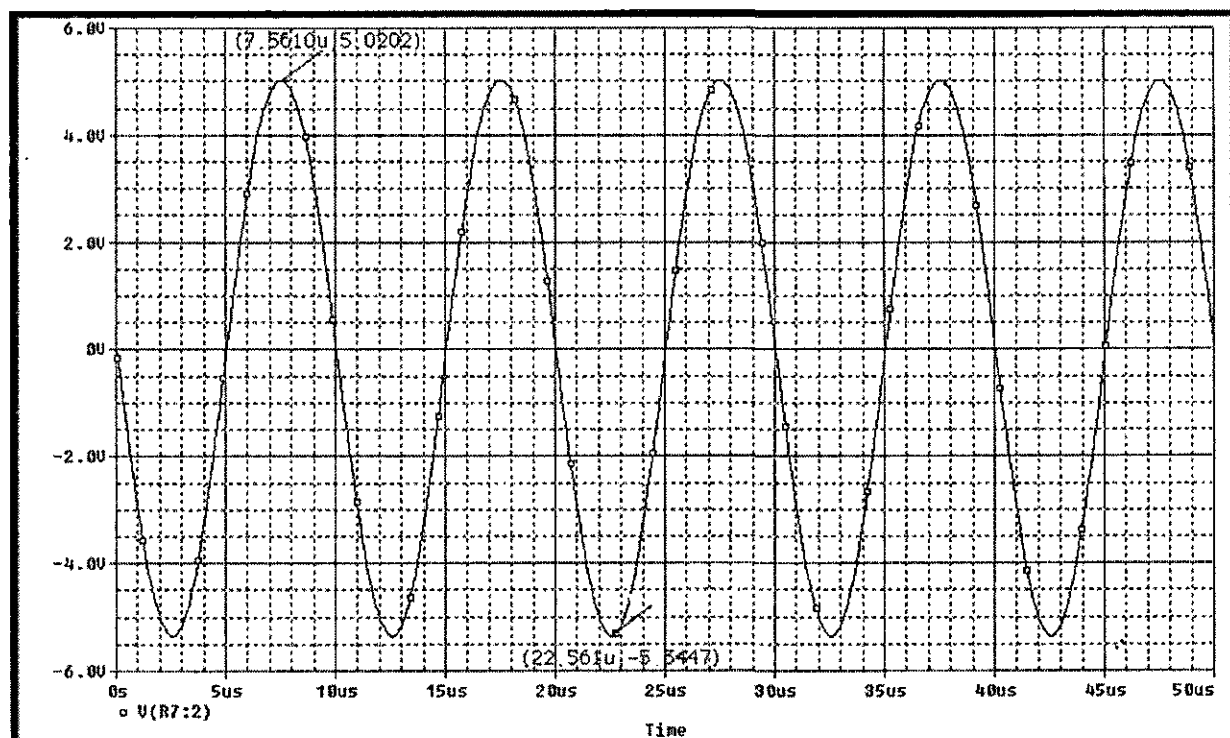

from simulation: $gain = \frac{5.0202 - (-5.3447)}{250mV \times 2} = 20.7298V/V$

P.6

Problem 2

$$V_{t0} = 1V, K_P = 50 \mu A/V^2, W = 50 \mu m, L = 5 \mu m$$

$$(\lambda = 0)$$

a) $V_{GS} = 4V, V_{DS} = 10V$

$$V_{GS} = 4V \geq 1V = V_{t0}$$

$$V_{GS} - V_{t0} = 4V - 1V = 3V \leq V_{DS} = 10V$$

The NMOS
is in
Saturation

$$K = \left(\frac{W}{L}\right) \cdot \left(\frac{K_P}{2}\right) = \left(\frac{50 \mu m}{5 \mu m}\right) \cdot \left(\frac{50 \mu A/V^2}{2}\right) = 250 \frac{\mu A}{V^2}$$

in saturation:
(with $\lambda = 0$) $I_D = K (V_{GS} - V_{t0})^2 = (250 \times 10^{-6} \frac{A}{V^2}) (4V - 1V)^2$

$$\boxed{I_D = 2.25 \text{ mA}}$$

b) $V_{GS} = 4V, V_{DS} = 2V$

$$V_{GS} = 4V \geq 1V = V_{t0}$$

$$V_{GS} - V_{t0} = 4V - 1V = 3V > 2V = V_{DS}$$

The NMOS
is in the
triode region

in triode:
(with $\lambda = 0$) $I_D = K \cdot [2 \cdot (V_{GS} - V_{t0}) \cdot V_{DS} - V_{DS}^2]$

$$I_D = (250 \times 10^{-6} \frac{A}{V^2}) \cdot [2 \cdot (4V - 1V) \cdot 2V - (2V)^2]$$

$$\boxed{I_D = 2 \text{ mA}}$$


c) $V_{GS} = 0V, V_{DS} = 10V$

$$V_{GS} = 0V < 1V = V_{t0} \rightarrow \text{The NMOS is in } \boxed{\text{cutoff.}}$$

$$\hookrightarrow \boxed{I_D = 0}$$

P. 7

Problem 3

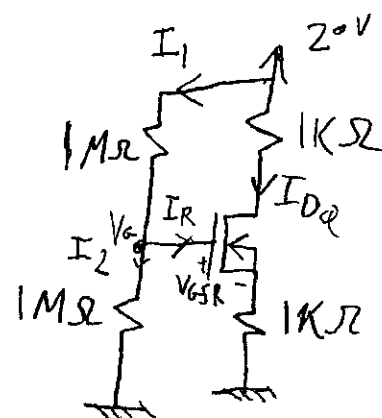

a) KVL: (Assume Saturation)
 $20 - I_1 \times 1M\Omega - I_2 \times 1M\Omega = 0$

$$I_2 + I_R = I_1, \quad I_R = 0$$

$$\therefore I_1 = I_2$$

$$\therefore I_1 = \frac{20}{2M} = 10\mu A$$

$$\therefore V_G = 20 - 10\mu A \times 1M\Omega = 10V$$

$$V_G - V_{GSR} - I_{DQ} \times 1K\Omega = 0$$

$$V_G - V_{GSR} - K(V_{GSR} - V_{t_0})^2(1 + \lambda V_{DS}) \times 1K\Omega = 0 \quad (1)$$

$$\therefore V_{GSR} = 6V \rightarrow I_{DQ} = K(V_{GSR} - V_{t_0})^2(1 + \lambda V_{DS}) = 4mA$$

$$V_{DS} = 20 - I_{DQ} \times 2K\Omega = 12V > V_{GSR} - V_{t_0} = 2V \rightarrow \therefore \text{Saturation}$$

b) Resolving (1) $\rightarrow V_{GSR} = 3.76556V$

$$\therefore I_{DQ} = K(V_{GSR} - V_{t_0})^2(1 + \lambda V_{DS}) = 6.23444mA$$

$$V_{DS} = 20 - I_{DQ} \times 2K\Omega = 7.5343V > V_{GSR} - V_{t_0} = 1.76556V$$

$\rightarrow \therefore \text{Saturation}$