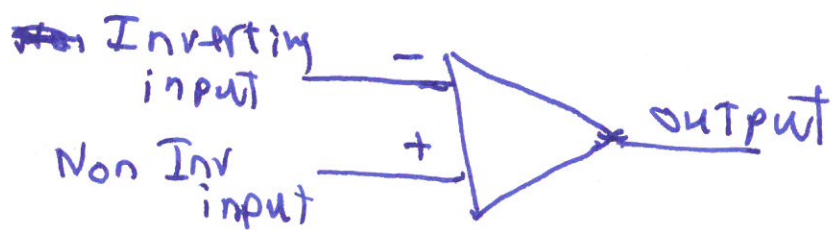


W e / 14 Sep 2016


(15)



Gain is  $\infty$

$$i_+ = i_- = 0$$

Transimpedance Amp  $i_{in}$   $V_{out}$

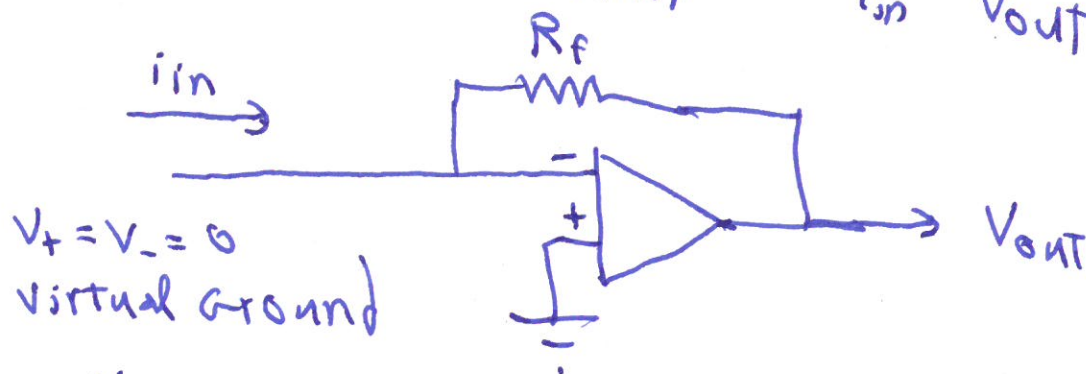


$$V_{out} = -i_{in} R_f$$

$$V_- = V_+ = 0$$

$V_{in} = 0$  for any current;  $R_{in} = 0$

$$R_{out} = 0$$

Voltage Amplifier

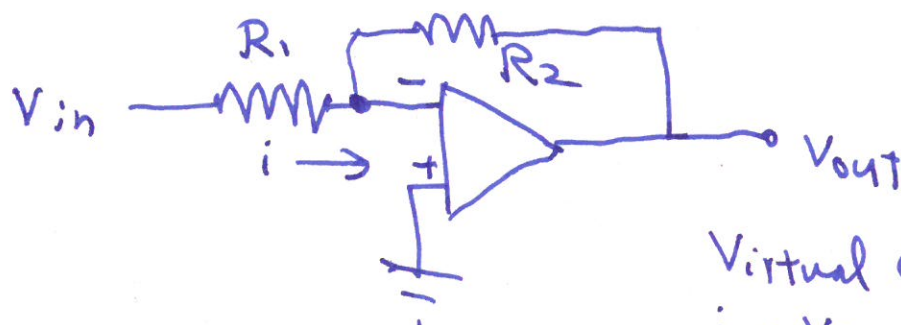

Virtual Ground

$$i = \frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2}$$

$$V_{out} = -V_{in} \frac{R_2}{R_1}$$

$$A_v = -R_2 / R_1$$

(16)

$$A_v = - \frac{R_2}{R_1}$$


Most Common Amplifier

$$R_{in} = R_1$$


~ Not so good

$$R_{out} \approx 0$$

Good for Voltage out

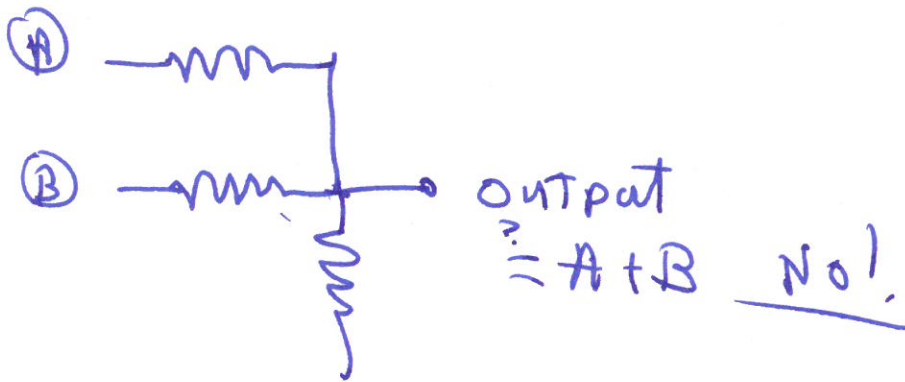

Summing Junction

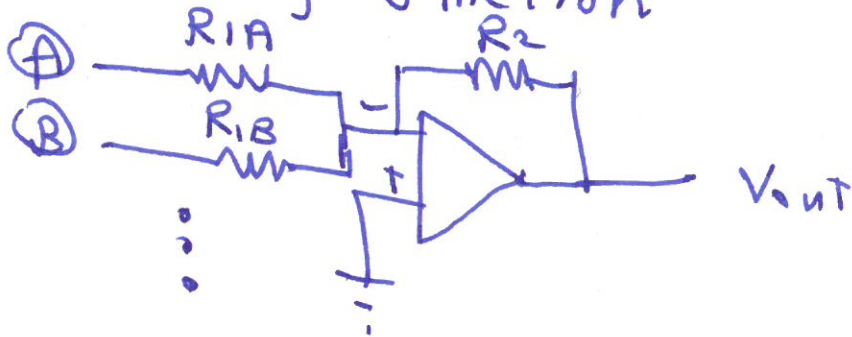


$$V_{out} = - \frac{R_2}{R_{1A}} V_A - \frac{R_2}{R_{1B}} V_B \dots$$

# Exercise

Design A D-A converter  
input 0 or +5 volts on each  
Channel

|         | (B) | (A) |                              |
|---------|-----|-----|------------------------------|
|         | ↓   | ↓   |                              |
| 0 0 0 1 |     |     | → $V_{out} = 1 \text{ Volt}$ |
| 0 0 1 0 |     |     | → 2                          |
| 0 0 1 1 |     |     | → 3                          |
| ⋮       |     |     | ⋮                            |

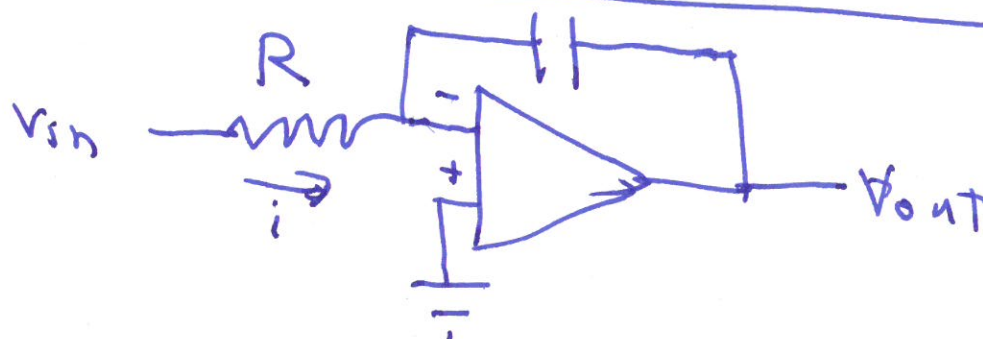


$$i = \frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$

$$V_{out}(t) = V_{out}(0) + \frac{\int_0^t V_{in}(t') dt'}{RC}$$



## Low Pass filter

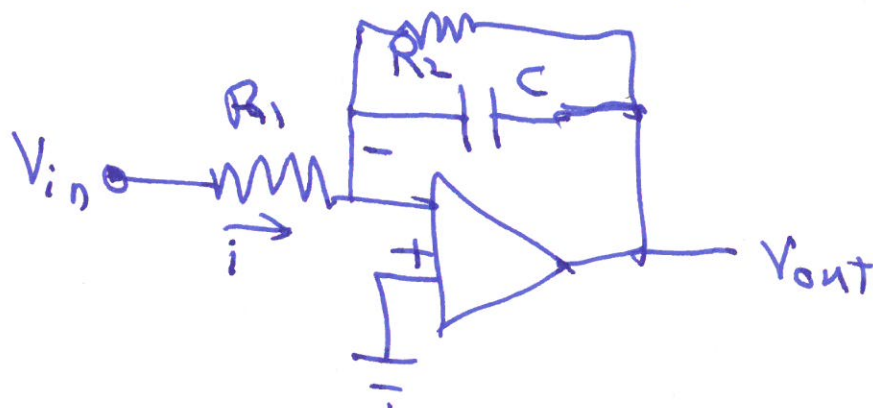

Frequency Domain

$$i = \frac{V_{in}}{R_1} = \frac{-V_{out}}{R_2 \parallel \frac{1}{j\omega C}}$$

$$V_{out} = -V_{in}$$

$$\frac{R_2 \parallel \frac{1}{j\omega C}}{R_1} = \frac{-V_{in} R_2 / j\omega C}{R_1 (R_2 + \frac{1}{j\omega C})}$$

$$A_v = \frac{V_{out}}{V_{in}} =$$

$$\frac{-R_2}{R_1 R_2 j\omega C + R_1}$$


Special Cases

$$C \rightarrow 0$$

$$A_v = -\frac{R_2}{R_1}$$

$$R_2 \rightarrow \infty$$


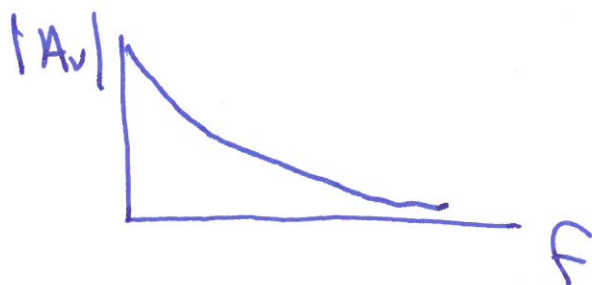
$$\frac{V_{out}}{V_{in}} = -\frac{1}{R_1 j\omega C}$$



$$\int \cos \omega t = \frac{1}{\omega} \sin \omega t$$

General case
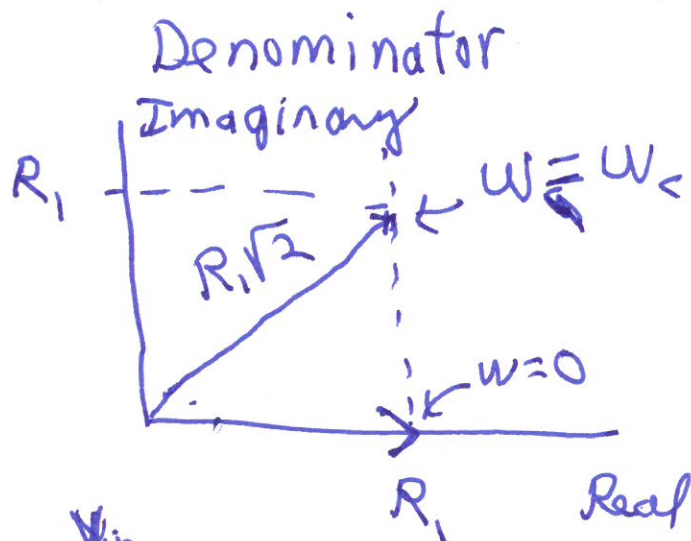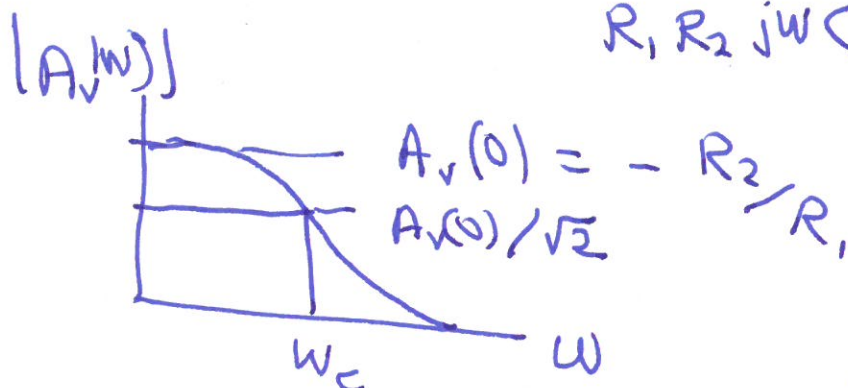
$$A_v(\omega) = - \frac{R_2}{R_1 R_2 j\omega C + R_1}$$



$$R_1 R_2 \omega_c = R_1$$

$$\omega_c = \frac{1}{R_2 C}$$

$$f_c = \frac{1}{2\pi R_2 C}$$

