

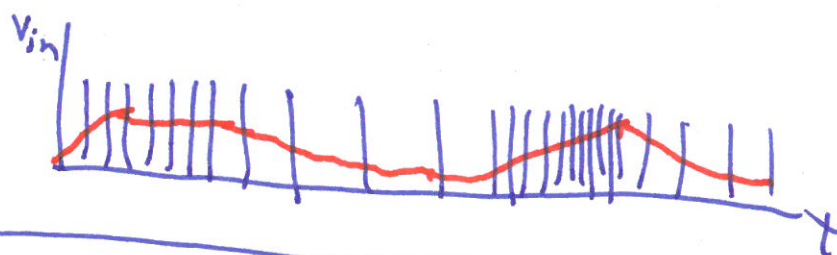


Thu 15 Sep 2016 (week 2)

20

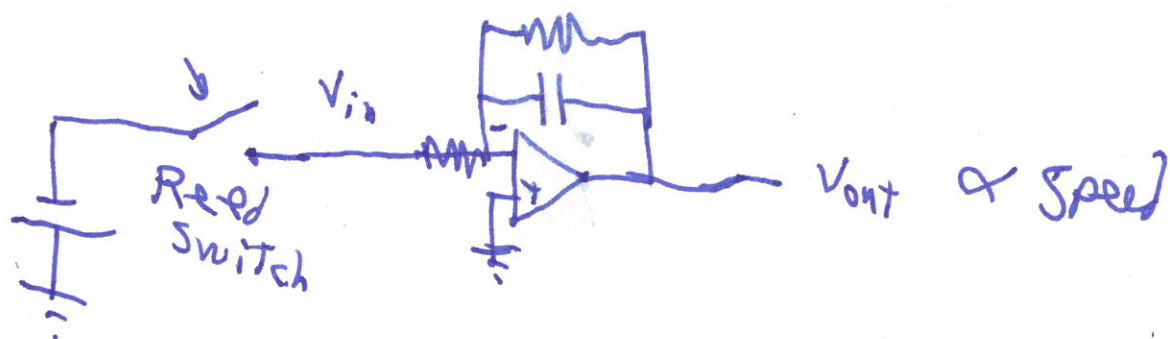

Buffer Amp

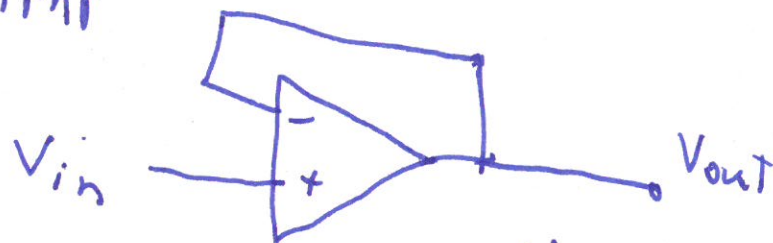


$$A_v = 1$$

$$R_{in} \rightarrow \infty$$

$$V_{out} = V_{in}$$

$$R_{out} \rightarrow 0$$

High impedance input





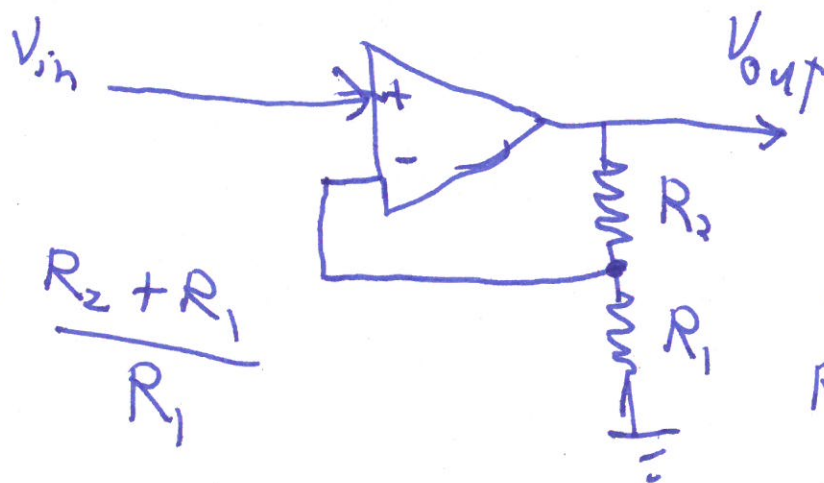


$$A_v = \frac{R_2 + R_1}{R_1}$$

$$R_{in} \rightarrow \infty$$

$$R_{out} \rightarrow 0$$

(21)

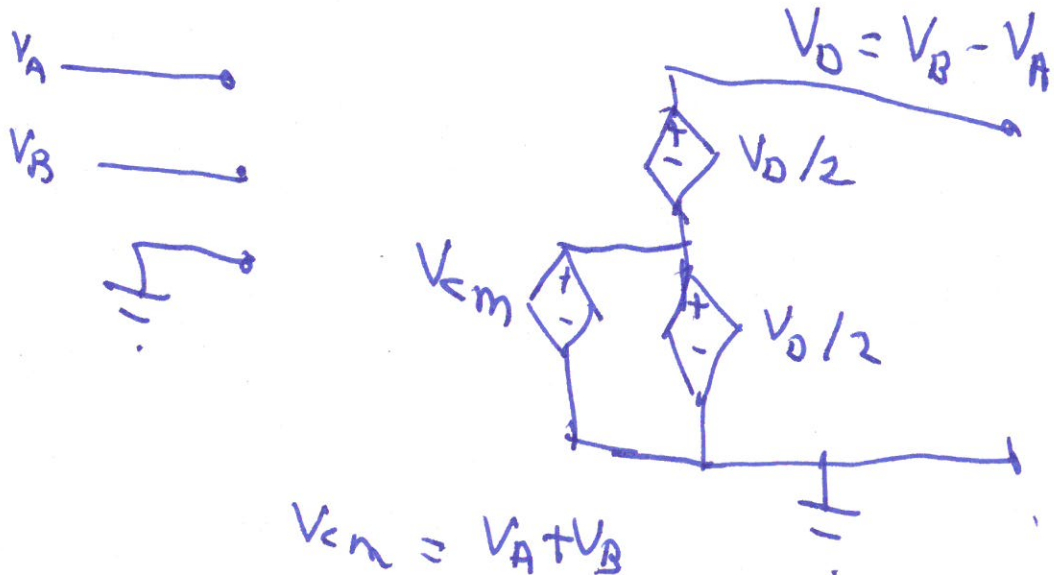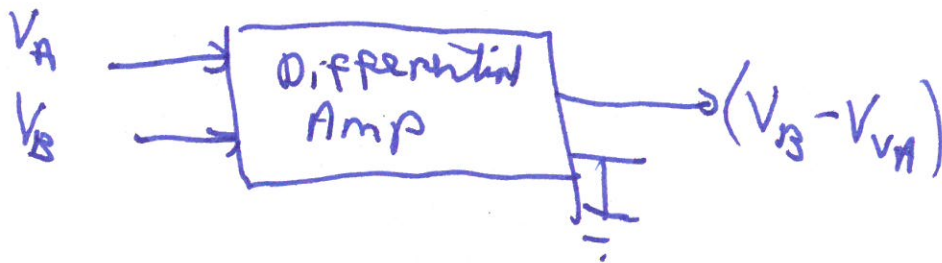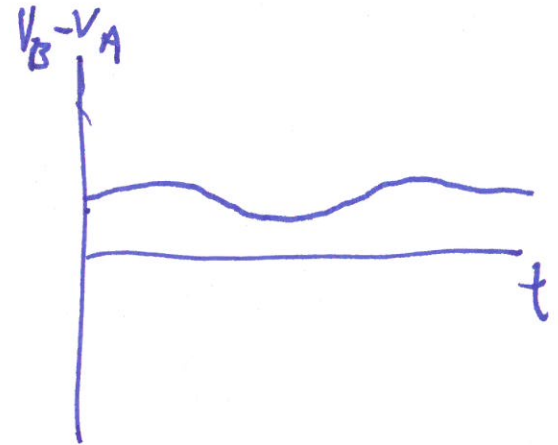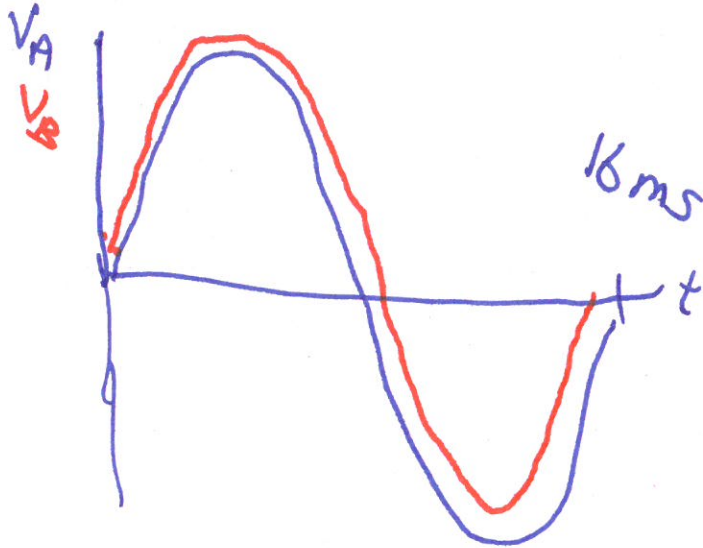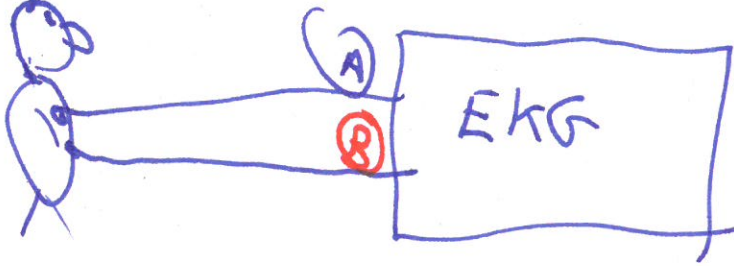

$$V_{cm} = \frac{V_A + V_B}{2}$$

$$V_{cm(in)} = 100V$$

$$V_{D(in)} \approx 1mV$$


$$A_{vcm} \leq 10^{-4} \rightarrow V_{cm(out)} = 10mV$$

$$A_{vD} = 1000 \rightarrow V_{D(out)} = 1Volt$$

Common mode Rejection Ratio

$$CMRR = \left| \frac{A_{vD}}{A_{vcm}} \right|^2$$
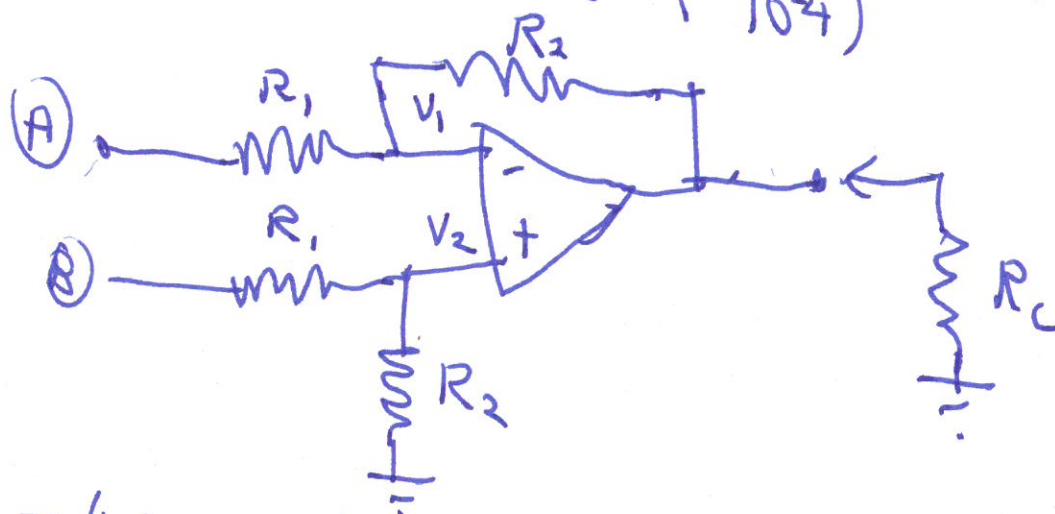
$$CMRR = 20 \log_{10} \left(\frac{1000}{10^{-4}} \right) = 140dB$$



$$V_1 = (V_{out} - V_A) \times \frac{R_1}{R_1 + R_2} + V_A$$

$$= V_A \frac{R_2}{R_1 + R_2} + V_{out} \frac{R_1}{R_1 + R_2}$$

(23)

$$V_{2E} = V_B \frac{R_2}{R_1 + R_2}$$

$$V_{out} \frac{R}{R_1 + R_2} + V_A \frac{R_2}{R_1 + R_2} = V_2 \frac{R_2}{R_1 + R_2}$$

$$V_{out} = \frac{V_B R_2 - V_A R_2}{R_1}$$

$$V_{out} = \frac{R_2}{R_1} (V_B - V_A) \quad \text{Good Diff Amp.}$$

Transfer function

Phasor Notation

 $A_v(f)$

Phasors

$$A_v = \frac{V_{out}}{V_{in}} \quad (\text{Complex})$$

$$V_i = 0.1 \text{ V } \cos(2000\pi t - 30^\circ)$$


radians deg

$$V_{in} = 0.1 \text{ V } \angle -30^\circ \quad \text{or} \quad 0.1 e^{j\pi/6}$$



$$V_{out} = 10 \text{ V } \angle 15^\circ \quad \text{or} \quad 10 e^{j\pi/12}$$

$$A_v = 100 \angle 45^\circ \quad \text{or} \quad 100 e^{j\pi/4}$$


$$A_v = 20 \text{ dB at } 45^\circ$$

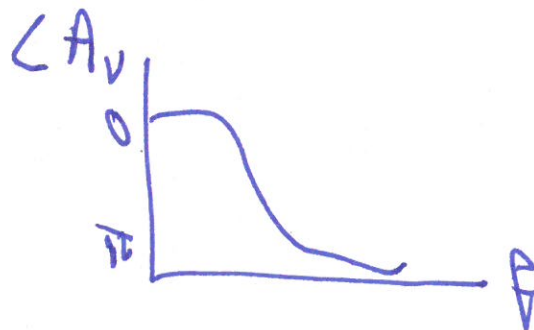

Example

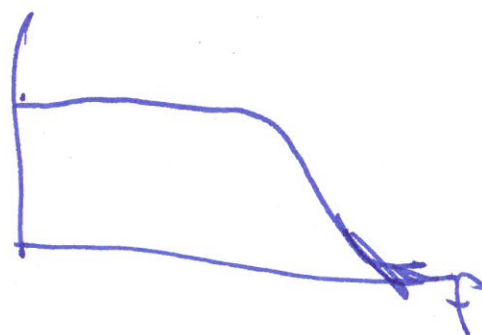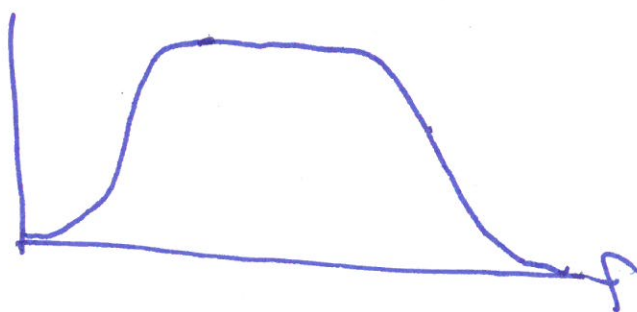

Resistors

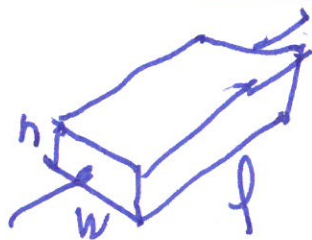

$$R = \rho \frac{l}{hw}$$

↑ resistivity

typical resistors few $k\Omega$