

19 Sep 2016


25

Imperfections

Linear ones: gain, Bandwidth, Resistance

Non Linear: Saturation.

DC: Bias currents + Voltages.

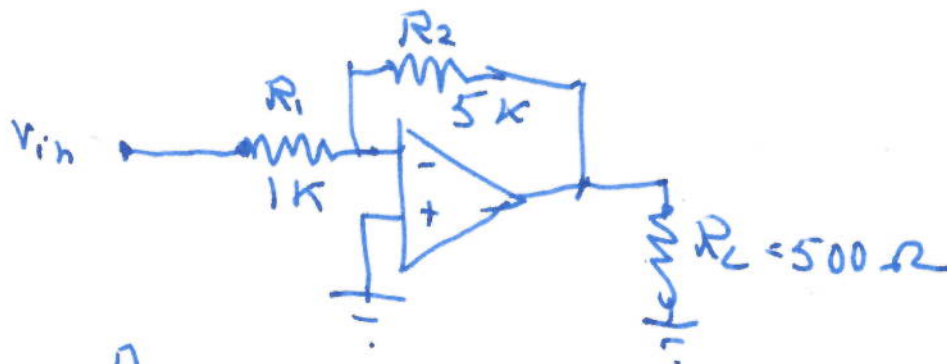

$$A_v = -5$$

$$\left. \begin{array}{l} \textcircled{1} \quad V_{out} = A_v V_{in} = -5 V_{in} \\ \quad \quad V_{out} = V_{supply} - = -12V \\ \textcircled{2} \quad V_{out} = V_{supply} + = +12V \end{array} \right\} \text{Piecewise Linear Solution}$$

$$\textcircled{1} \quad V_{out} = A_v V_{in}$$

$$-12V < V_{out} < +12V$$

$$V_- = V_+ = 0$$

Real ground

$$\textcircled{2} \quad V_{out} = 12V$$

$$V_+ = 0$$

$$V_- = V_{in} + (V_{out} - V_{in}) \frac{R_1}{R_1 + R_2}$$


$$V_- = V_{supply} \frac{R_1}{R_1 + R_2} + V_{in} \frac{R_2}{R_1 + R_2}$$

$V_- < 0$ (test)

③ $V_- = V_{supply} \frac{R_1}{R_1 + R_2} + V_{in} \frac{R_2}{R_1 + R_2}$

$V_- > 0$ (test)


Transfer Characteristic

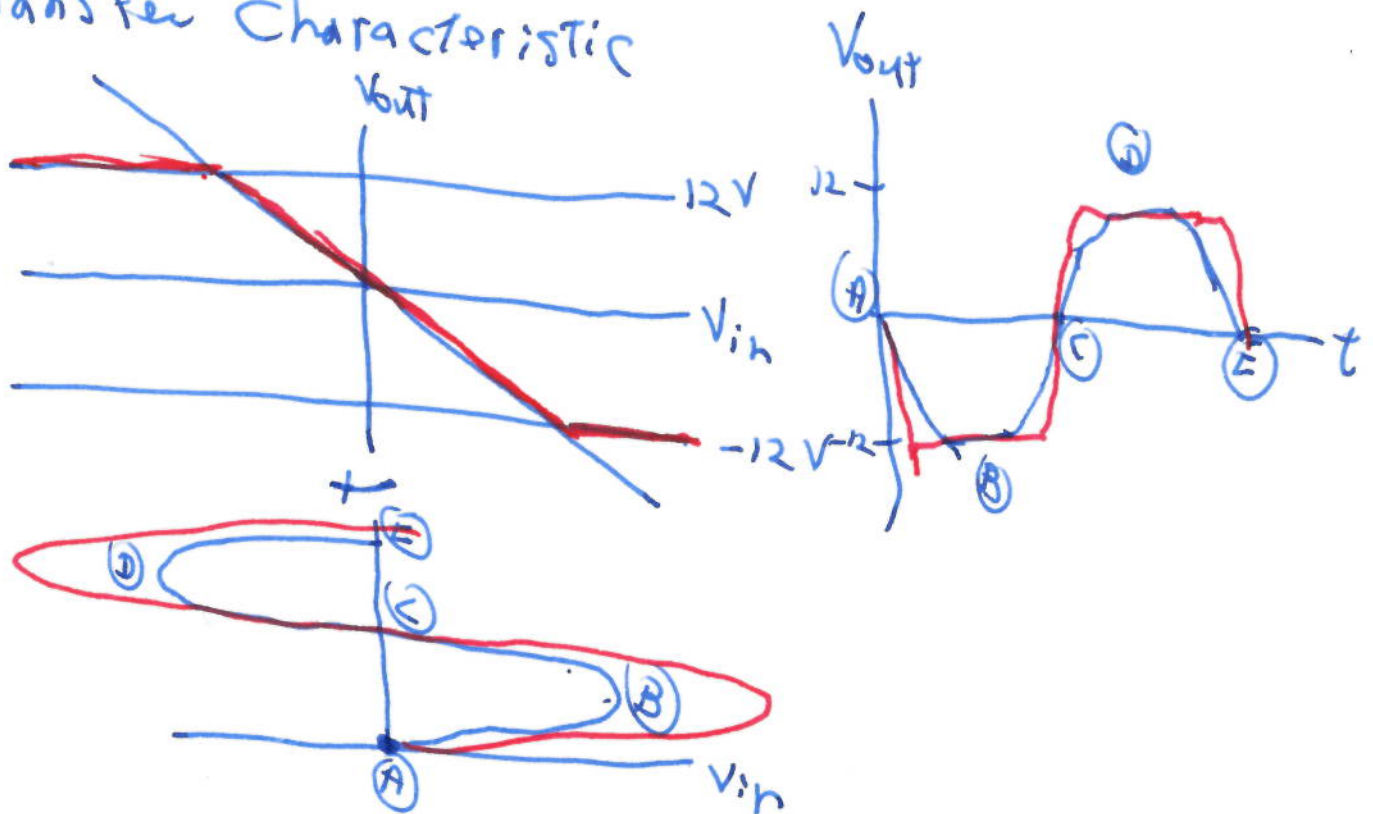

or current limit.

unipolar PS

(22)

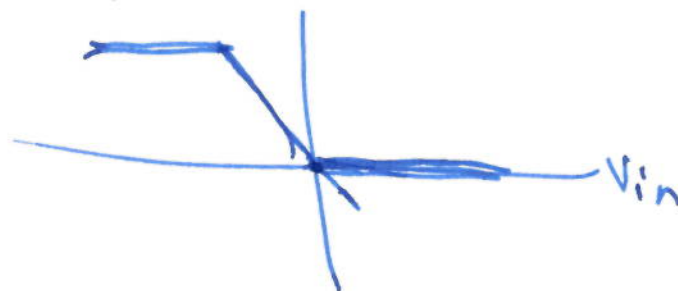


Solution: Capacitive coupling.

Open-loop Gain

Real OpAmp



A_{OL} large but finite
eg 10^5

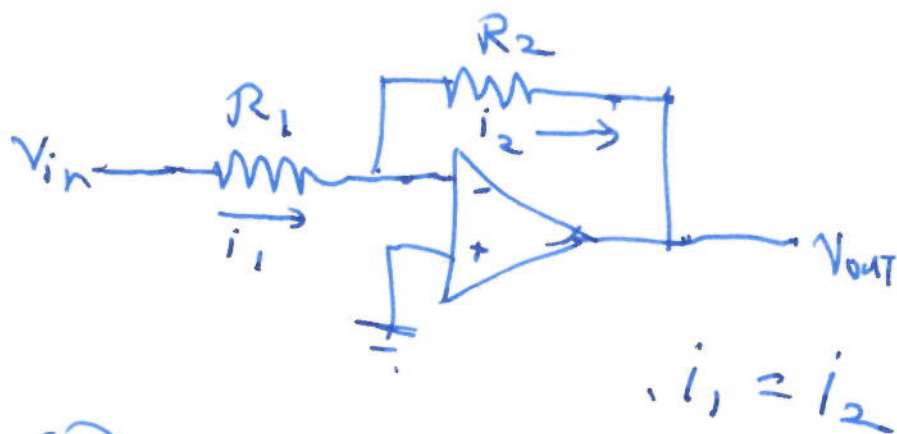

(A) $i_1 = (V_{in} - V_-) / R_1$

(B) $i_2 = (V_- - V_{out}) / R_2$

Not saturated; $V_{out} = A_{OL} (V_+ - V_-)$

(A)
$$\frac{V_{in} + \frac{V_{out}}{A_{OL}}}{R_1} =$$

(B)
$$-\frac{\frac{V_{out}}{A_{OL}} - V_{out}}{R_2}$$

Real ground

$$\frac{V_{out}}{A_{OL} R_1} + \frac{V_{out}}{A_{OL} R_2} + \frac{V_{out}}{R_2} = - \frac{V_{in}}{R_1}$$

$$A_v = \frac{V_{out}}{V_{in}} = -1$$

$$= - \frac{R_2}{R_1} \frac{A_{OL}}{\frac{R_2}{R_1} + 1 + A_{OL}}$$