

21 Sep 2016

(29)

Yesterday:

$$A_v = - \frac{R_2}{R_1} \frac{A_{OL}}{\frac{R_2}{R_1} + 1 + A_{OL}}$$

Target gain = $-\frac{R_2}{R_1}$

if $A_{OL} \rightarrow \infty$

$$A_v = -\frac{R_2}{R_1}$$

if $A_v \text{ target} \rightarrow \infty$

$$A_v = A_{OL}$$

Examples:

$$A_{OL} = 10^5$$


100dB

$$10^3$$

60dB

$$V_- = - \frac{V_{out}}{A_{OL}}$$


Remember LPF

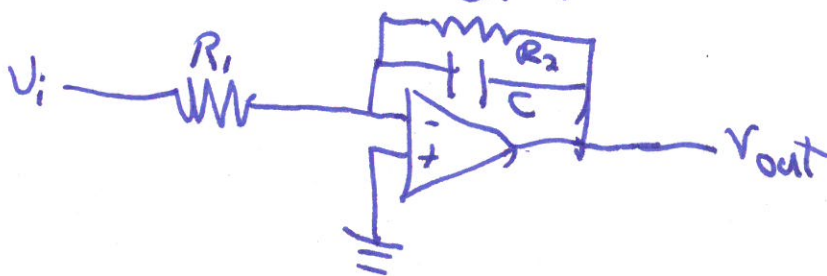

$$A_v = - \frac{R_2}{R_1 R_2 j\omega C + R_1}$$

$$= - \frac{R_2}{R_1} \frac{1}{1 + R_2 j\omega C}$$

Denominator

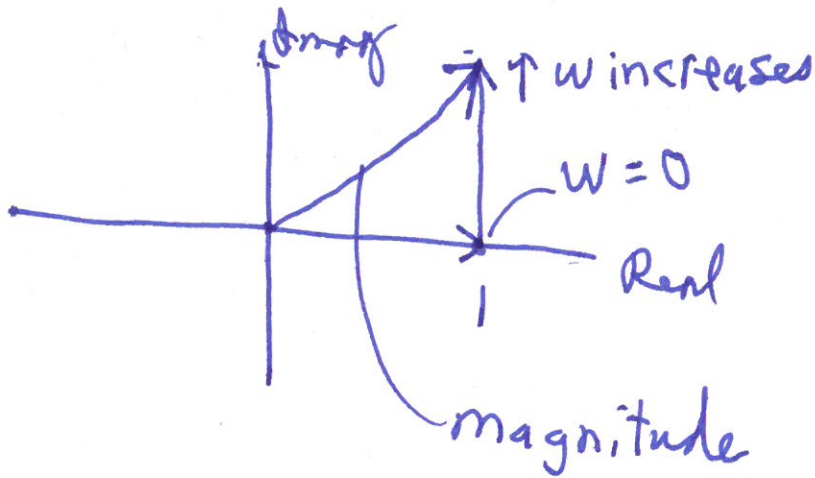

$$\frac{1}{j} = \frac{j}{j \cdot j} = \frac{j}{-1} = -j$$

Cutoff frequency

$$1 = R_2 \omega_c C$$

$$\omega = 2\pi f$$

$$A_v = -\frac{R_2}{R_1} \frac{1}{1 + j\omega \frac{R_2 C}{R_1}} = -\frac{R_2}{R_1} \frac{1}{1 + j\frac{f}{f_c}}$$

$$A_v(f) = A_v(0) \frac{1}{1 + j\frac{f}{f_c}}$$

↑ Lorentzian

For a real op Amp

$$A_{OL}(f) = A_{OL}(0) \frac{1}{1 + j\frac{f}{f_{BOL}}}$$

↑ characteristics of the op Amp

31

$$A_{VOL}(f) = - \frac{R_2}{R_1}$$

↑ No load ($R_L \rightarrow \infty$)
Gain of the circuit

$$\frac{A_{OL}(f)}{\frac{R_2}{R_1} + 1 + A_{OL}(f)}$$

↑ A_{OL} of the op Amp

$$A_{VOL}(f) = - \frac{R_2}{R_1}$$

$$\frac{A_{OL}(0) \frac{1}{1+jf/f_{BOL}}}{\frac{R_2}{R_1} + 1 + A_{OL}(f) \frac{1}{1+jf/f_{BOL}}}$$

After some math

$$A_{VOL}(0) f_B = A_{OL} f_{BOL}$$

↑ gain bandwidth of the circuit ↑ gain Bandwidth of the op Amp

$$A_{VOL}(f) = - \frac{R_2}{R_1} \frac{1}{1+jf/f_B}$$

Gain - Band width Product is constant

~~$A_{vol}(0) f_B$~~

$$A_0 f_{BOL} = 10^6 \text{ Hz}$$

If I ask for $A_{vol}(0) = \overset{10}{\cancel{20}} \text{ dB} \quad (20 \text{ dB})$

$$f_B = \frac{10^6 \text{ Hz}}{10}$$

$$= 10^5 \text{ Hz}$$

$$\left(\frac{\cancel{A_{vol}} A_{vol} f_{BOL}}{A_{vol}(0)} \right)$$
