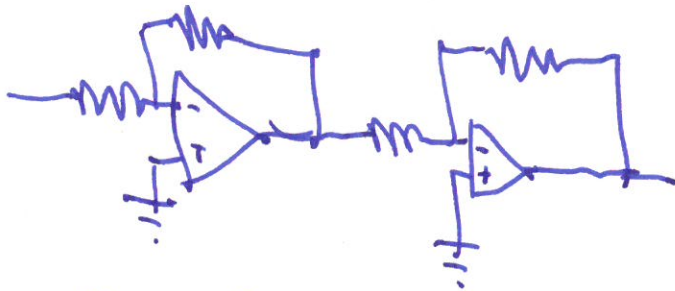


Multi Stage Amps



$$A_v(f) = \frac{A_{v1}(0)}{1 + j f / f_{B1}} \cdot \frac{A_{v2}(0)}{1 + j f / f_{B2}}$$

$$= A_{v1}(0) A_{v2}(0)$$

$$\frac{1 + j f \left(\frac{1}{f_{B1}} + \frac{1}{f_{B2}} \right) + f^2 / (f_{B1} f_{B2})}{f_{B \text{ eff}} \approx \frac{1}{f_{B1}} + \frac{1}{f_{B2}}}$$

f small

f large

gain $\propto \frac{1}{f^2}$ (40dB/decade)

1 stage


100
 $A_v = 100^2$
 20dB
 40dB
 60dB
 1MHz
 10kHz
 100Hz

2 stages


40dB 644kHz.

DC imperfections


(34)

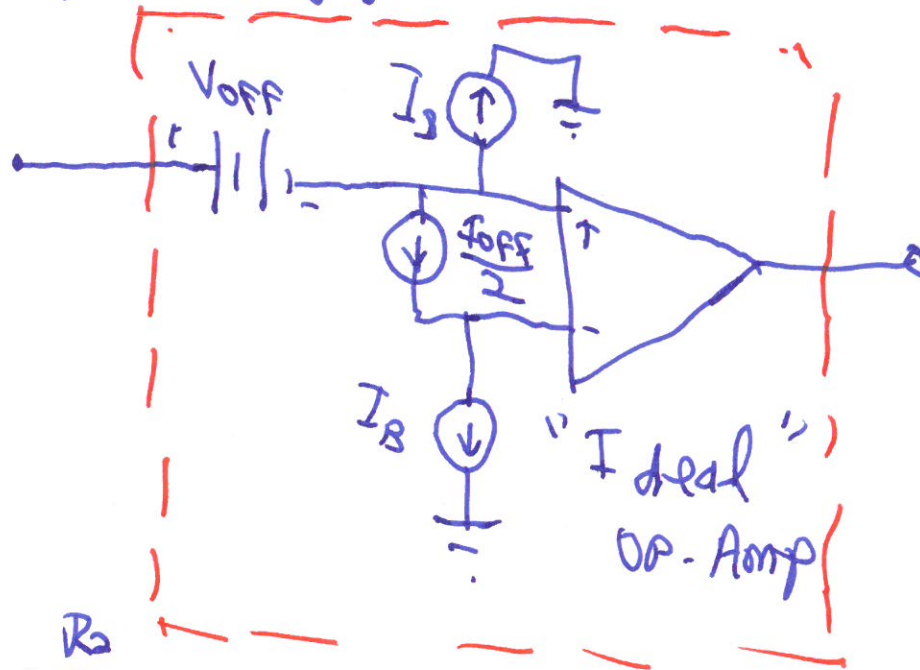

what we want

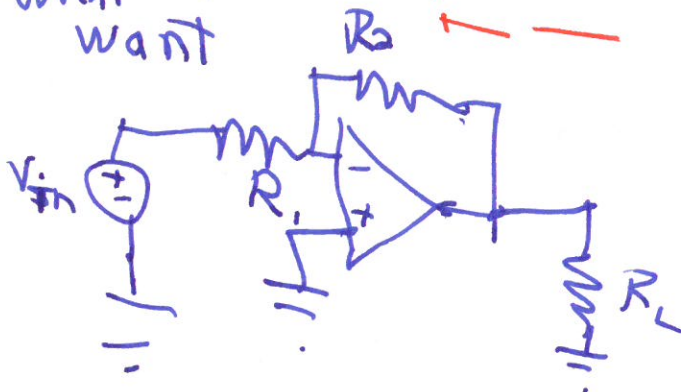


offset voltage

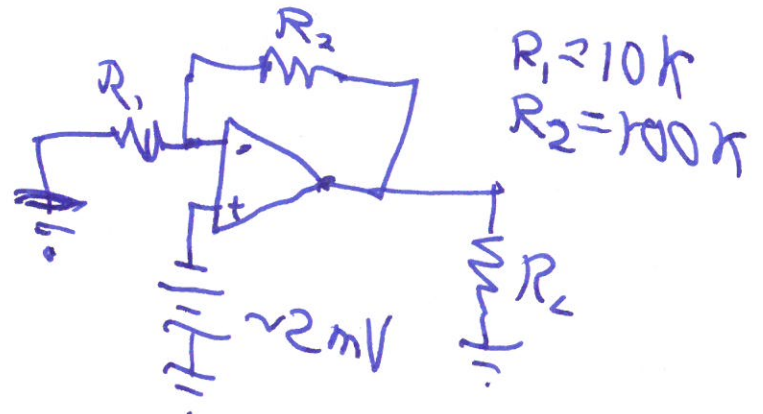

$R_1 \approx 10k$
 $R_2 = 100k$

Bias Current

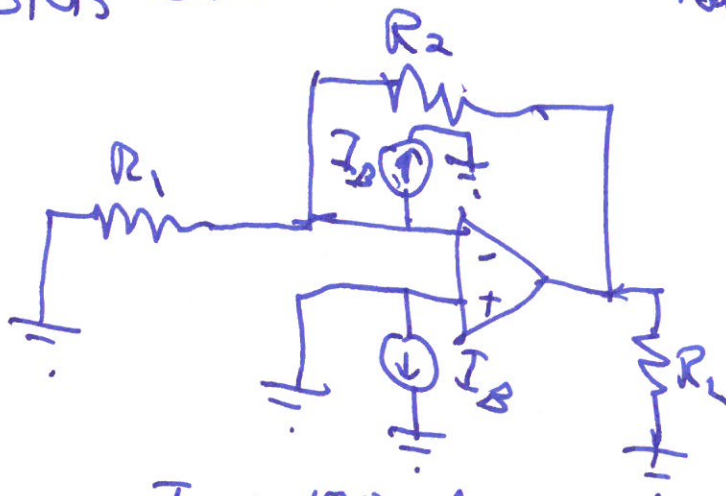


$I_B \approx 100nA$

$V_{out} = R_2 I_B \approx 10mV$

$V_{out} = (1 + \frac{R_2}{R_1}) V_{off} \approx 22mV$

offset current

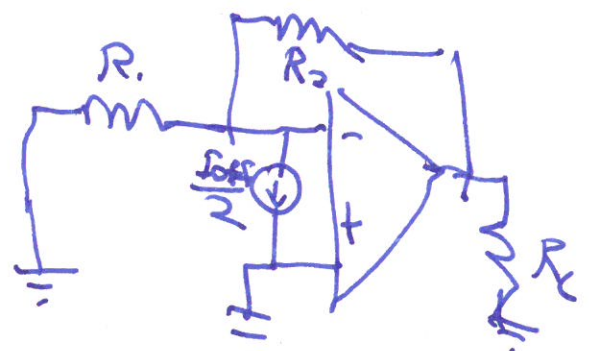

$V_{out} = -R_2 \frac{I_{off}}{2} \approx -2mV$

Desired output

$$V_{in} \frac{-R_2}{R_1} \Rightarrow V_{in} \times 10$$

Offset voltage

$$\left(1 + \frac{R_2}{R_1}\right) V_{off} \approx 22 \text{ mV}$$

Bias Current

$$V_{off} = R_2 I_B \approx 10 \text{ mV}$$

Offset current

$$-R_2 \frac{I_{off}}{2} \approx -2 \text{ mV}$$

Worst Case

$$22 + 10 + 2 = 34 \text{ mV}$$

$$-22 + 0 - 2 = -24 \text{ mV}$$

Typical

$$5 \text{ mV} \pm \sqrt{22^2 + 2^2}$$

about 27 mV uncertainty
in output

Dynamic Range

$$\frac{V_{max}}{V_{min}} = \frac{15 \text{ V}}{27 \text{ mV}}$$

$$\approx 555 \quad (55 \text{ dB})$$

correct for Bias current

