


5 Oct 2016

50


$$\begin{array}{ccccccc}
 & N_A & + & n & = & N_D & + & p \\
 \text{N-type} & 0? & & \uparrow \downarrow & & \uparrow & & \downarrow \\
 \text{P-type} & \uparrow & & \downarrow & & 0? & & \uparrow \downarrow
 \end{array}$$

$$\begin{array}{lcl}
 \text{N-type} & n = N_D - N_A + p & \approx N_D \\
 \text{P-type} & p & \approx N_A
 \end{array}$$



Junction

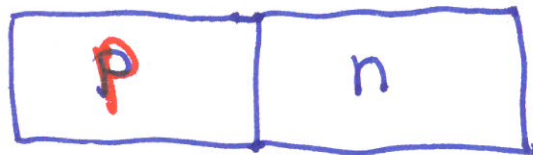

Concentration

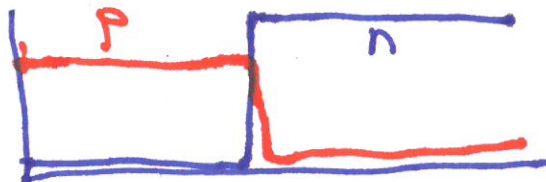


Diffusion Current

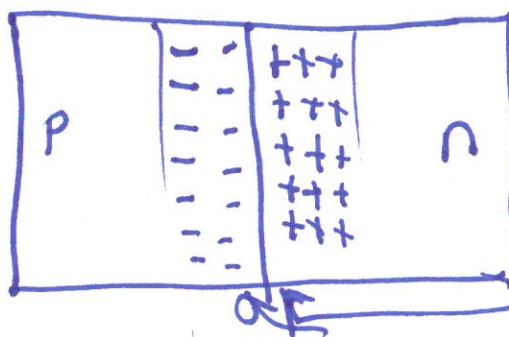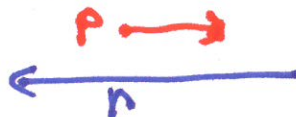


Depletion Region

51

~~50~~

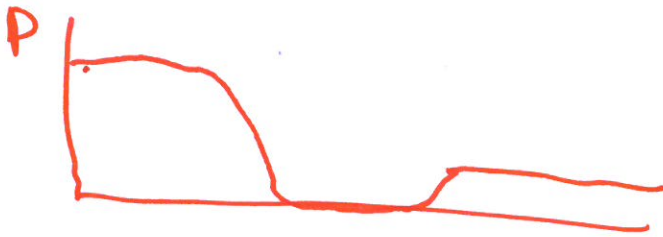



$p \rightarrow$
 $n \leftarrow$

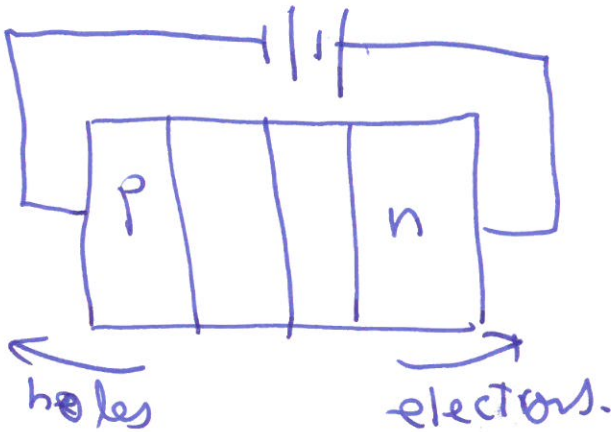

Wider
Depletion
Region

$$C = \frac{\epsilon A}{D}$$


Reverse Current
Saturation Current, I_s

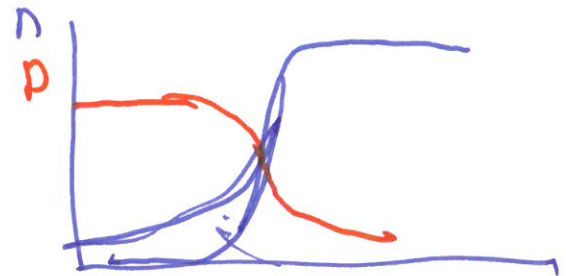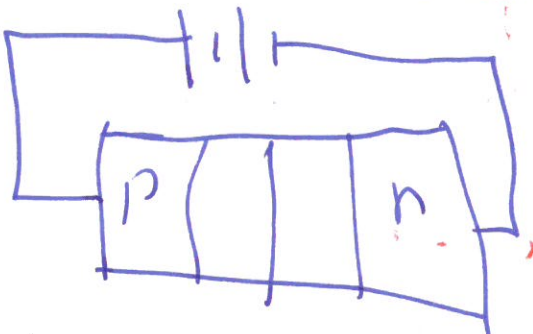

Shockley Equation

52
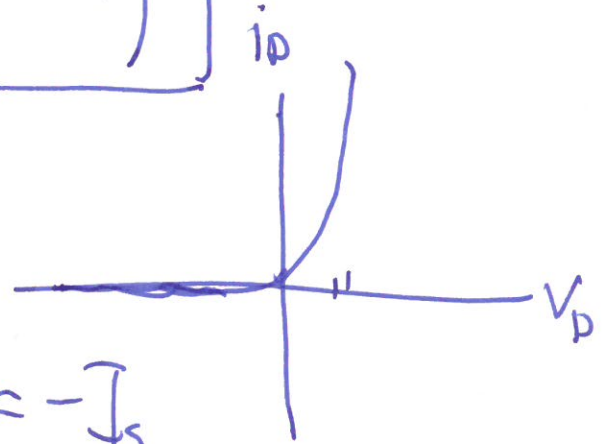
$$i_D = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$



Reverse Bias

$$i_D = -I_S$$

Forward Bias

$$i_D \approx I_S e^{\frac{V_D}{nV_T}}$$


V_T = thermal voltage
25 mV @ room temp.


$$1 < n < 2$$

Use this equation carefully.

Usually solve for V_D

Example

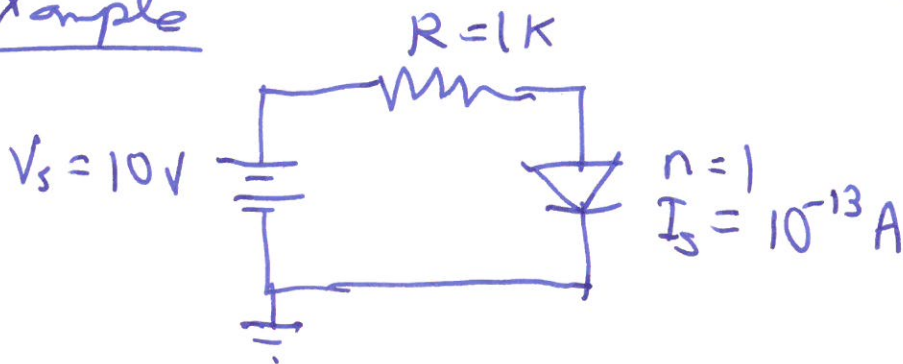

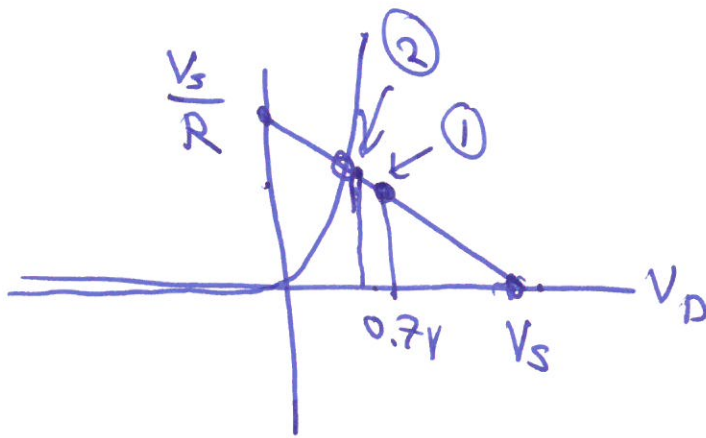

Guess $V_D = 0.7 \text{ V}$

calculate $i_D = \frac{V_S - V_D}{R} = 9.3 \text{ mA}$ (1)

Use S.Eq.

for V_D $\frac{V_D}{nV_T} = \ln \frac{i_D}{I_S}$

$V_D = nV_T \ln \frac{i_D}{I_S} = 0.6314 \text{ V}$ (1)


Second Time

$i_D = 9.4 \text{ mA}$

$V_D = 0.6316 \text{ ~~mA~~ V}$ (2)

Small signal model


54

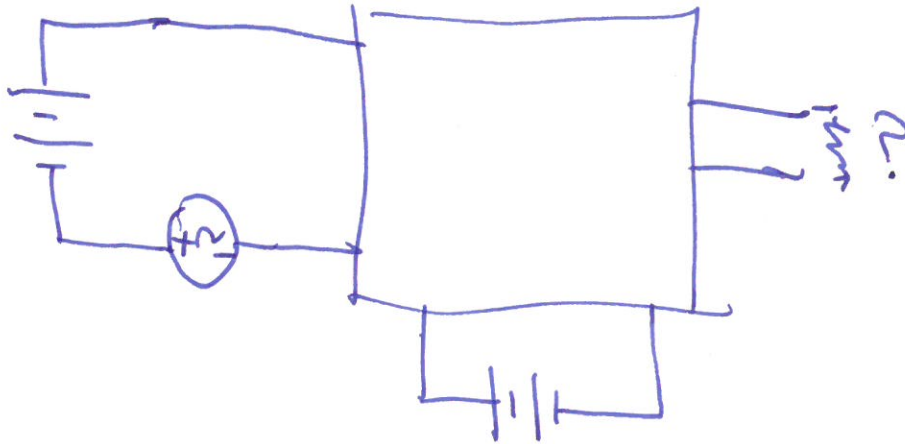

$$V_D = V_D + v_d$$

↑ ↑ ↑
 Total DC AC
 Voltage

$$i_D = I_D + i_d$$

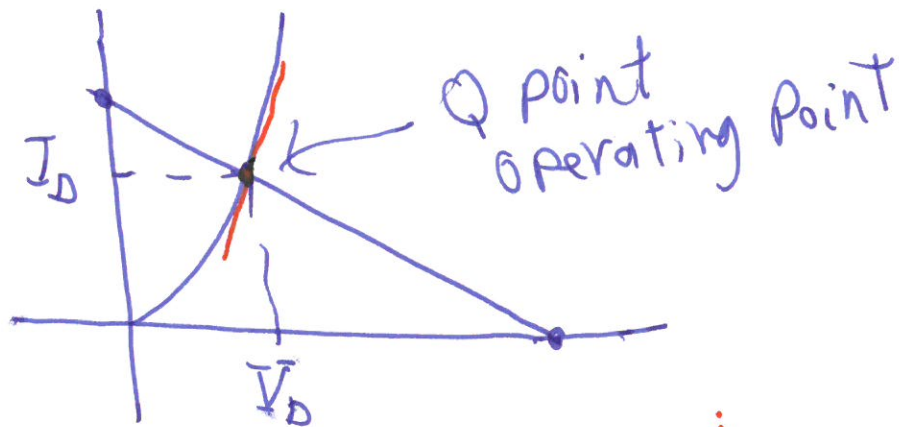

$$r_d = \left(\frac{di_D}{dV_D} \right)^{-1}$$

