

6 October 2016

55

Derivative $\frac{di_D}{dV_D}$

$$i_D = I_S e^{V_D / (nV_T)}$$


$$\frac{di_D}{dV_D} = I_S \frac{1}{nV_T} e^{V_D / (nV_T)}$$

$$\frac{di_D}{dV_D} = \frac{i_D}{nV_T}$$

$$r_d = \frac{nV_T}{i_D}$$

AC equivalent of a diode is a resistor


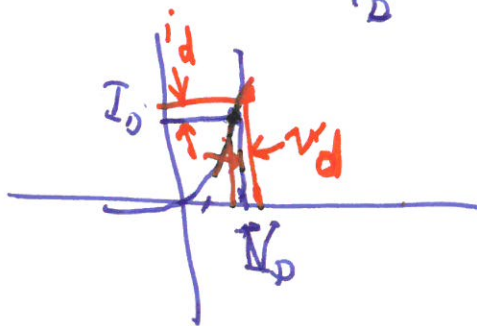
$$r_d = \frac{nV_T}{i_D} = \frac{nV_T}{I_D}$$




I_D is the DC current

i_d is the AC current

$$i_D = I_D + i_d$$

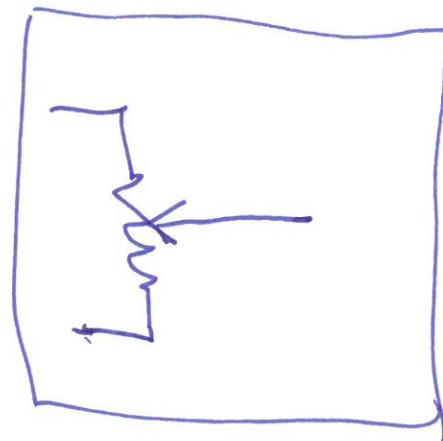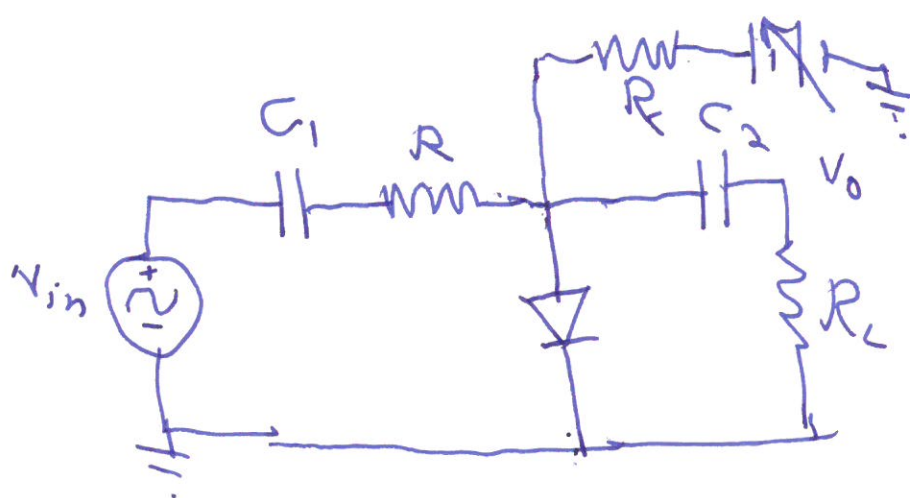

① DC circuit

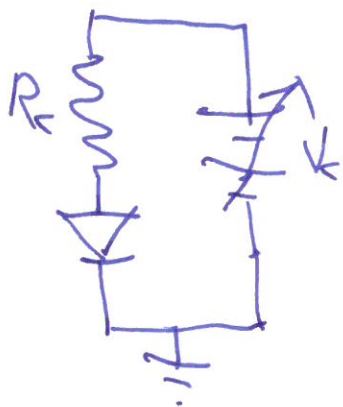


$$I_D = \frac{V_c - 0.7V}{R_c}$$

② Small signal model
Diode in AC circuit is a resistor

$$r_D = \frac{nV_T}{I_D}$$

③ AC circuit

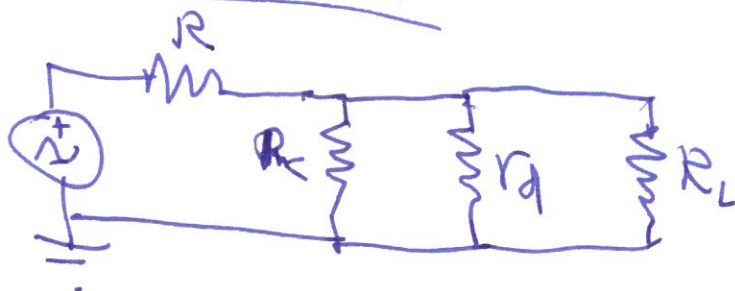

$$R_L \rightarrow \infty$$

$$R_c \rightarrow \infty$$

$$n = 1 \quad R \gg r_d$$

$$\frac{V_o}{V_{in}} = \frac{r_d}{R + r_d} \approx \frac{r_D}{R} = \frac{R_c}{R} \frac{0.025V}{V_c - 0.7V}$$

All depends on $V_d \ll V_D$



$$\frac{d^2 i_D}{dV_D^2} \rightarrow \Delta i_D \propto (\Delta V_D)^2$$

Keep ac signal small WRT DC
Else distortion.

Photodiode

Shockley Eq

$$i_D = I_S (-1 + e^{V/V_T})$$

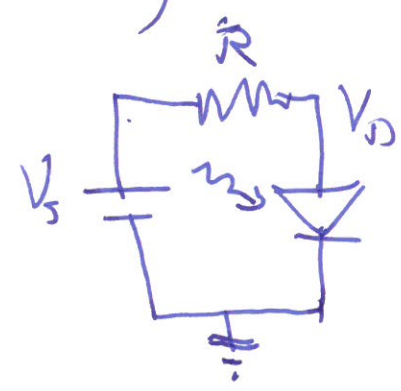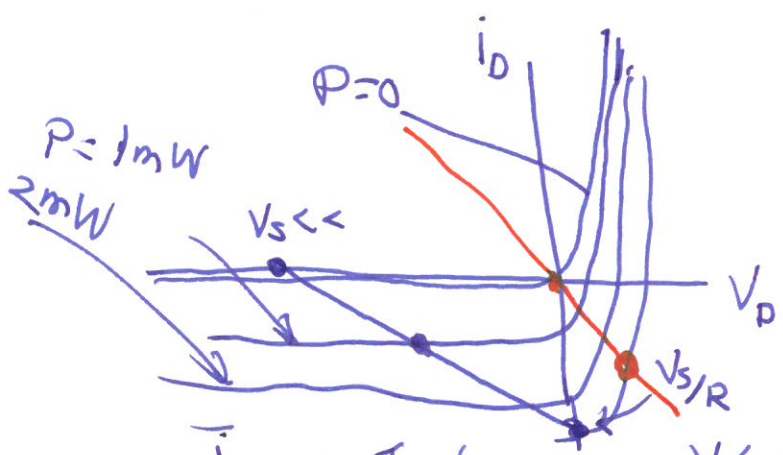

$$i_D = I_S (-1 + e^{V/V_T}) - ? P_{optical}$$

$V_S \ll 0$

No light: $V_D = V_S$ (neg)

↑ light $V_D \rightarrow 0$


Too much light $V_D \approx 0$

$V_S = 0$

↑ light


$V_D \rightarrow +$

$i_D \rightarrow -$

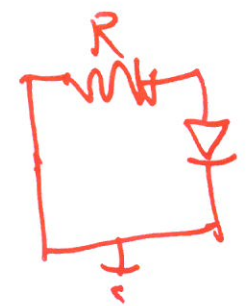



$P = i_D V_D < 0$ diode is a power source

$V_S = 0$ but use transimpedance amp

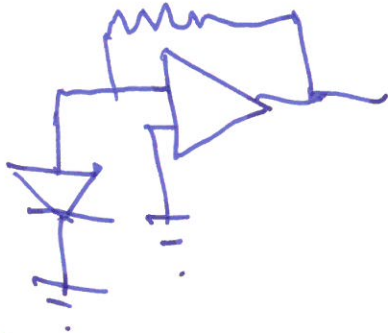


$V_{out} \propto I + P_{optical}$

Final Example: power supply

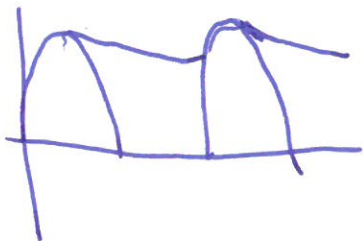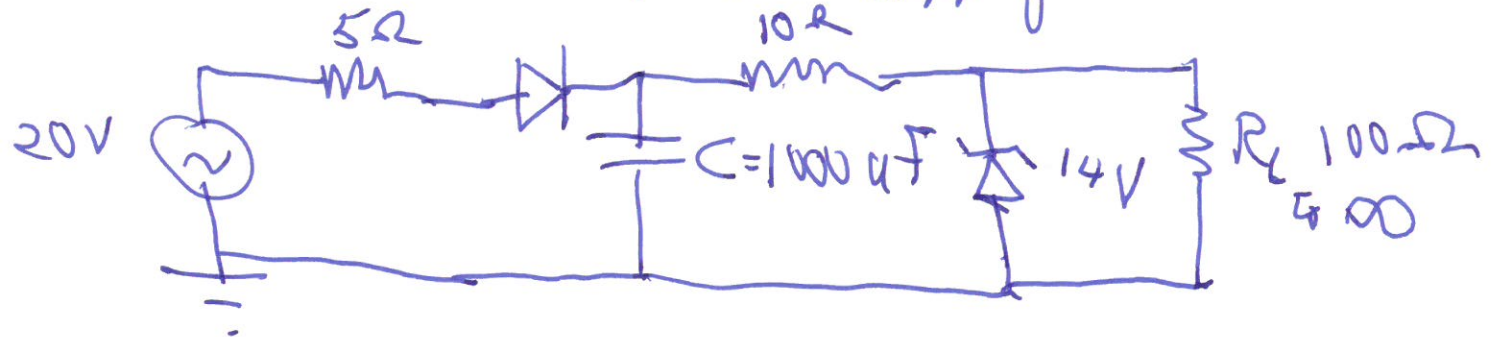

Without Zener

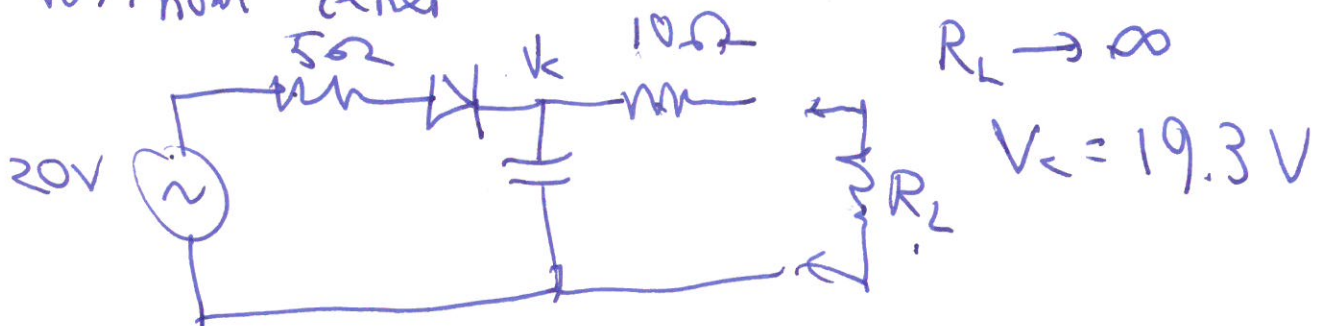

(59)

with $R_L = 100 \Omega$



Charge: $V_C = (20V - 0.7V) \frac{110 \Omega}{115 \Omega}$

~~$V_C = \frac{110 \Omega}{115 \Omega}$~~

Discharge

$$V_C = V_{C_{\max}} e^{-t/RC} \quad R = 110 \Omega$$


$$= 18.5V$$

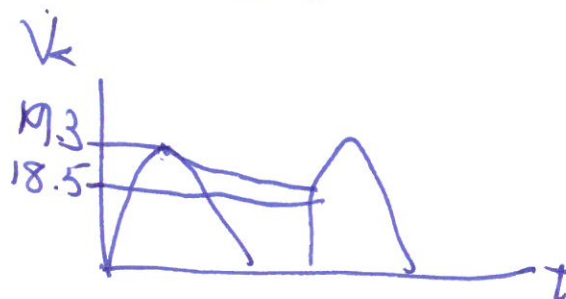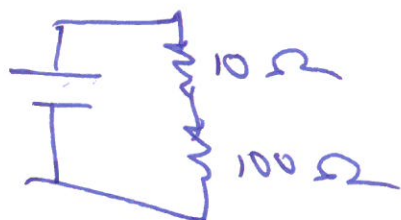

$$V_{out} = V_C \frac{100}{110}$$

$$V_{out_{min}} = 15.9V$$

put the zener in

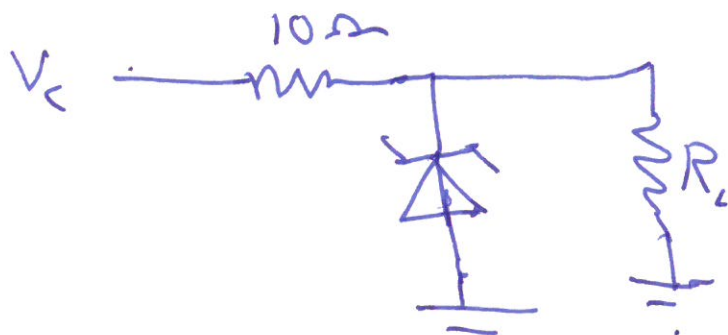

$$I_{Load} = \frac{14V}{100 \Omega} = 0.14A$$

$$I_{zener} = \frac{(V_C - 14V)}{10 \Omega} \quad 0.31 \text{ to } 0.05A$$