
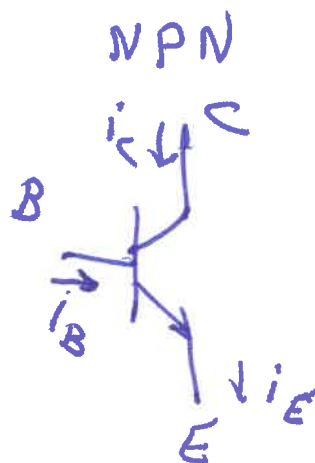
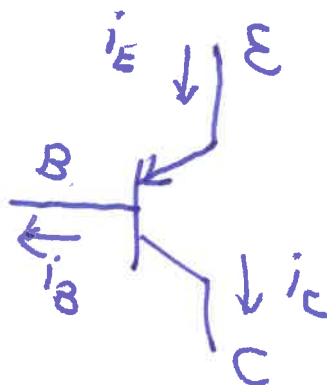


Thu 20 Oct 2016

70

PNP

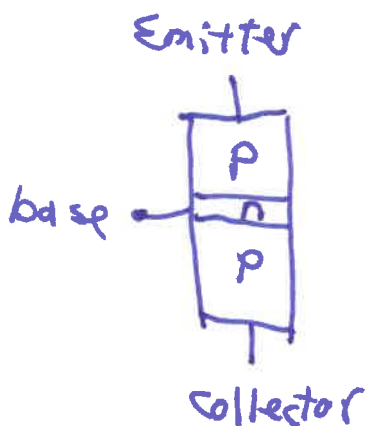

Same as
NPN

$$\begin{cases} i_C = \beta i_B \\ i_E = \alpha i_B \end{cases}$$

$$\alpha = \frac{\beta}{\beta + 1}$$



$$i_E = i_C + i_B$$

Different
from
NPN


$$i_E = I_{ES} [e^{-V_{BE}/V_T} - 1]$$

$$i_B = (1 - \alpha) I_{ES} [e^{-V_{BE}/V_T} - 1]$$

IV Curves

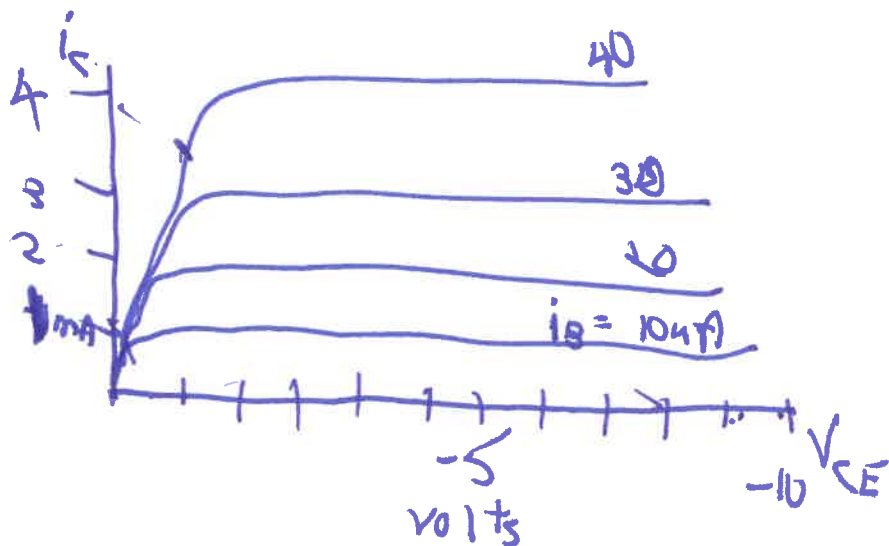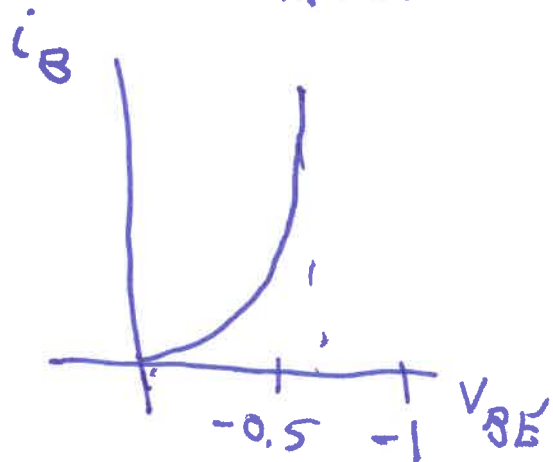

(71)

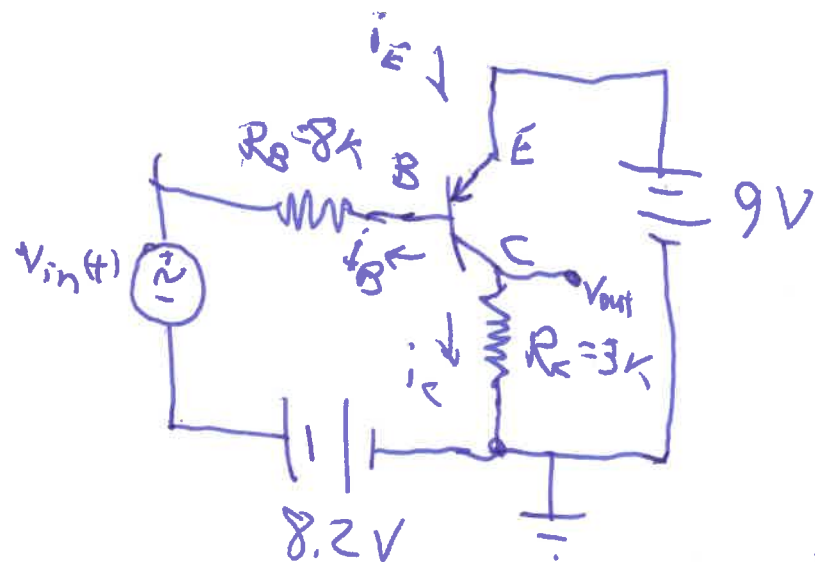

Common
Emitter
Amp.

Solve the DC circuit
to find i_{BQ}

$$i_{BQ} = \frac{9V - 0.6V - 8.2V}{8k}$$

$$= \frac{0.2V}{8k} = 25 \mu A$$

$$i_C = \beta i_B = 2.5 \text{ mA}$$

DC solution

$$I_{BQ} = 25 \mu A$$

$$I_{CQ} = 2.5 \text{ mA}$$

$$V_{CEQ} = 7.5V$$

$$V_{CE} = -2.5V$$

AC circuit



$$i_b = \frac{v_{in(t)}}{R_B}$$

$$i_C = \beta i_B$$

$$v_C = +i_C R_C$$

$$v_{out} = v_C = R_C \beta \frac{-v_{in}}{R_B}$$

$$= -\beta \frac{R_C}{R_B} v_{in}$$

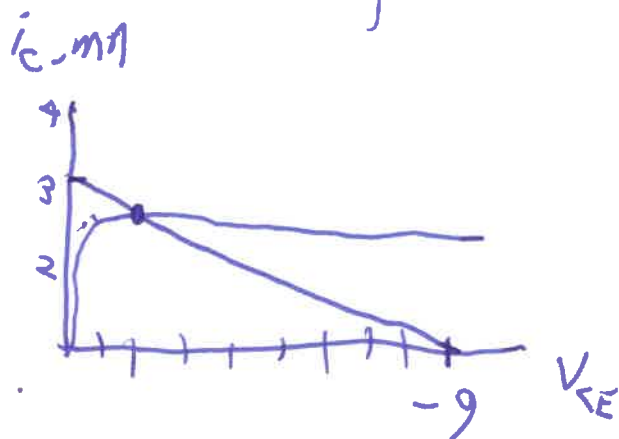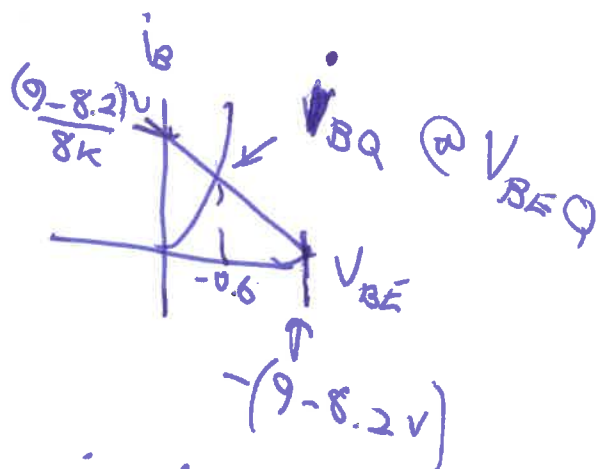



$$A_v = -\beta \frac{R_C}{R_B} = -100 \frac{3k\Omega}{8k\Omega} = -37$$

(~~12 dB~~) 32 dB


AC + DC models

Superposition

NPN

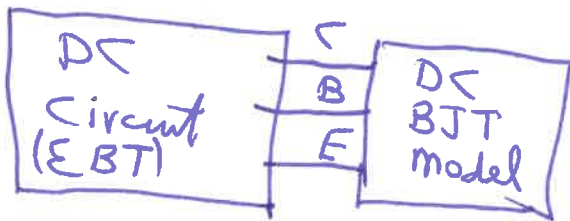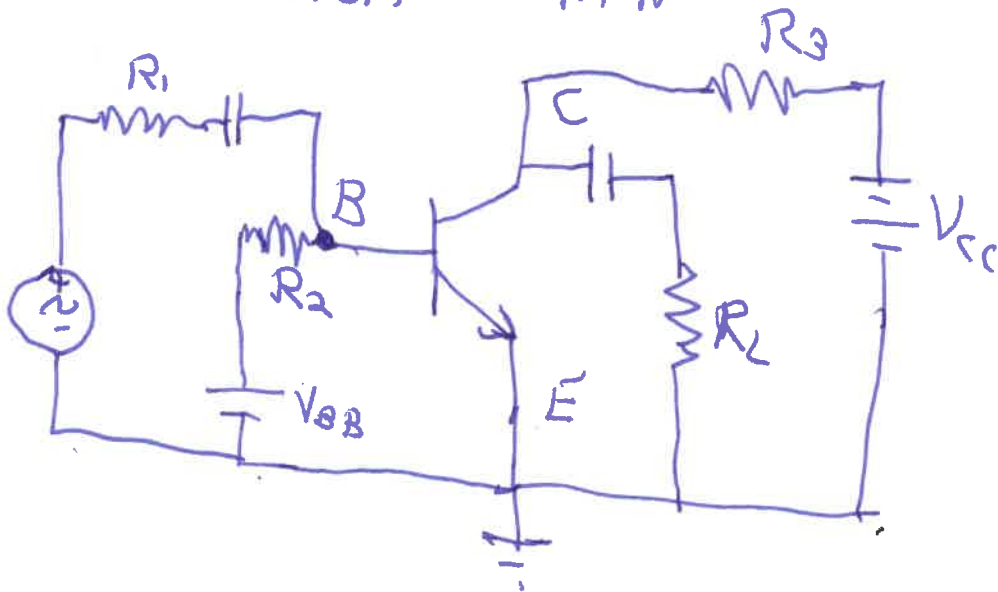

Solve for all
 I_x, V_{xy}

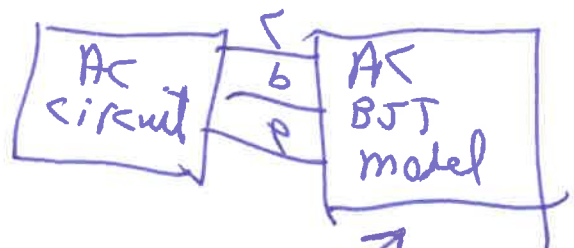

Solve for
 A_v, R_{in}, R_{out}

Fig 4.19

