

Small Signal Model

Notation.

$i_B(t)$ = total current

$V_{BE}(t)$ = total V_{BE} (range)

I_B = DC part

$i_b(t)$ = AC part

$$i_B(t) = I_B + i_b(t)$$


Sinusoids

$$i_b(t) = I_b e^{j\omega t}$$

AC part complex peak current

$$\text{or } i_b(t) = I_b \cos(\omega t + \phi)$$

real peak phase

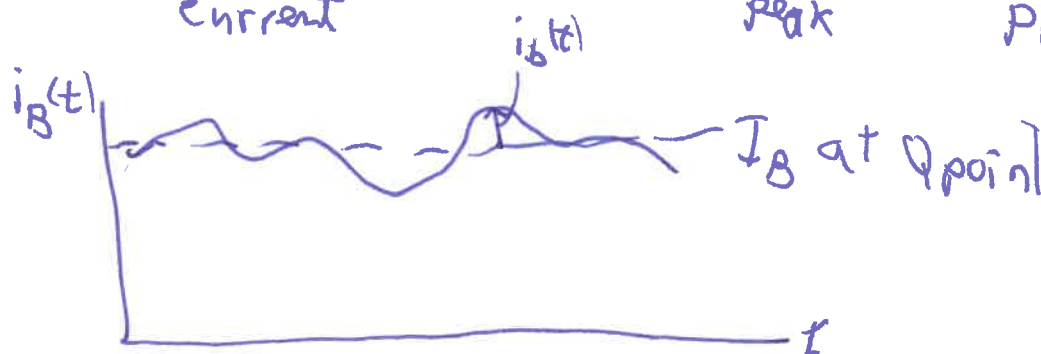

Base-Emitter Circuit


$$i_B(t) = \frac{I_S}{\beta} e^{V_{BE}(t)/V_T}$$

$$V_{BE} = V_{BE} + v_{be}(t)$$

AC part (small)

$$i_B(t) = \frac{I_S}{\beta} e^{V_{BE}/V_T} e^{v_{be}(t)/V_T}$$
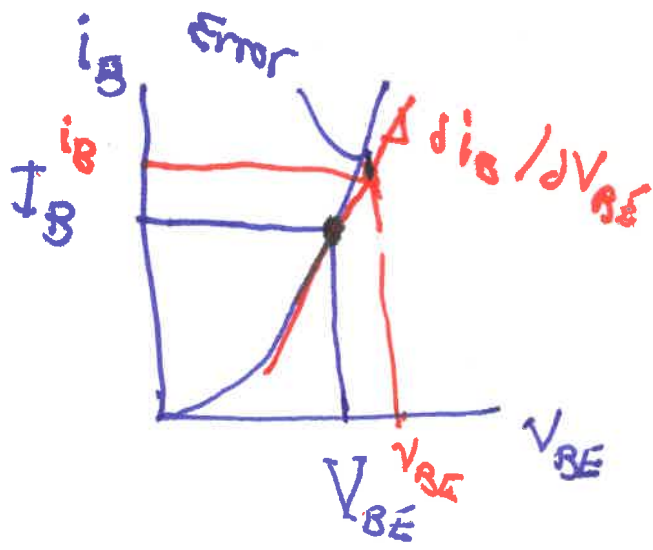
$$= \left(\frac{I_S}{\beta} e^{V_{BE}/V_T} \right) \left(1 + \frac{v_{be}(t)}{V_T} \right)$$



$$i_B(t) = I_B \left(1 + \frac{I_B}{V_T} v_{be}(t) \right)$$

~~$$I_B + i_b(t) = I_B + \frac{I_B}{V_T} v_{be}(t)$$~~

For $A \ll 1$ the "be" circuit looks like


$$r_{\pi} = \frac{V_T}{I_B} = \frac{\beta V_T}{I_C}$$

Collector current

$$i_c(t) = \beta i_b(t)$$

$$I_C + i_c(t) = \beta I_B + \beta i_b(t)$$

$$i_c(t) = \beta i_b(t)$$

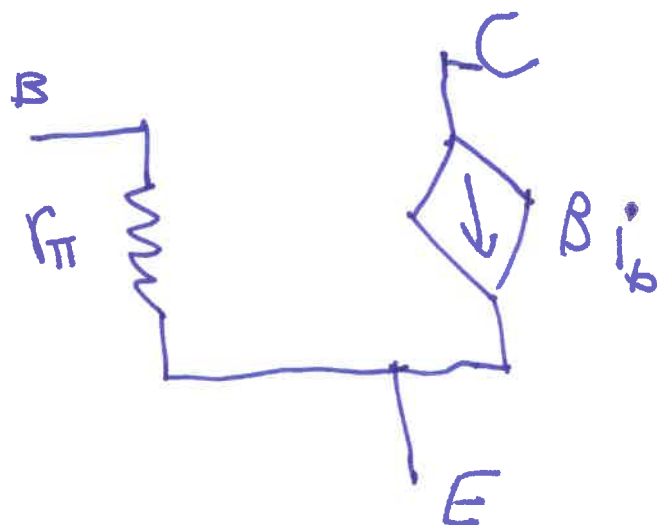

Pi model

$$i_b(t) = \frac{V_{be}(t)}{r_{\pi}}$$


$$i_c(t) = \frac{\beta}{r_{\pi}} V_{be}(t)$$

Transconductance


$$i_c(t) = g_m V_{be}(t)$$

$$g_m = \frac{\beta}{r_{\pi}}$$

$$g_m = \frac{I_c}{V_T}$$

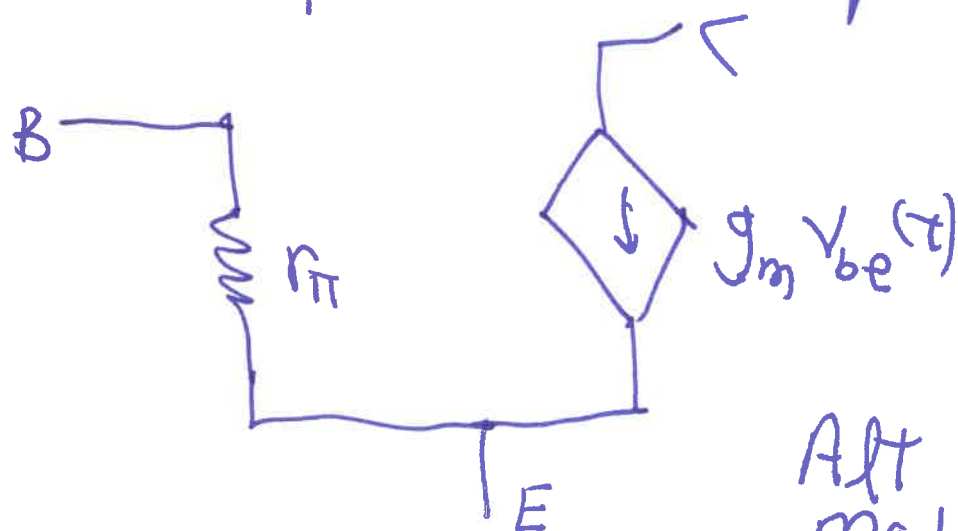Independent of β , I_s 

Alt Pi model

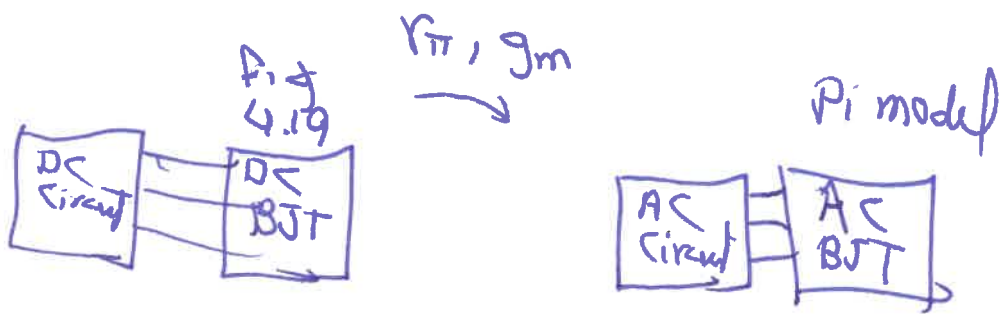

Numbers

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 0.04 \frac{\text{A}}{\text{V}}$$

$$r_{\pi} = \beta \frac{V_T}{I_C} = \frac{100 \times 25 \text{ mV}}{1 \text{ mA}} = 2.5 \text{ K}$$

AC Circuits Common Emitter Amplifier

