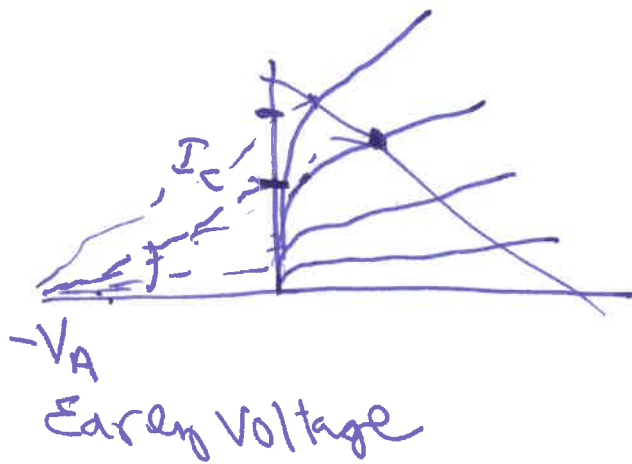


Mon 31 Oct 2016




88



$$r_o \text{ or } r_{ce} = \frac{dV_{CE}}{dI_C} \quad (\text{inverse slope})$$

$$r_o = \frac{V_A}{I_C}$$

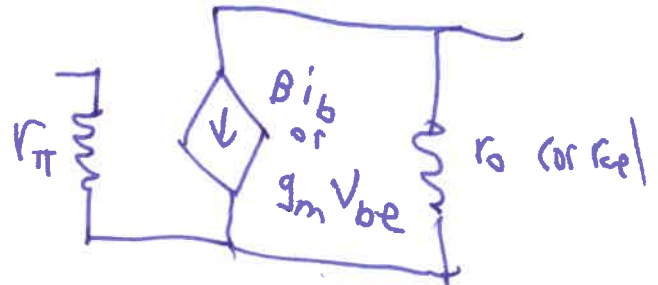



BJT Amplifiers

$$A_i = A_v \frac{R_{in}}{R_L}$$

Common Emitter	In B	out C	Voltage Gain and Current Gain
Common Collector (Emitter follower)	B	E	$A_v \approx 1$
Common Base	E	C	$A_i \approx 1$


Why Common Collector

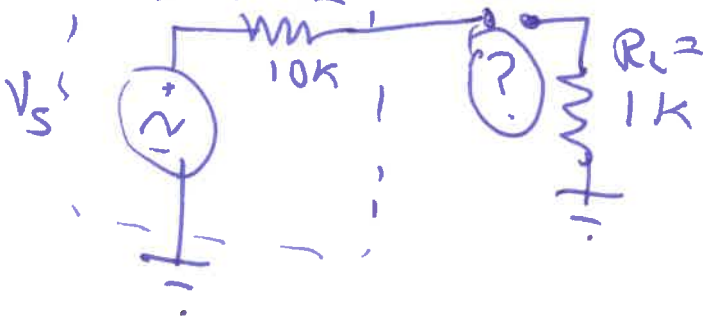

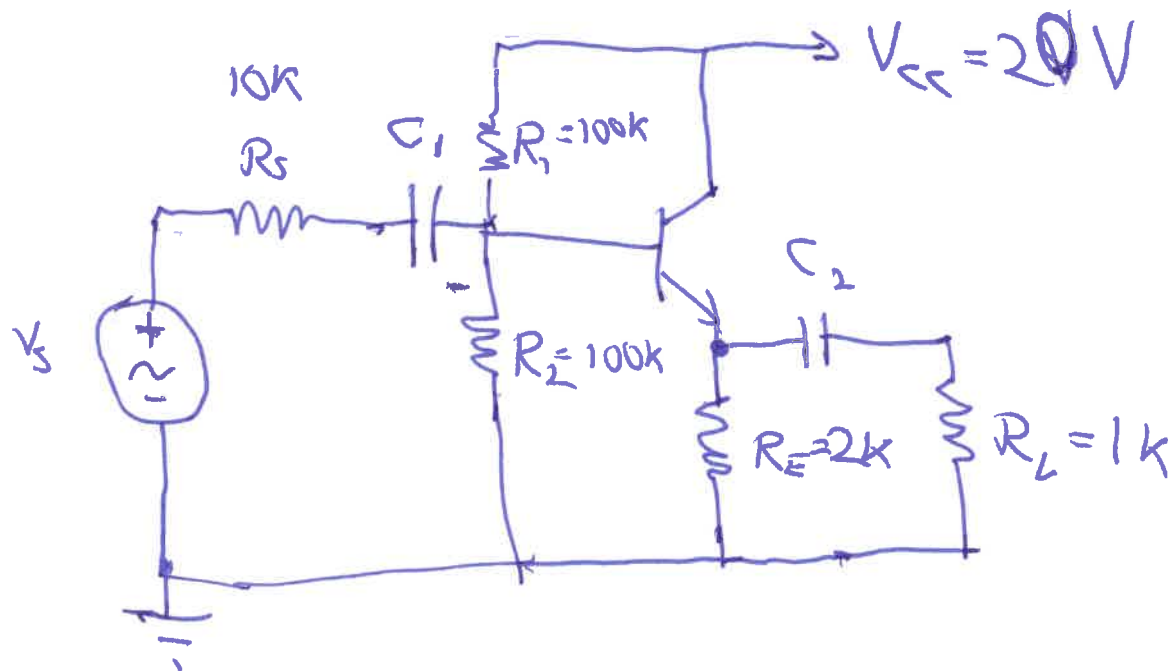

4-Resistor circuit with $R_c = 0$

DC circuit

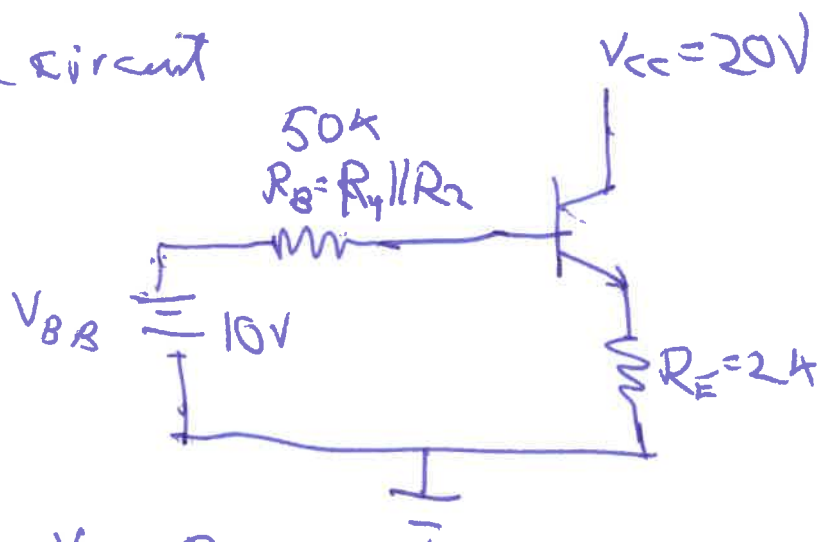

$$V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2} = 10V$$

$$i_{sc} = V_{CC} / R_1$$

$$R_B = R_1 || R_2$$


$$V_{BB} - I_B R_B - I_B (\beta + 1) R_E = 0$$

$$I_B = \frac{V_{BB} - 0.7V}{R_B + (\beta + 1) R_E} = 46 \mu A$$

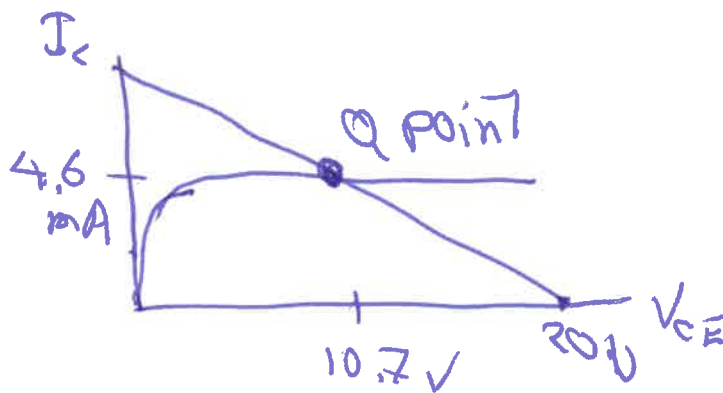(90)

$$I_C = \beta I_B = 4.6 \text{ mA} \quad (\text{Good!})$$

$$V_{CE} = V_C - (\beta + 1) I_B R_E = 10.7 \text{ V}$$




Small signal model

$$r_{\pi} = \frac{\beta V_T}{I_C} = \frac{100 \times 25 \text{ mV}}{4.6 \text{ mA}} = 544 \Omega$$

$$\beta = 100$$

AC Circuit

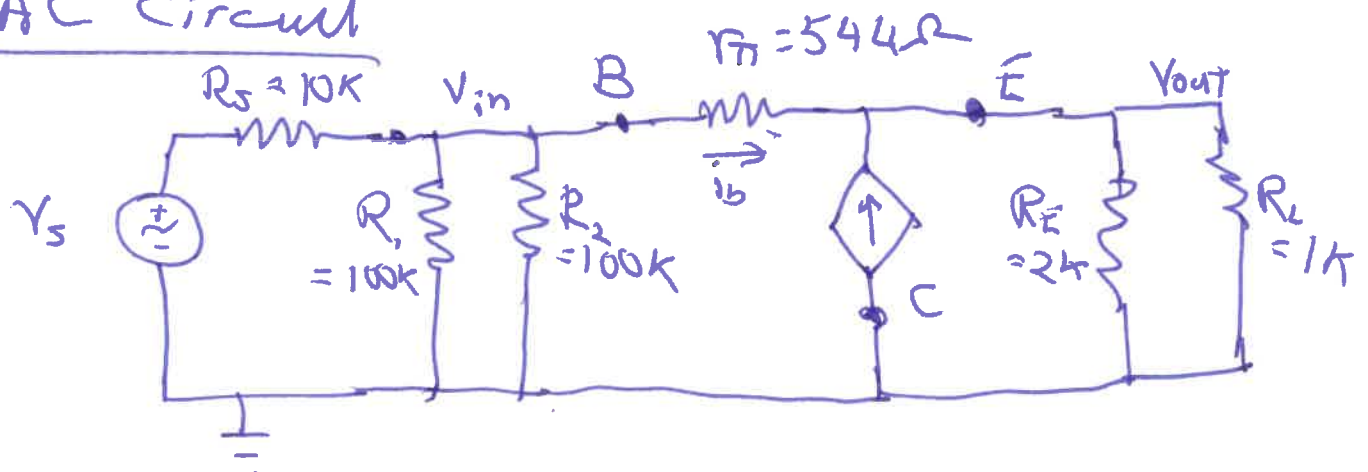


(91)

$$V_{in} = i_b r_{\pi} + (\beta + 1) i_b (R_E \parallel R_L)$$

$$V_{out} = (\beta + 1) i_b (R_E \parallel R_L)$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{R_E \parallel R_L}{R_E \parallel R_L + \frac{r_{\pi}}{\beta + 1}} = \frac{666 \Omega}{666 \Omega + \frac{544}{101}}$$

$$A_v = 0.992$$

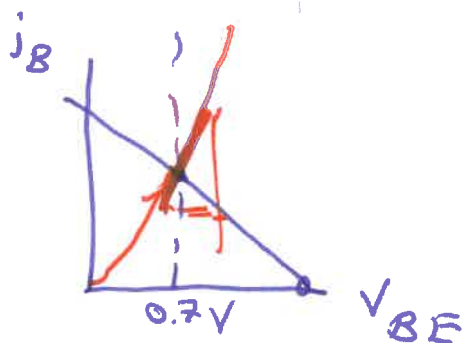

input impedance

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{in}}{i_b} = r_{\pi} + (\beta + 1)(R_E \parallel R_L)$$

$$= 544 + 101 \times 666 = 67.3 \text{ k}$$

output impedance.

$$Z = R_E \parallel \frac{r_{\pi} + (R_S \parallel R_1 \parallel R_2)}{\beta + 1} \approx 2 \text{ k} \parallel \frac{10 \text{ k}}{101}$$

$$\approx 100 \Omega$$

No Amp

