
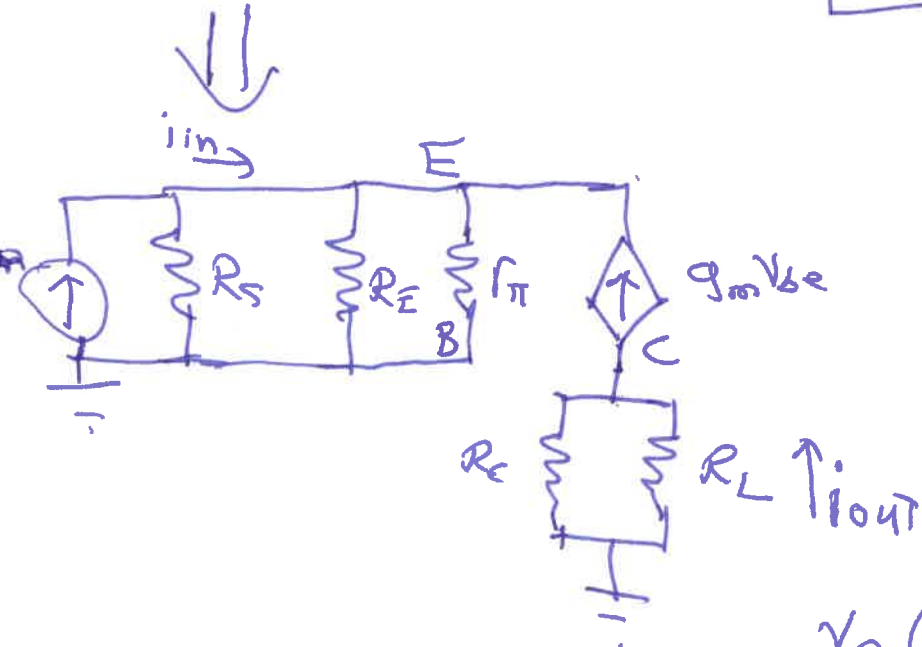
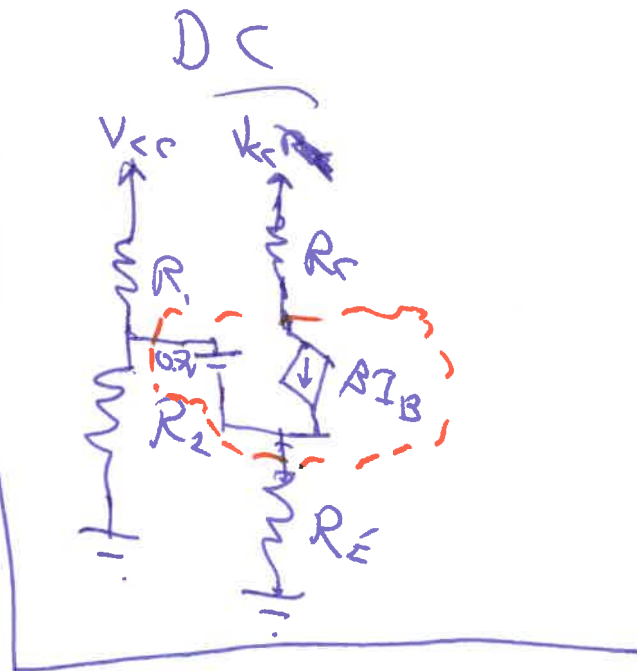
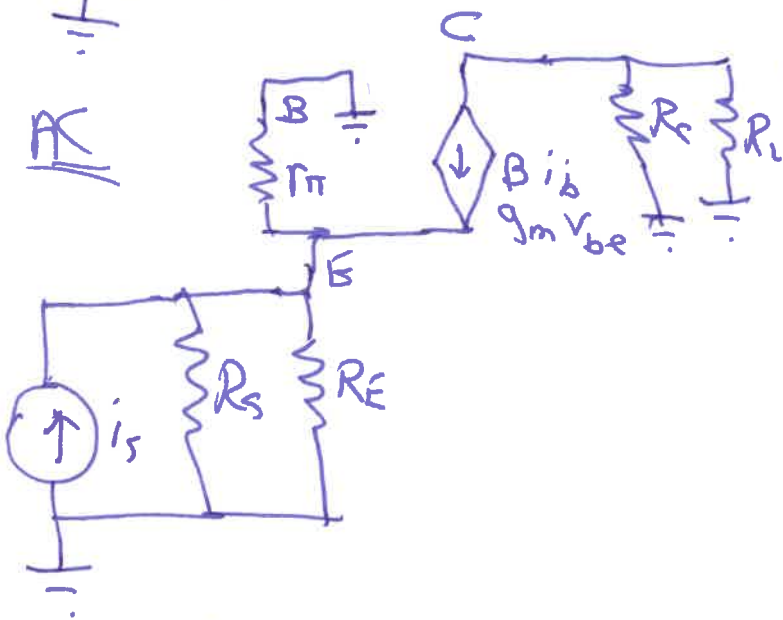


Wed 2 Nov 2016

93

Common Base Amp.

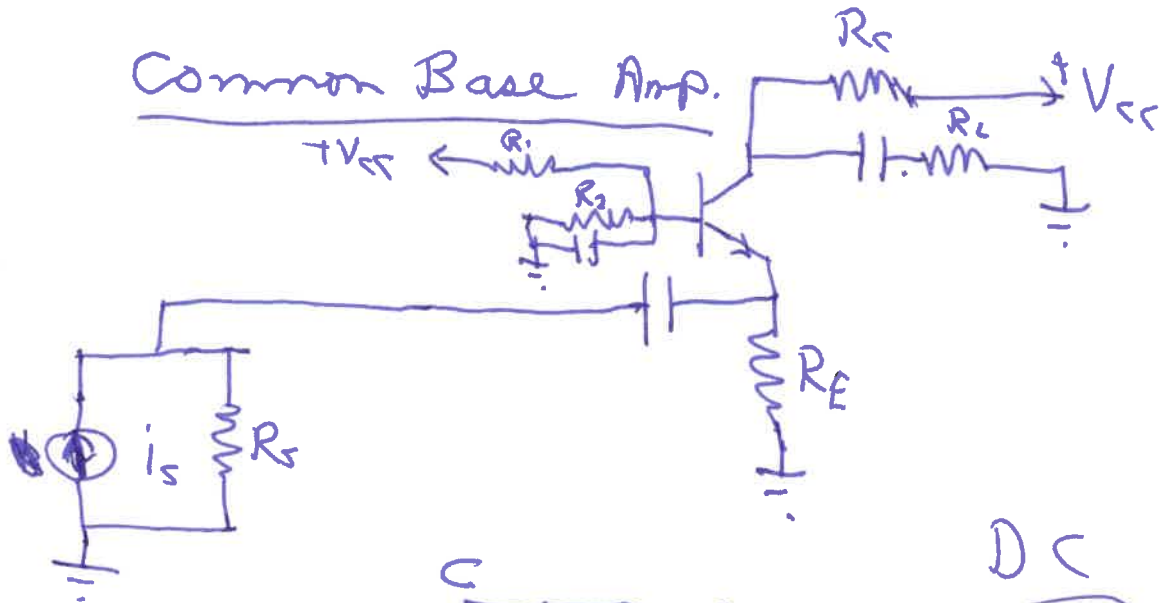

$$V_e = (i_{in} + g_m V_{be})(R_E || r_{\pi})$$

$$V_b = 0 \quad V_{be} = -V_e$$

$$V_e (1 - g_m (R_E || r_{\pi})) = i_{in} (R_E || r_{\pi})$$

$$(g_m V_{be})$$

$$i_c = -g_m V_e = -g_m i_{in} \frac{(R_E \parallel r_\pi)}{1 - g_m (R_E \parallel r_\pi)}$$

$$i_{out} = \frac{R_c}{R_c + R_c} \frac{g_m (R_E \parallel r_\pi)}{g_m (R_E \parallel r_\pi) - 1} i_{in}$$

↑
current divider


R_c small, R_E small


$$i_{out} \approx i_{in}$$

Common E $\rightarrow$ high gain


Common C
Emitter follower $\rightarrow A_v = 1$

Common B $\rightarrow A_i = 1$

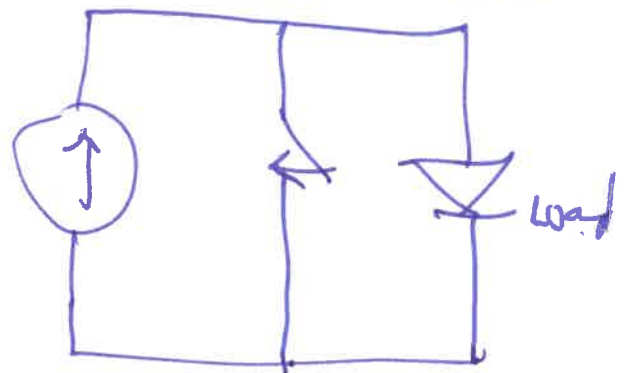

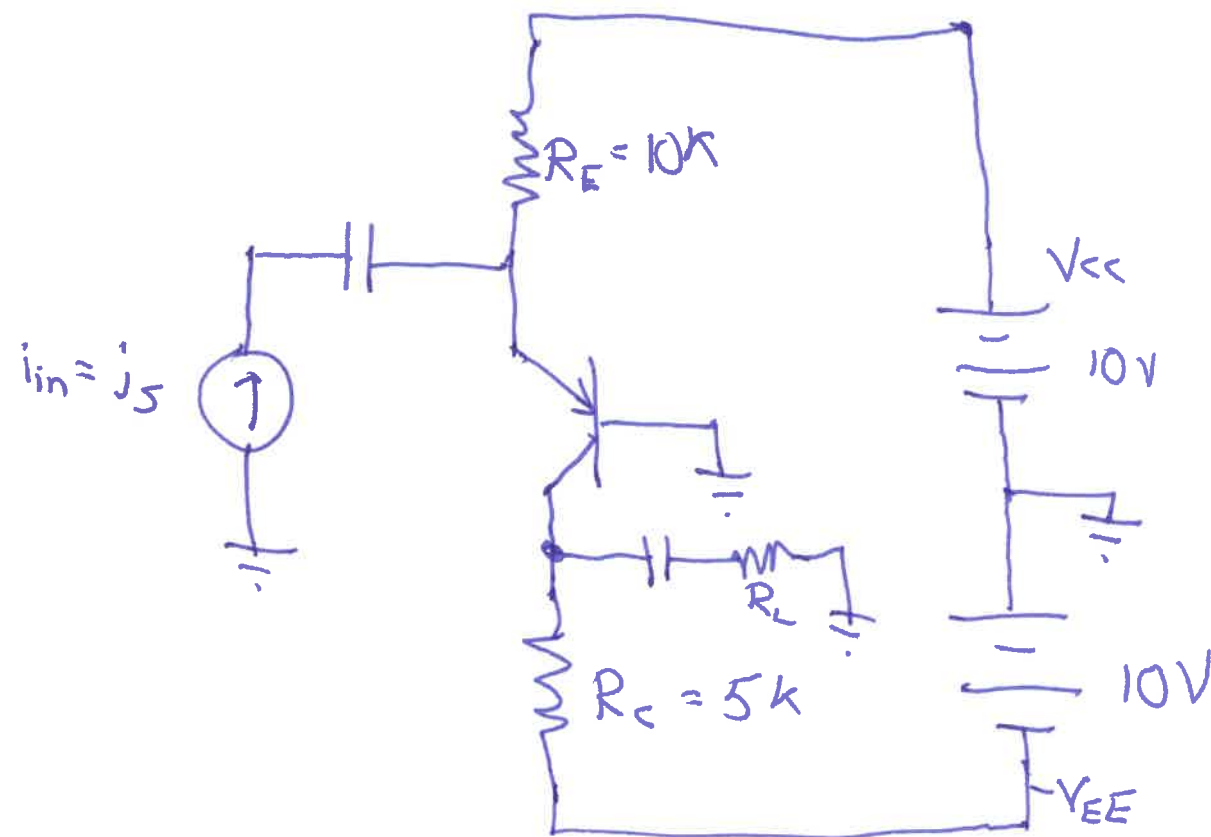

DC Circuit
(Active mode)

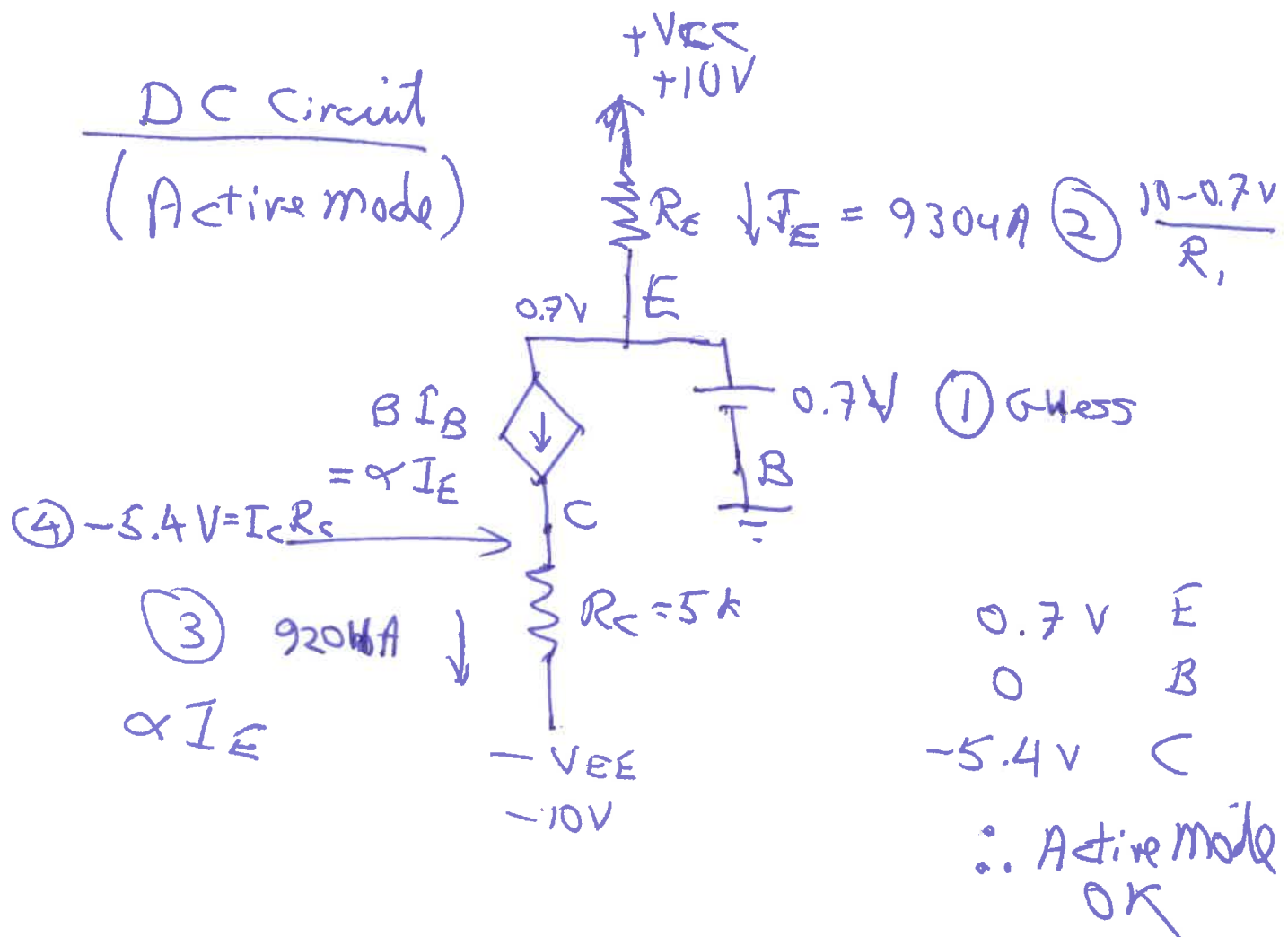



(96)

Small signal model

$$i_c = \beta i_b \quad \text{or} \quad i_c = \alpha i_e \quad \text{or} \quad g_m = \frac{i_c}{V_T}$$

$$= 0.037 \frac{\text{A}}{\text{V}}$$
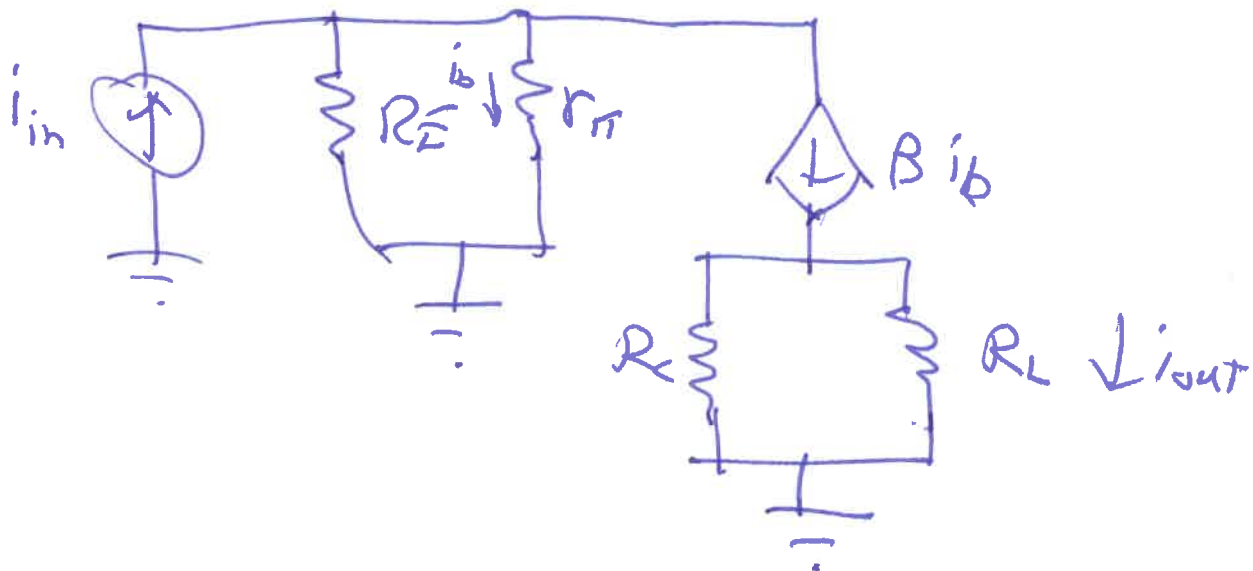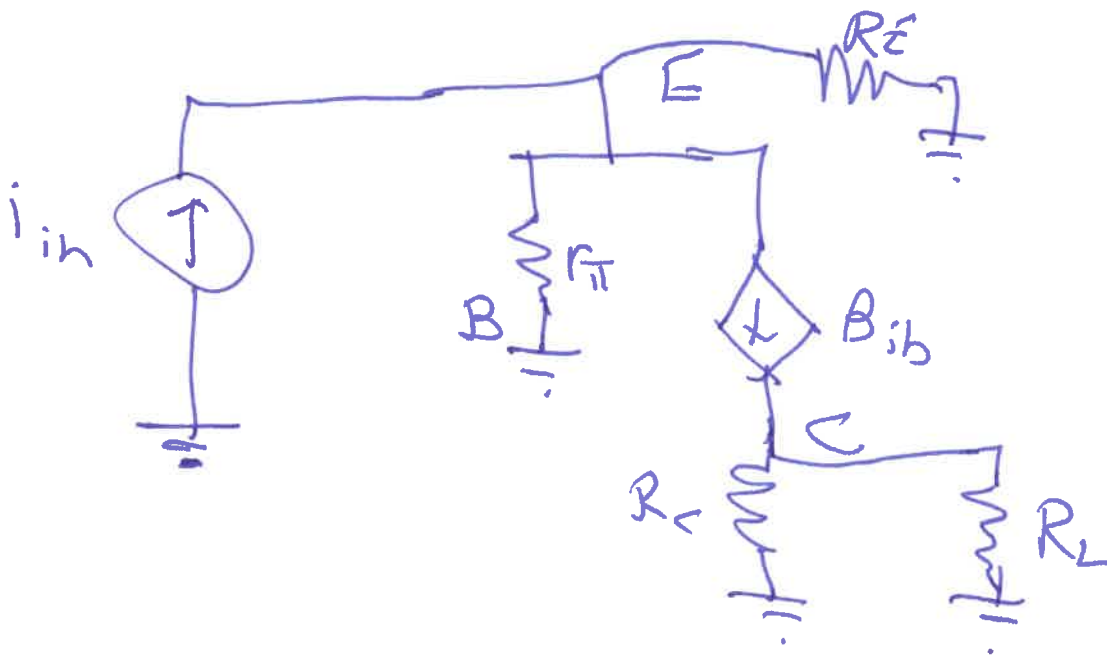
$$r_\pi = \beta \frac{V_T}{I_C} = 100 \times \frac{25 \text{ mV}}{0.92 \text{ mA}} = 2.7 \text{ k}$$



$$i_{in} = i_b \frac{R_E}{R_E + R_{\pi}} + \beta i_b = \frac{10k}{127k} \times 100 i_b$$

$$\approx 100 i_b$$

$$i_{out} = \beta i_b \frac{R_c}{R_E + R_c} \approx 100 i_b$$

$$A_v \approx 1$$

