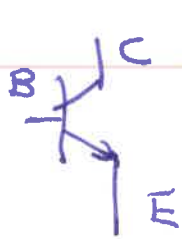


7 Nov 2016


101

FET vs BJT

NPN
BJT





N-channel FET

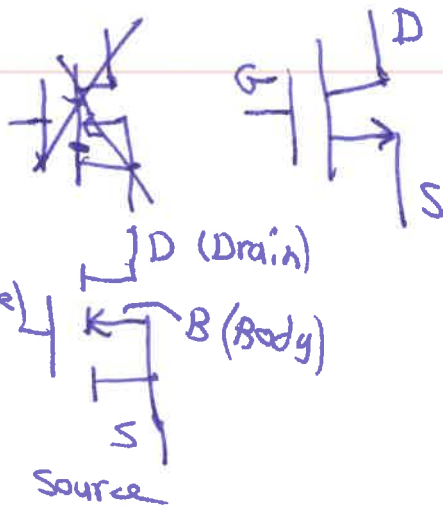

PNP
BJT



P-channel FET

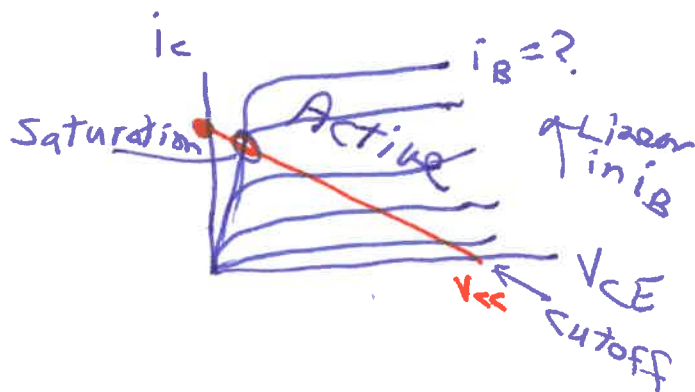
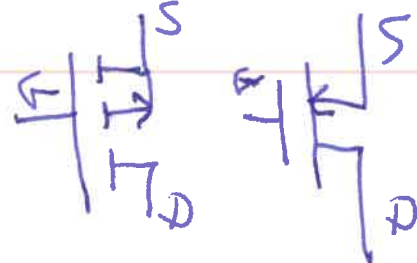


Active mode $\rightarrow$ amps

i_B is the parameter given

$$i_c = \beta i_B$$


$$i_E = (\beta + 1) i_B$$

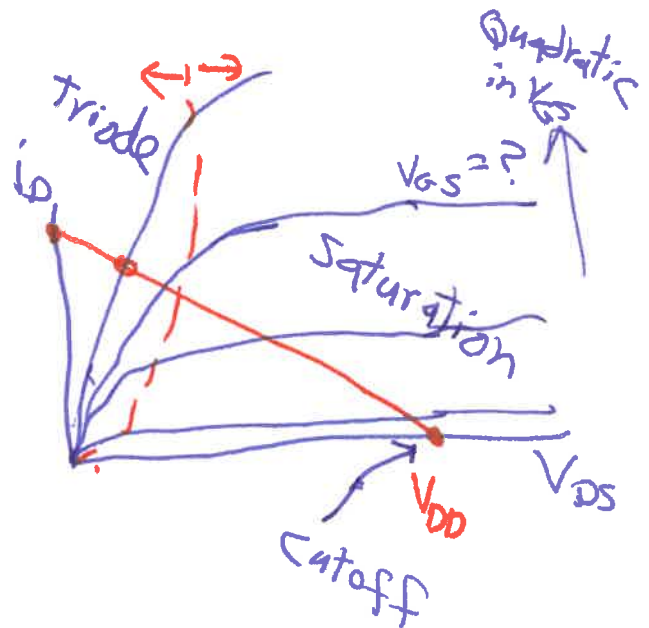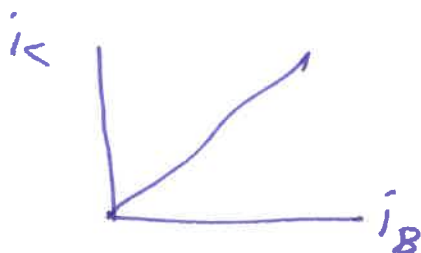


Saturation $\rightarrow$ amps

V_{GS} is the parameter quadratic



$$i_D \propto (V_{GS} - V_{TO})^2$$

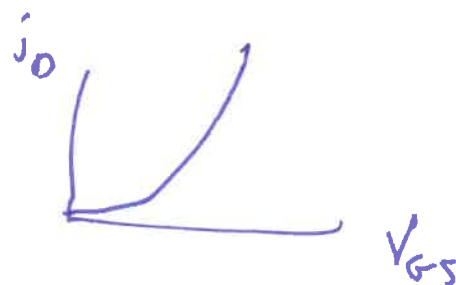

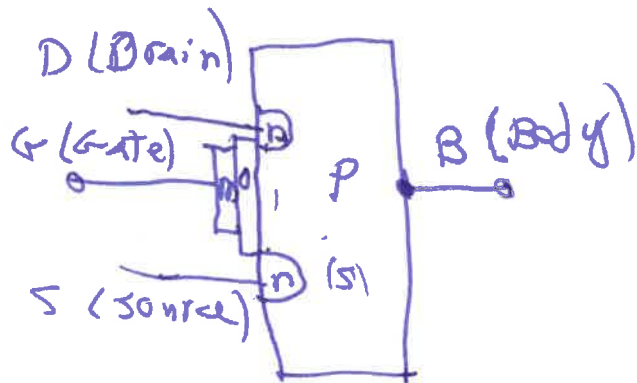Common ~~Emitter~~ or Common Source Power Amp.
 Collector Drain $A_v \approx 1$
 Base Gate $A_i = 1$



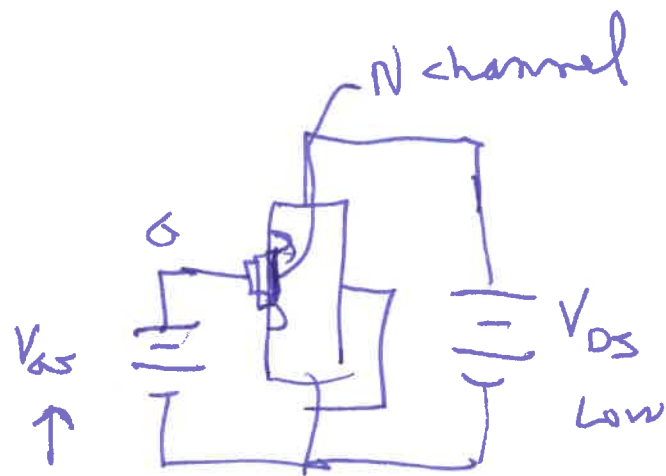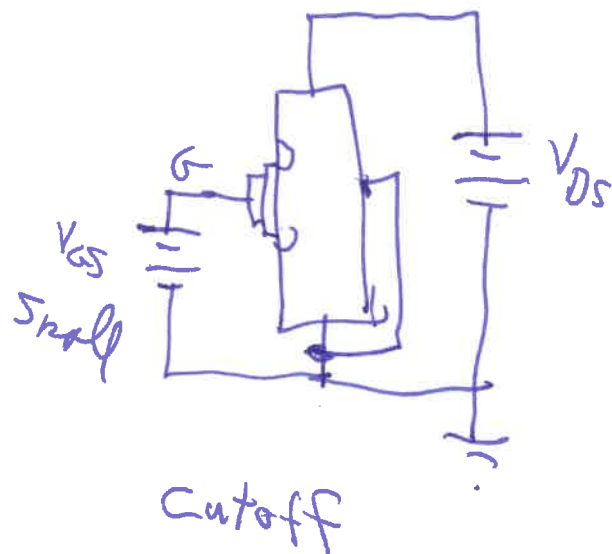
N - m (metal) O (oxide) S (semiconductor)



$$i_D \propto (V_{GS} - V_{TO})$$

$$i_D \propto V_{DS}$$
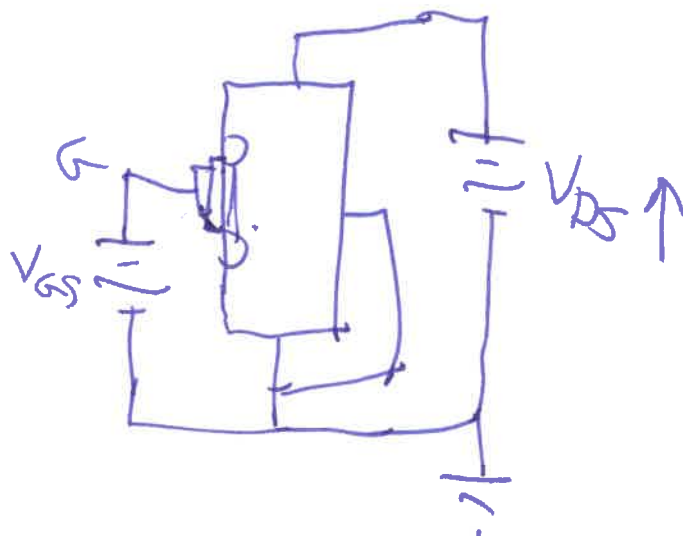
$$i_D = K [2(V_{GS} - V_{TO})V_{DS} - V_{DS}^2] \quad (\text{Triode})$$



$$i_D = K (V_{GS} - V_{TO})^2 \quad \text{Saturation}$$

Triode $i_D = k [2(V_{GS} - V_{TO}) V_{DS} - V_{DS}^2]$

Saturation $i_D = k (V_{GS} - V_{TO})^2$

Boundary $i_D = k V_{DS}^2$