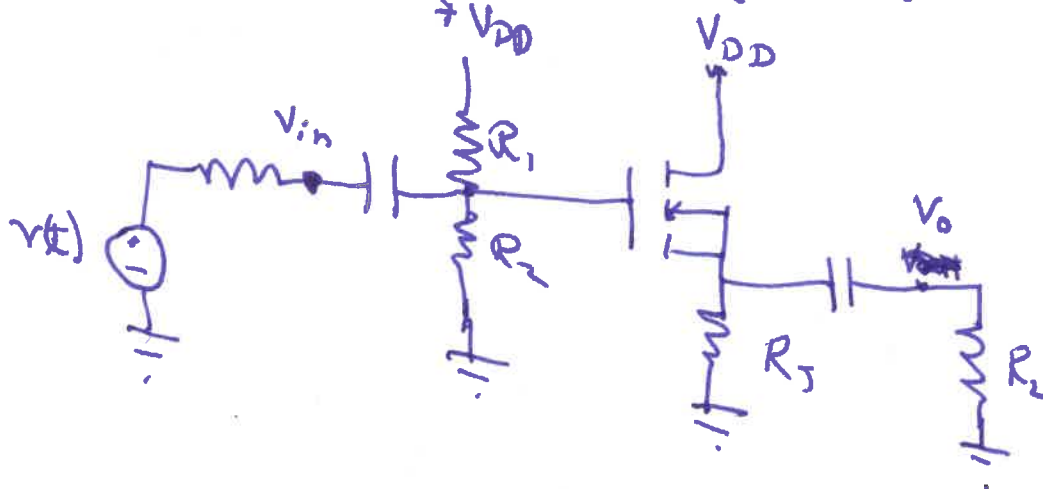


mon 21 Nov 2016


123

Common Drain Amp (Source Follower)



$$V_{in} = V_{GS} + V_o$$

$$V_o = g_m V_{GS} (R_L || R_S || r_d)$$

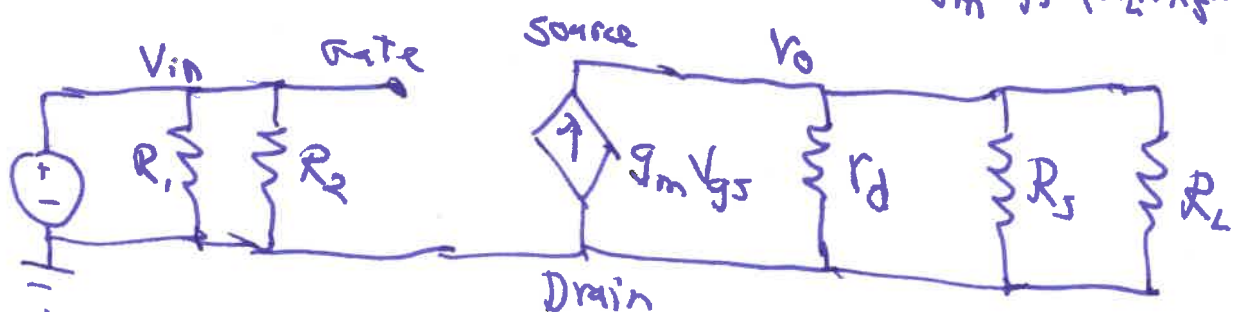

$$V_{in} = V_{GS} + g_m V_{GS} (R_L || R_S || r_d)$$

$$V_{in} = V_{GS} - V_o + (V_{in} - V_o) g_m (R_L || R_S || r_d)$$

$$A_r = \frac{V_o}{V_{in}} = \frac{g_m (R_L || R_S || r_d)}{1 + g_m (R_L || R_S || r_d)}$$

$$g_m = 9 \frac{mA}{V}$$


$$R_L = 300 \Omega \ll R_S, r_d$$

$$A_r = \frac{2.7}{3.7} = 0.73$$

$$R_{in} = R_1 \parallel R_2$$

without
proof
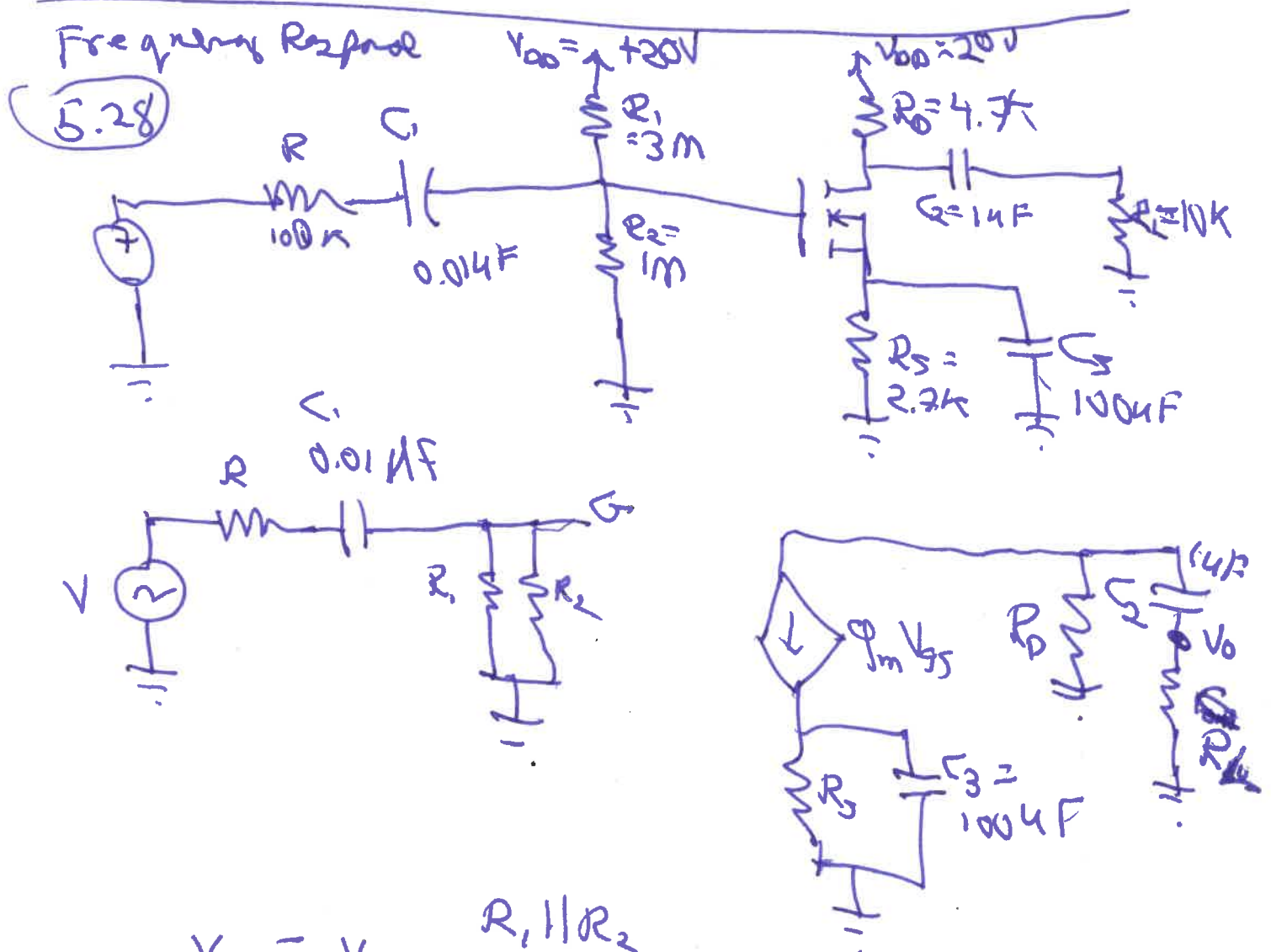
$$R_o = \frac{1}{g_m} \parallel R_5 \parallel r_d$$



$$V_g = V \frac{R_1 \parallel R_2}{R + \frac{1}{j\omega C_1} + R_1 \parallel R_2}$$

$$V_s = i_d \left(R_5 \parallel \frac{1}{j\omega C_3} \right) \quad i_d = g_m V_{gs} = g_m (V_g - V_s)$$

$$i_d = g_m V \frac{R_1 \parallel R_2}{R - \frac{1}{j\omega C_1} + R_1 \parallel R_2} - g_m i_d R_S \parallel \frac{1}{j\omega C_5}$$


$$i_d = \left(1 + g_m (R_S \parallel \frac{1}{j\omega C_5}) \right) g_m V \frac{R_1 \parallel R_2}{R - \frac{1}{j\omega C_1} + R_1 \parallel R_2}$$

$$V_d = -i_d R_D \parallel \left(\frac{1}{j\omega C_2} + R_L \right)$$

$$V_{out} = V_d \frac{R_L}{\frac{1}{j\omega C_2} + R_L} = - \frac{i_d R_D R_L}{R_D + \frac{1}{j\omega C_2} + R_L}$$


$$V_{in} = V \frac{\frac{1}{j\omega C_1} + (R_1 \parallel R_2)}{R + \frac{1}{j\omega C_1} + (R_1 \parallel R_2)}$$

$$A_v = \frac{V_{out}}{V_{in}}$$

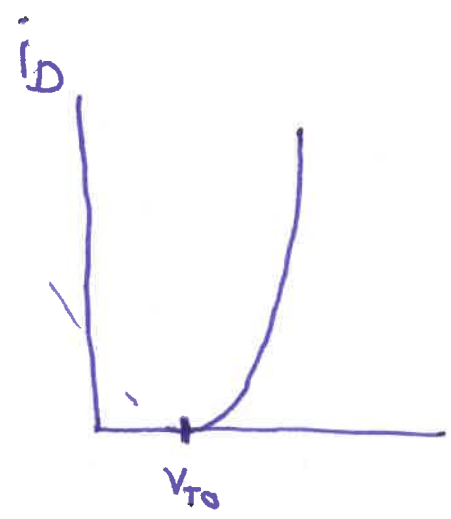

Enhancement
FET

$$i_D = K(V_{GS} - V_{T0})^2$$

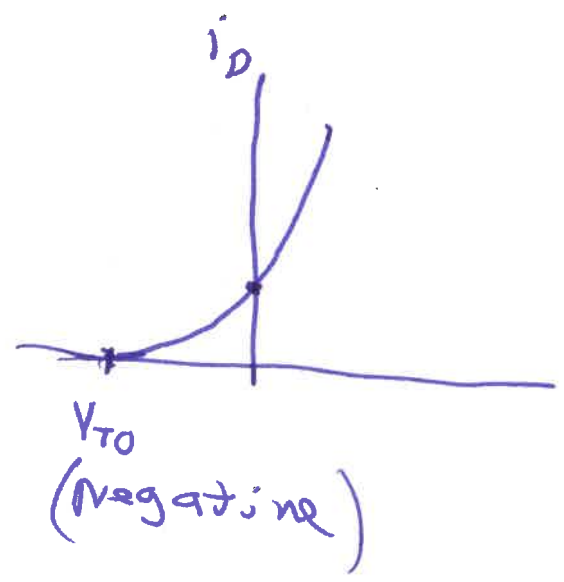


Depletion
FET

Circuit Symbol




V_{GS}

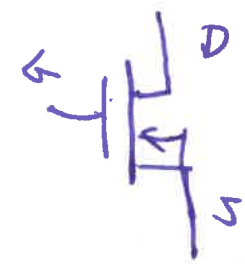


Junction FET

J-FET

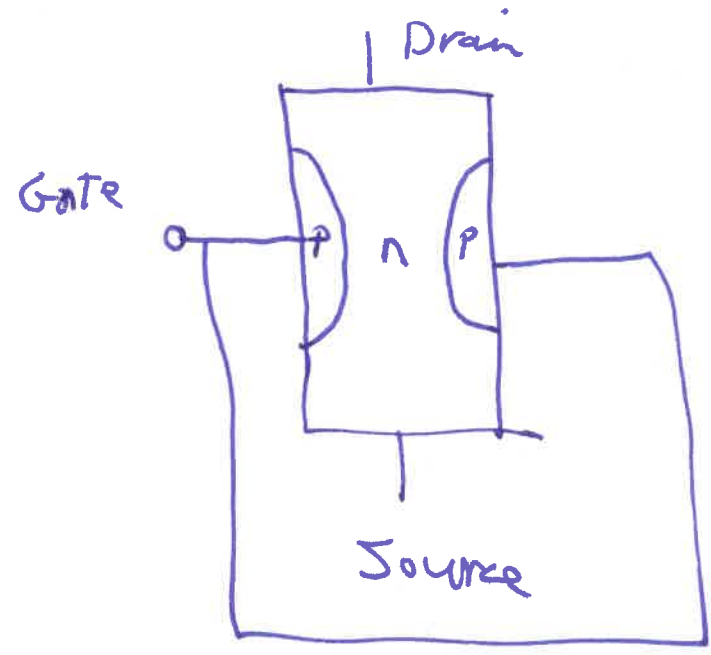

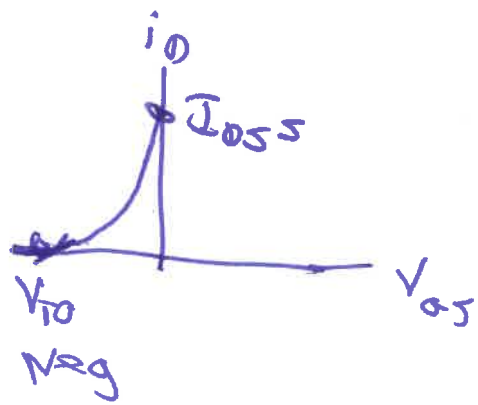$V_{GS} = 0$
Channel exists
Current flows
 $V_{GS} < 0$
Channel is Pinched
Less current flows
 $V_{GS} = V_{T0} \quad i_D = 0$



V_{GS} must be < 0


$$K = \frac{I_{DSS}}{V_{GS}^2}$$

PFET


NFET

	MOSFET	JFET
Enh	y	N
Depl	y	y


N-JFET symbol

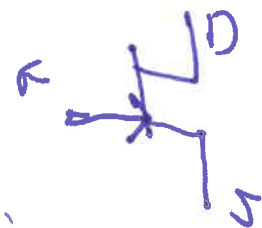

P-JFET

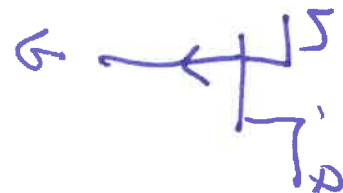


Active Load


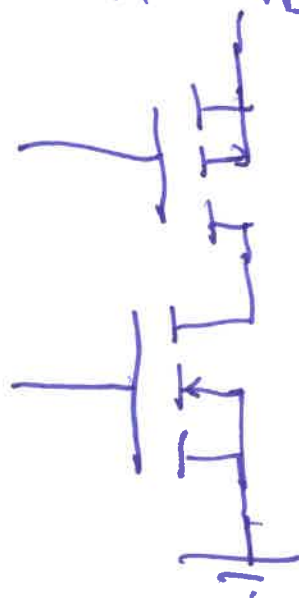


PFET

NFET

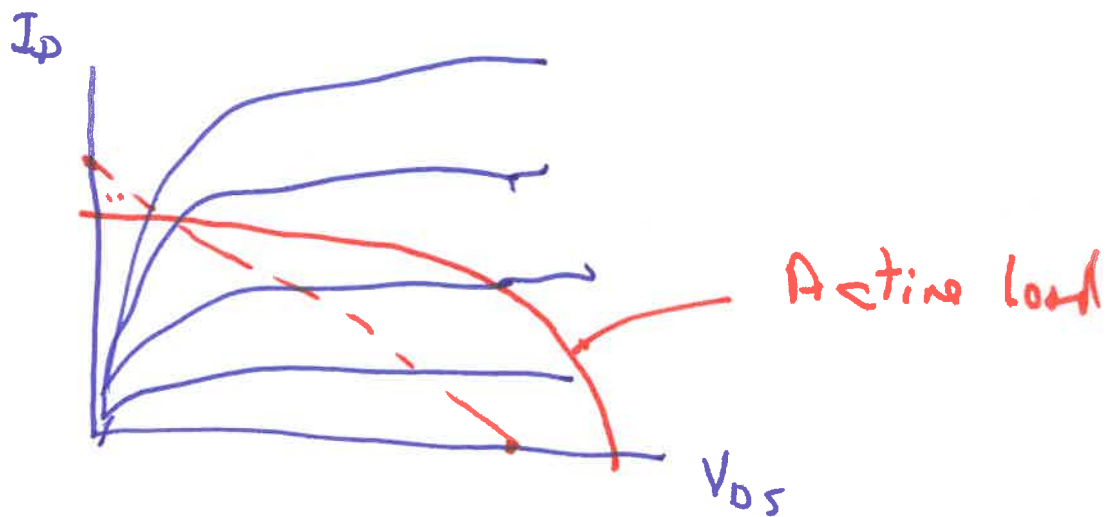

BJT Symbols

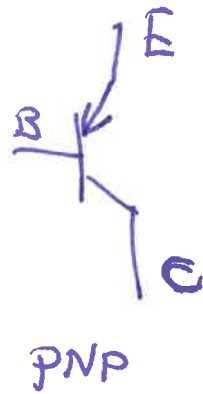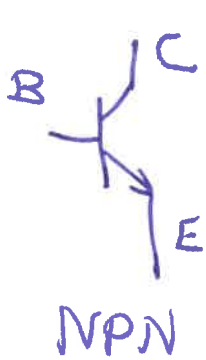


$$i_c = \beta i_B$$

$$i_E = i_c + i_B$$

$$i_E = (\beta + 1) i_B$$

$$i_c = \alpha i_E \quad \alpha = \frac{\beta}{\beta + 1}$$

$$i_c = I_S e^{V_{BE}/V_T}$$

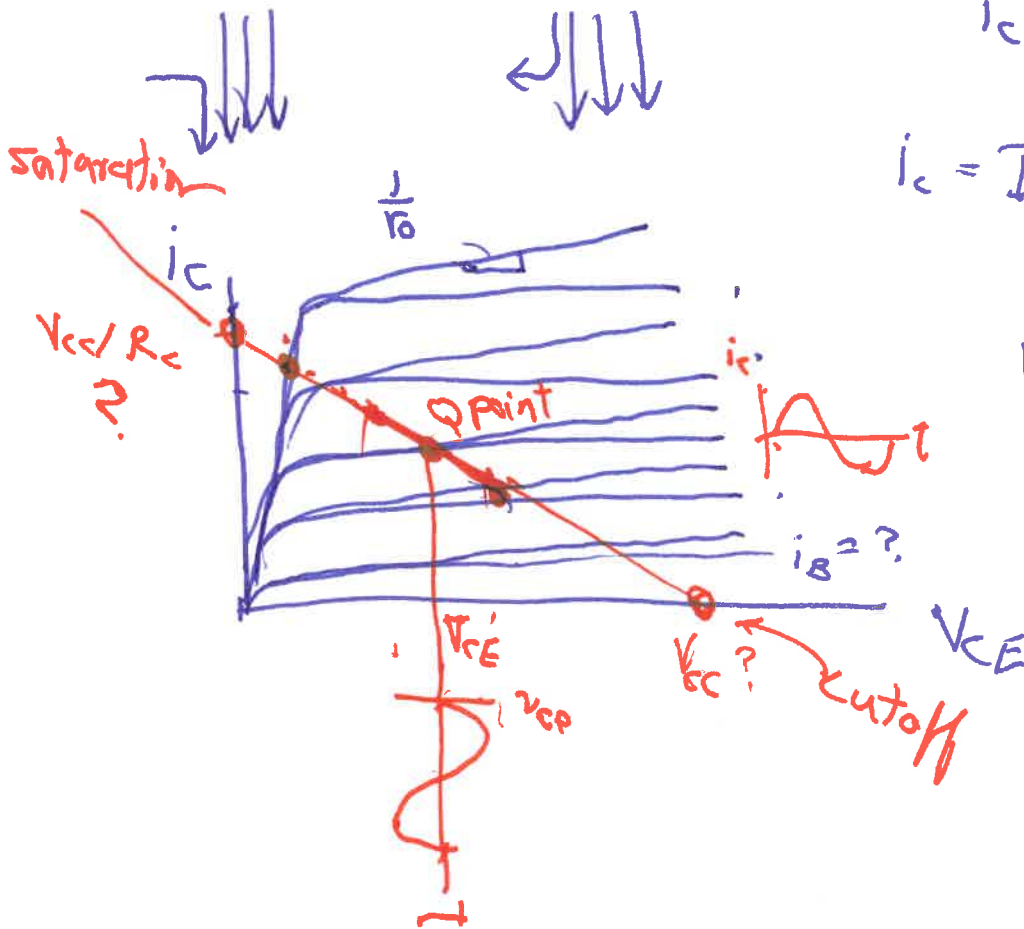

$$r_o = \frac{V_A}{I_C} \leftarrow \text{Early Voltage}$$

$I_C \leftarrow \text{DC "Current Q Point"}$

Active

$$V_{BE} = 0.7V$$

$$I_C = \beta I_B$$

$$V_{CE} > 0.2V$$

Saturation

$$V_{BE} = 0.7V$$

$$V_{CE} = 0.2V$$



(130)

cutoff

$$I_B = 0$$

$$V_{CE} = V_{CC}$$

Small signal model

$$V_T = 25 \text{ mV}$$

$$(a) i_c = \beta i_b$$


or

$$g_m = \frac{I_C}{V_T}$$

$$(b) i_c = g_m V_{be}$$

$$r_{\pi} = \frac{\beta V_T}{I_C}$$
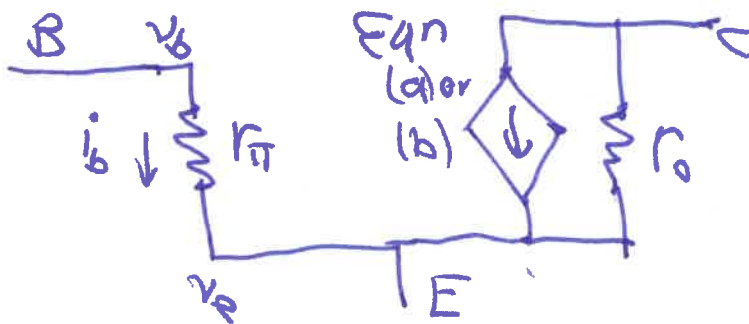
$$r_o = \frac{V_A}{I_C} \quad \text{or} \quad \left(\frac{d i_c}{d V_{CE}} \right)^{-1}$$



AC circuit

Small V_{in} or $i_{in} \rightarrow V_{out}$ or i_{out} R_{in} R_{out}

$$A_v = \frac{V_{out}}{V_{in}}$$

$$A_i = \frac{i_{out}}{i_{in}}$$

$$R_{in} = \frac{V_{in}}{i_{in}}$$

$$R_{out} = \frac{V_{out}(R_L \rightarrow \infty)}{i_{out}(R_L \rightarrow 0)}$$

Typical circuits

121

Common Emitter

$$|A_v| > 1 \quad |A_i| > 1$$

Common Base

$$A_i \approx 1$$



Common Collector

$$A_v \approx 1$$

4 - Resistor Model.

Logic

Inverter

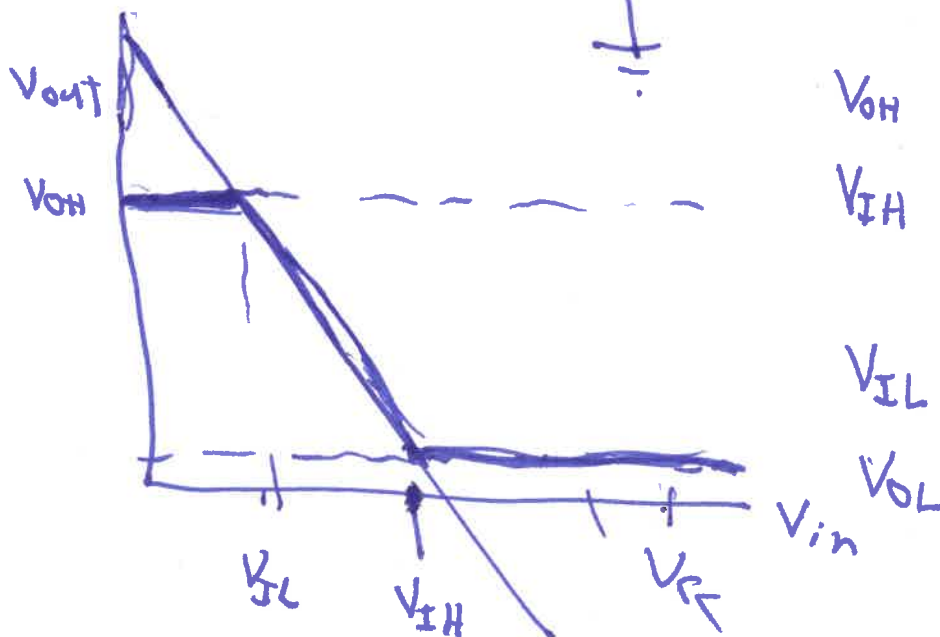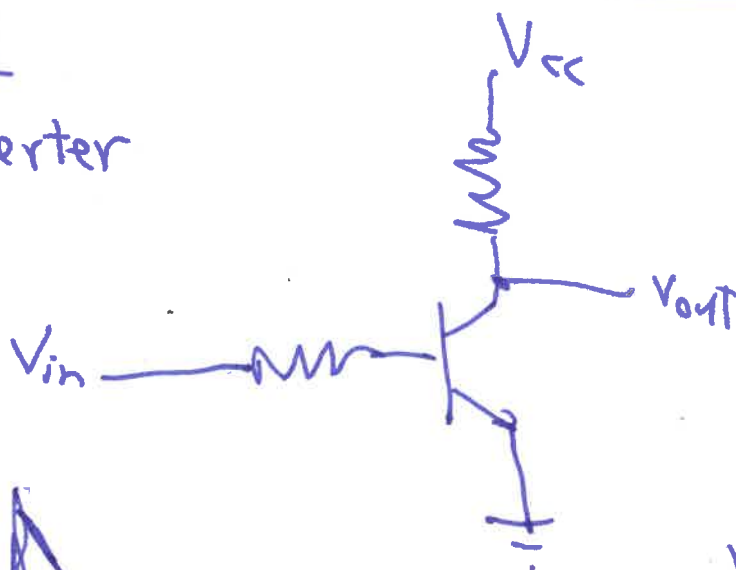

V_{OH}

V_{IH}

V_{IL}

V_{OL}

V_{in}


V_{IL}

V_{IH}

V_{th}

~~V_{OH}~~

~~V_{IH}~~

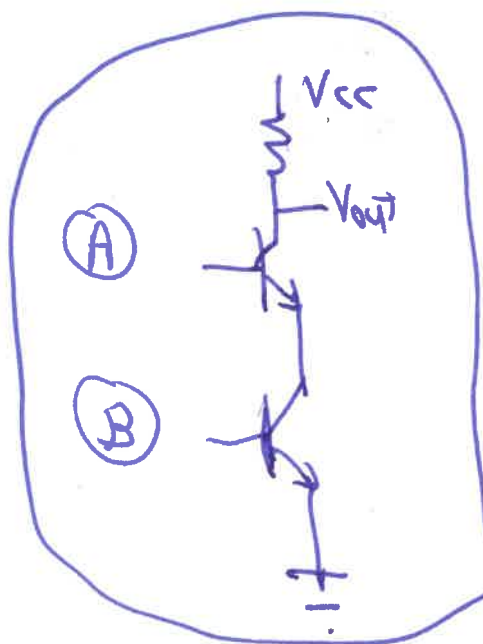

IN			
A	B		
L	L		
L	H		
H	L		
H	H		

out

H	H
H	L
H	L
L	L

NAND NOR

