

Mon 4 Dec 2016

137
141

Announcements:

HW 10 wed


Check Blackboard

Review wed


Watch website

Email Re Final conflicts

Reminder : Inverter

 


NOR

 


A	B	Out
H	H	L
H	L	L
L	H	L
L	L	H

Not (A or B)

NAND

 



Memory

 




5	0	5
0	5	0

Non linearity
Positive feedback } — Bistable system



CMOS Logic Inverter

  

CMOS Inverter Behavior

   


Inverter Transition Trajectory

  

FET Logic Characteristics

- Wide Voltage Swing (0 to 5 V)
 - Good noise margins
- Near Zero Power Consumption (static)
- Low Output Resistance
 - Can Drive Large Loads
 - Low Noise
- High Input Resistance

Output Resistance

 

- Transistor with High v_{GS} ($=v_{DD}$) is in Triode

– Steep IV Slope=Low R

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[(v_{GS} - v_{thr}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$


$$\frac{di_D}{dv_{DS}} = \mu_n C_{ox} \frac{W}{L} \left[(v_{GS} - V_{thr}) - V_{DS} \right]$$

$$\frac{di_D}{dv_{DS}} \approx \mu_n C_{ox} \frac{W}{L} \left[(v_{DD} - V_{thr}) - 0 \right]$$

$$R_{DS} \approx \frac{1}{\mu_n C_{ox} \frac{W}{L} (v_{DD} - V_{thr})} \approx \frac{1}{20 \times 10^{-6} (A/V^2) \times 50 \times 5V} = 200 \Omega$$


Input Resistance

 - Input to Gates Only
 - Infinite Resistance



3 cases: Triode + Sat
sat + Triode
sat + sat

Equations for FET Logic (1)

 

Now, Assume $\mu_n = \mu_p \times 2$
Also Same W/L and V_{thr}
 $\left(\frac{W}{L}\right)_n = \frac{1}{2} \left(\frac{W}{L}\right)_p$

Triode $V_{out} < V_{in} - V_{thr}$

$$i_{DP} = \mu_p C_{ox} \frac{W}{L} \left[V_{DD} - V_{in} - |V_{thr}| \right] \left[V_{DD} - V_{out} - \frac{1}{2} (V_{DD} - V_{out})^2 \right]$$

Saturation

$$i_{DP} = \mu_p C_{ox} \frac{W}{L} \frac{(V_{DD} - V_{in} - |V_{thr}|)^2}{2} \left(1 + \frac{V_{DD} - V_{out}}{V_A} \right)$$


Triode $V_{out} > V_{in} + |V_{thr}|$

$$i_{DN} = \mu_n C_{ox} \frac{W}{L} \left[(V_{in} - V_{thr}) V_{out} - \frac{1}{2} V_{out}^2 \right]$$

Saturation

$$i_{DN} = \mu_n C_{ox} \frac{W}{L} \frac{(V_{in} - V_{thr})^2}{2} \left(1 + \frac{V_{out}}{V_A} \right)$$

Equations for FET Logic (2)

 

Both in Saturation

$$i_D = \mu C_{ox} \frac{W}{L} \left(\frac{V_{DD} - v_{in} - |V_{thr}|}{2} \right)^2 \left(1 + \frac{V_{DD} - v_{out}}{V_A} \right)$$

$$i_D = \mu C_{ox} \frac{W}{L} \left(\frac{v_{in} - V_{thr}}{2} \right)^2 \left(1 + \frac{v_{out}}{V_A} \right)$$

$$\frac{(V_{DD} - v_{in} - |V_{thr}|)^2}{2} \left(1 + \frac{V_{DD} - v_{out}}{V_A} \right) = \frac{(v_{in} - V_{thr})^2}{2} \left(1 + \frac{v_{out}}{V_A} \right)$$

$$\text{Trust Me } v_{out} = \frac{V_{DD}}{2} - \frac{V_{DD} + 2V_A}{V_{DD} - 2V_{thr}} \left(v_{in} - \frac{V_{DD}}{2} \right)$$

Equations for FET Logic (3)

Both in Saturation



Upper Limit $v_{out} = V_{DD}$


$$\frac{V_{DD}}{2} = -\frac{V_{DD} + 2V_A}{V_{DD} - 2V_{thr}} \left(v_{in} - \frac{V_{DD}}{2} \right)$$

$$v_{in} = \frac{V_{DD}}{2} - \frac{V_{DD} - 2V_{thr}}{2} \frac{V_{DD} + 2V_A}{V_{DD} - 2V_A}$$

Lower Limit $v_{out} = 0$

$$v_{in} = \frac{V_{DD}}{2} + \frac{V_{DD} - 2V_{thr}}{2} \frac{V_{DD} + 2V_A}{V_{DD} - 2V_A}$$

Regions of Operation

 

It is left as an exercise for the student to calculate the curve in the other two regions.