Homework Set 10
EECE2412: Electronics– Fall 2014
Due Wednesday, 3 December 2024

Prof. Charles A. DiMarzio

24 November 2024

File: 12521/hw10.tex

1 NFET

Solve Problem 5.7 in the Text (Hambley).

2 Load Line

Solve Problem 5.18 in the Text (Hambley).

3 Common–Source Amplifier

Solve Problem 5.38 in the Text (Hambley).

4 Common–Drain Amplifier

Solve Problem 5.46 in the Text (Hambley).

5 Common–Gate Amplifier

Solve Problem 5.72 in the Text (Hambley).