Homework Set 7
EECE2412: Electronics– Fall 2014
Due Wednesday, 23 Oct 2024

Prof. Charles A. DiMarzio

16 October 2024

File: 12521/hw7.tex

1 Transistor Parameters

Solve Problem 4.8 in the Text (Hambley).

2 Parallel Transistors

Solve Problem 4.13 in the Text (Hambley).

3 Simple Circuits: NPN and PNP

Solve Problem 4.14 in the Text (Hambley).

4 PSpice

Solve Problem 4.18 in the Text (Hambley).

5 Load Line

Solve Problem 4.20 in the Text (Hambley).

Continued →

6 Operating Regions

Solve Problem 4.28 in the Text (Hambley).