Homework Set 8
EECE2412: Electronics– Fall 2014
Due Wednesday, 30 Oct 2024

Prof. Charles A. DiMarzio

23 October 2024

File: 12521/hw8.tex

1 DC Solutions

Solve Problem 4.33 in the Text (Hambley).

2 More DC Solutions

Solve Problem 4.34 in the Text (Hambley).

3 More DC Solutions

Solve Problem 4.38 in the Text (Hambley).

4 AC Parameters

Solve Problem 4.42 in the Text (Hambley).

Continued . . .

5 AC Circuits

Solve Problem 4.43 in the Text (Hambley).

6 Common Emitter

Solve Problem 4.45 in the Text (Hambley).