Homework Set 9
EECE2412: Electronics– Fall 2014
Due Wednesday, 6 November 2024

Prof. Charles A. DiMarzio

30 October 2024

File: 12521/hw9.tex

1 Emitter Follower

Solve Problem 4.51 in the Text (Hambley).

2 AC Solutions: Common Emitter

Solve Problem 4.53 in the Text (Hambley).

3 AC Equations: Common Emitter

Solve Problem 4.54 in the Text (Hambley).

4 Logic Circuit

Solve Problem 4.62 in the Text (Hambley).

5 Logic Circuit Analysis

Solve Problem 4.64 in the Text (Hambley).